
 


# TM-implementation

 

We take liberties with the terms "TM" and "UTM", but in basic concepts we're ok.  
To build any TM, WE NEED:

--- FSM:


- state
- logic functions (output and next-state)

--- Tape: a variety of methods to RW symbols, we'll use registers (RAM).

--- Symbol set = a set of fixed length bit strings, e.g.,

- length 1 strings:  $S = \{0,1\}$  (symbol set has 2 symbols)
- length 2 strings:  $S = \{00, 01, 10, 11\}$  (4 symbols)
- length 3 strings:  $S = \{000, 001, 010, 011, 100, 101, 110, 111\}$  (8 symbols)

## Build FSM even-odd parity

 

functions

$$\left\{ \begin{array}{l} \text{OUT} : S \times \Sigma \rightarrow \Sigma \\ \text{Next\_State} : S \times \Sigma \rightarrow S \end{array} \right.$$

$$\Sigma = \text{Symbols} = \{0,1\}$$

$$S = \text{States} = \{A,B\} \xrightarrow{\text{encode}} \{0,1\}$$

OUT	
(A,0)	→ 0
(A,1)	→ 1
(B,0)	→ 1
(B,1)	→ 0

Next\_State	
(A,0)	→ A
(A,1)	→ B
(B,0)	→ B
(B,1)	→ A

We Need:

- functions
- STATE ELEMENTS

$$\{A,B,C,D\} \xrightarrow{\text{encode}} \{00,01,10,11\}$$

- in hardware for our simulator/computer/UTM.
- in desc. language so we can describe any TM.

Boolean functions

For our "UTM/simulator" to be universal (able to simulate any TM)

WE MUST HAVE:

- a description language able to describe any TM,
- a UTM/Simulator that can understand that language.

## LANGUAGE

Language (ISA) needs to be able to describe:

- Arbitrary set of states, including regs (= vars)
- Arbitrary set of symbols
- Arbitrary branching (via binary trees)
- RW to tape
- Arbitrary functions (next-state, output)

## UTM/simulator

simulates using

- current state (PC and var memory)
- read tape (LDR => reg)
- output function:  
ADD, AND, NOT ...
- next-state function:  
ADD, AND, NOT ...
- write tape (STR)
- change state  
PC ++, JMP, BRp, BRz, BRn  
STR => data state (var memory)


Represent description using small pieces, "instructions" that are "executed" by machine cycle:

- Instruction fetch
- Operand fetch
- Execute
  - Function evaluation
  - Change state (branching)
- Operand store

Separate UTM into 2 pieces

- FSM controller (simulator's state)
- Datapath

description of simulated TM

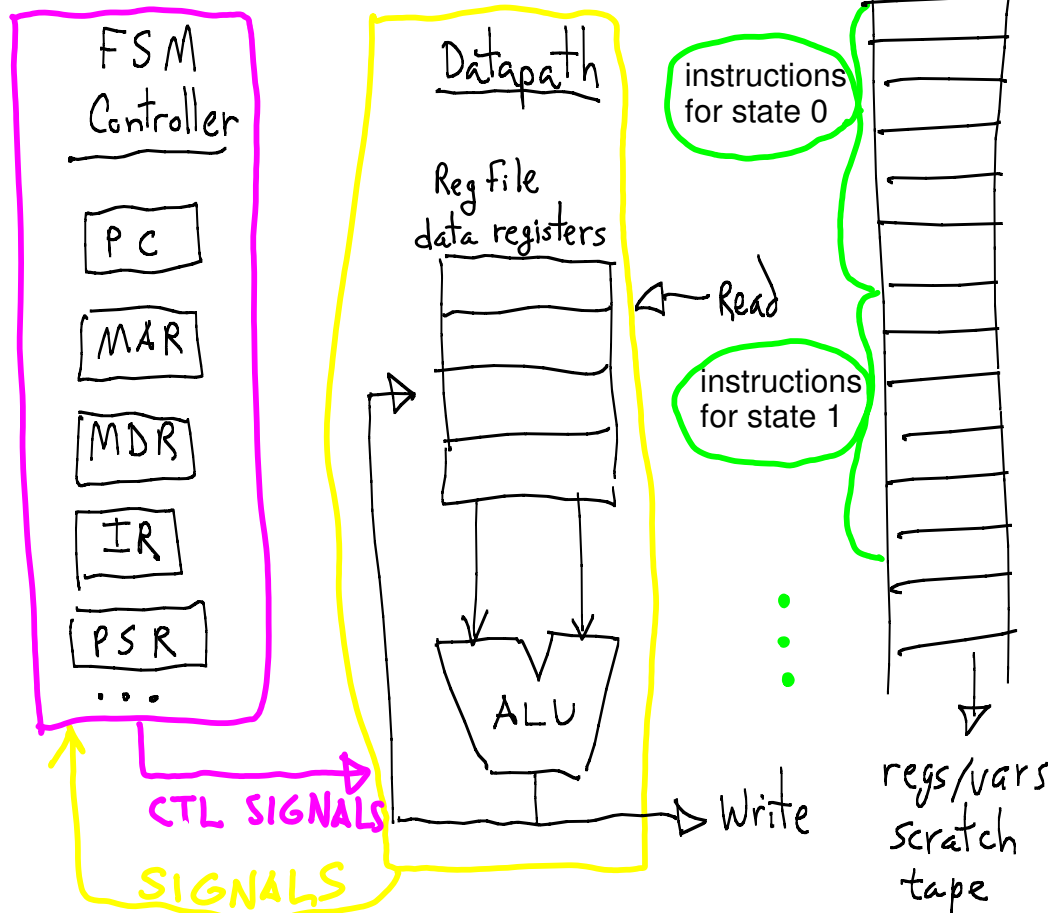







FSM Controller uses registers (e.g., PC) to remember:

- simulated machine's state (control state + data reg) (simulated data reg is var on tape.)
  - simulated symbols read (RegFile)
  - simulated machine's write symbols (RegFile)
  - its own machine state (controller state), ie. step of simulation
  - partial steps of function evaluations (next-state, output)
- these are in data registers, mostly, but also PSR, on tape, ...

# STATE ELEMENTS


pos. edge-triggered FF

Problem:

   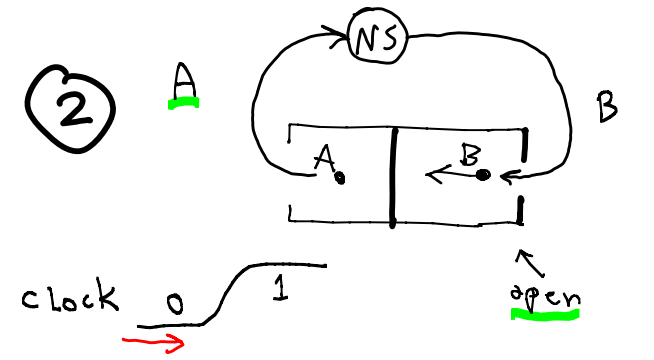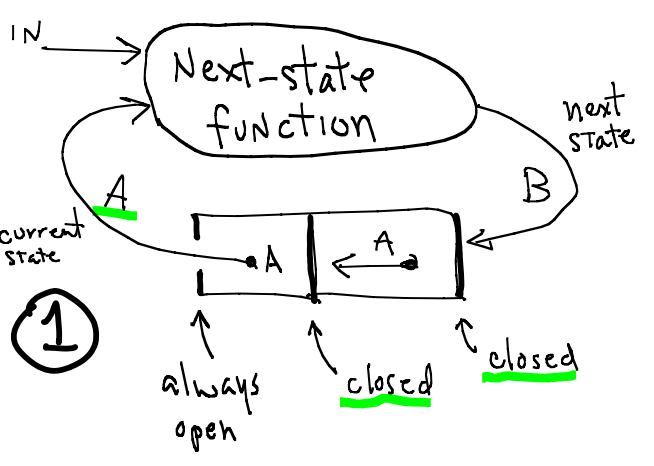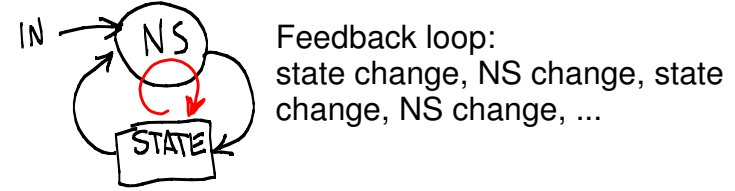

STATE CHANGE


 
## Valid/not Valid Timing, things take time



rise Time logic propagation

state change delay logic delay


delay until OUT responds to IN 0 → 1

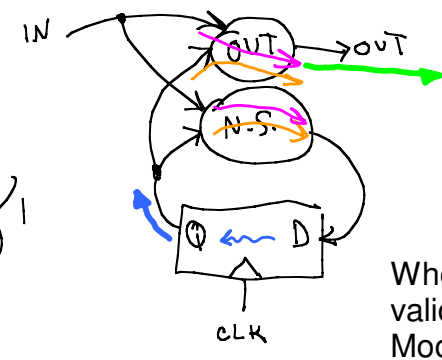 

When is OUT valid? Do better w/ Moore machine?


# One-hot FSM controller
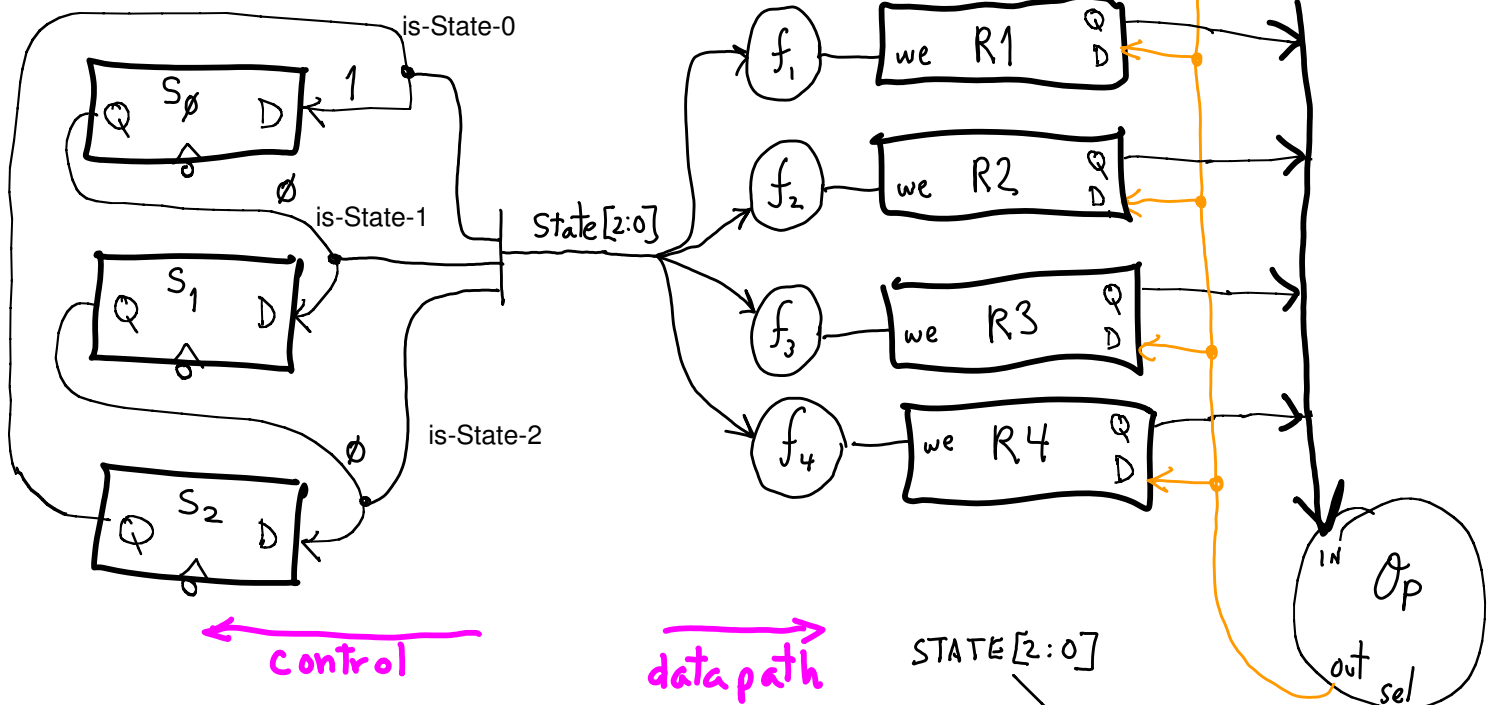
# Data registers and functions (write enable, select Operation/function)



Exactly one reg's Q = 1, represents controller's state.  
 State affects datapath:  
 --- which data registers are write enabled,  
 --- what function is selected as Op.  
 (IR opcode bits plus State affect Op select, IR is part of control state.)

## Control Branching in 1-hot?

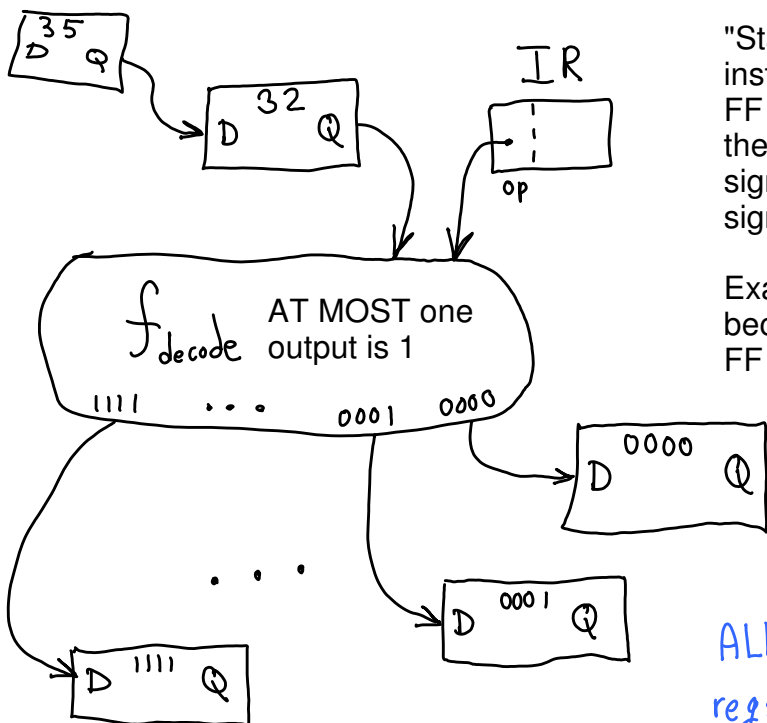


## LC3 Decode state-32
 
### Control branching

"State-0001" (ADD instruction's first state):  
 FF input is a function of the value of the State-32 signal and the 4-bit signal from IR[15:12].

Exactly ONE FF will become hot, if state-32 FF is hot.



ALL control state regs are write enabled

Can we describe functions such as Select? How? Two possibilities:


- (1) describe for any  $x$  how to calculate  $f(x)$ .
- (2) show for all  $x$ , the value of  $f(x)$ .

We choose (2) ==> a table.

INPUTS:					OUTPUTS:					
state-32	IR[15]	IR[14]	IR[13]	IR[12]	1111	1110	1101	...	0001	0000
1	0	0	0	0	0	0	0	...	0	1
1	0	0	0	1	0	0	0	...	1	0
...	...	...	...	...	...	...	...	...	...	...
1	1	1	1	0	0	1	0	...	0	0
1	1	1	1	1	1	0	0	...	0	0

(ignore all rows for state-32 == 0; they are not relevant: all outputs are 0.)

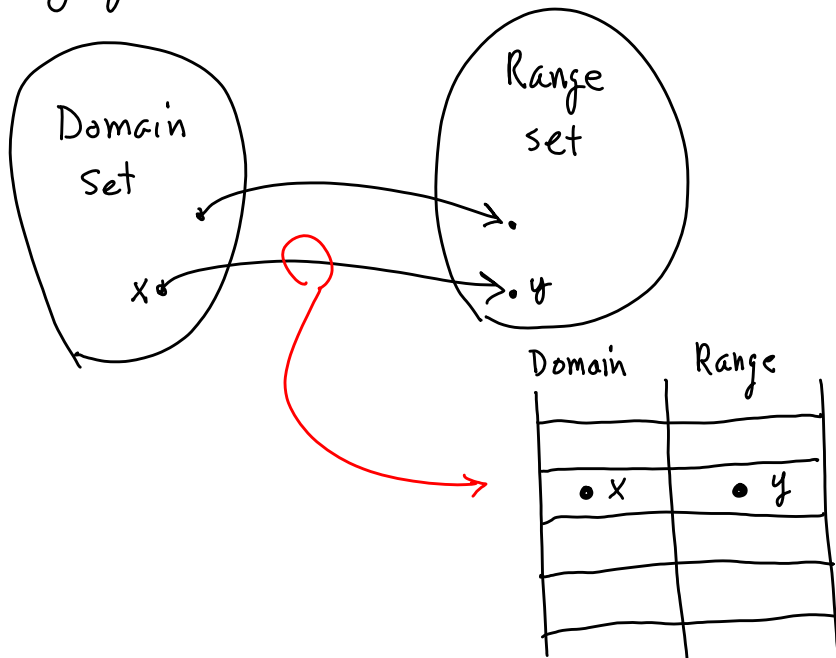Any function can be written as a table<sup>\*</sup>



what about relations that are not functions?  
 $(x, y)$   
 $(x, z)$   
 partial functions?

\* what about  $\mathbb{R}$ ?

\* what about  $2^{\mathbb{R}}$  (subsets of  $\mathbb{R}$ )?

# OR, microcoded controller

A-Reg has controller's current state.  
STATE is used as address to ROM.  
Memory word selected by A-Reg's content (address)


Each row (word) of ROM has datapath control bits.  
C-Reg has current "control word", its outputs control datapath.

Controller's Next-state bits are in next-state fields of C-Reg.

Control branching, One possibility:

- branching is two-way, NS1 or NS2
- MUX chooses one
- MUX.select =  $f(\text{STATE}, \text{IR}, \text{other inputs})$
- (Requires multi-stage branching for 16-way decode for LC3 ISA)

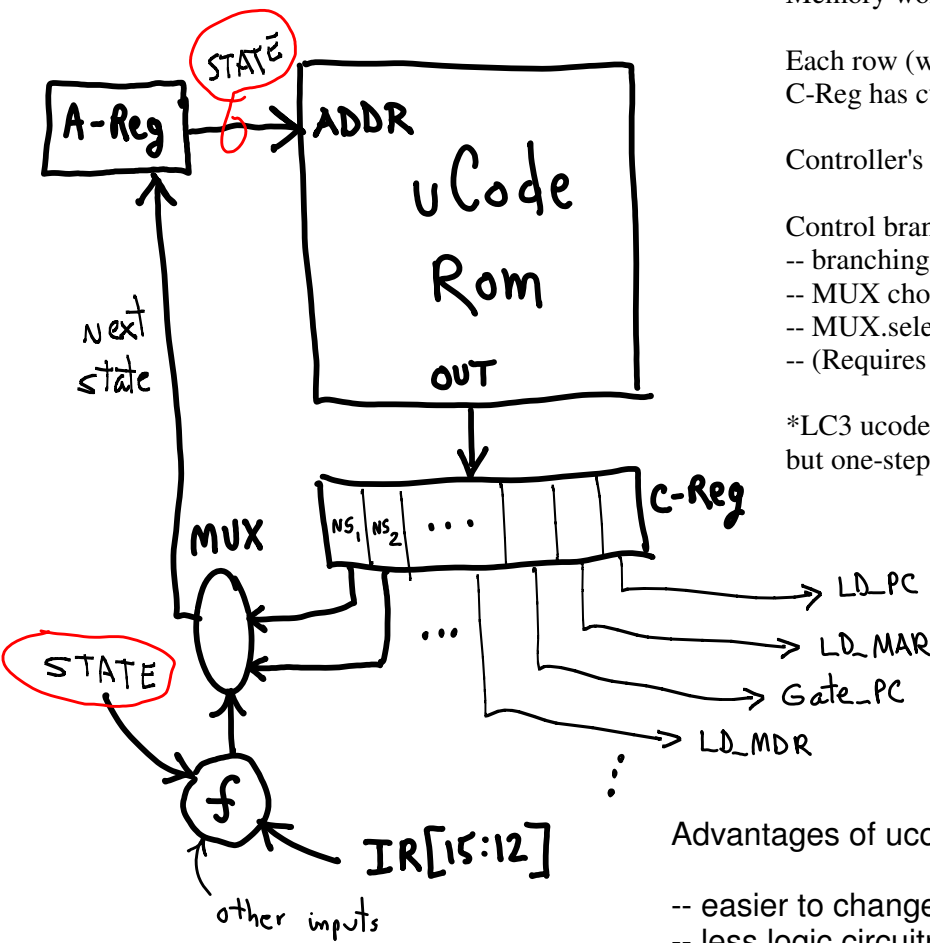\*LC3 ucode controller has different branch scheme. Harder to grasp, but one-step, 16-way branching.



} Control signals to Datapath

Advantages of ucode controller:

- easier to change
- less logic circuitry to figure out
- easier to expand to include new functionality: install bigger ROM.

Advantages of "random logic" controller:

- faster
- smaller (?)
- easier to distribute throughout machine

Let's get back to simpler things (FSM).


We will have:

--- 1-bit state elements


--- 1-bit function elements

How do we put them together to form a FSM?

# A mod-3 machine:

 


## STATE ENCODINGS

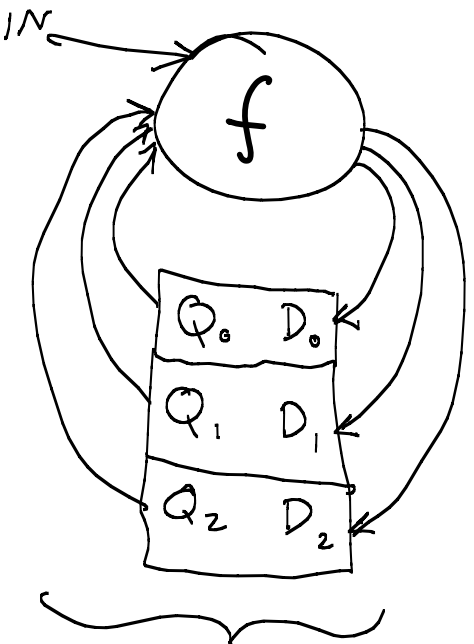

3 STATE ELEMENTS

One-hot

STATE	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
A	0	0	1
B	0	1	0
C	1	0	0

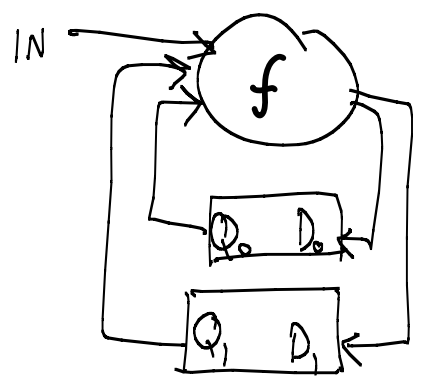

2 state elements

STATE	Q <sub>1</sub>	Q <sub>0</sub>
A	0	0
B	0	1
C	1	1

Can we describe f ? Let's use a table.

inputs:				outputs:			
IN	Q2	Q1	Q0	D2	D1	D0	
0	0	0	1 (A)	0	0	0 (A)	
1	0	0	1 (A)	0	1	0 (B)	
0	0	0	1 (B)	0	1	0 (B)	
1	0	0	1 (B)	0	1	0 (C)	
0	0	0	1 (C)	0	1	0 (C)	
0	0	0	1 (C)	0	1	0 (A)	
*	*	*	*	x	x	x	

("\*" row is for all other rows not shown. "X" is for don't care, either 0 or 1, since cannot happen.)

Can we describe f ? Let's use a table.

inputs:			outputs:	
IN	Q1	Q0	D1	D0
0	0	0 (A)	0	0 (A)
1	0	0 (A)	0	1 (B)
0	0	1 (B)	0	1 (B)
1	0	1 (B)	1	1 (C)
0	1	1 (C)	1	1 (C)
0	1	1 (C)	0	0 (A)
*	*	*	x	x

("\*" rows cannot be reached.)

If we have a universal language (able to describe any TM)

All we need to know is How To Build:

--- 1-bit state elements?

--- 1-bit functions?