
 


# TM-implementation


 


$k$ -bit symbols  
 e.g.,  $\Sigma = \{000, 001, \dots, 111\}$






FSM has input/output, but from/to where?

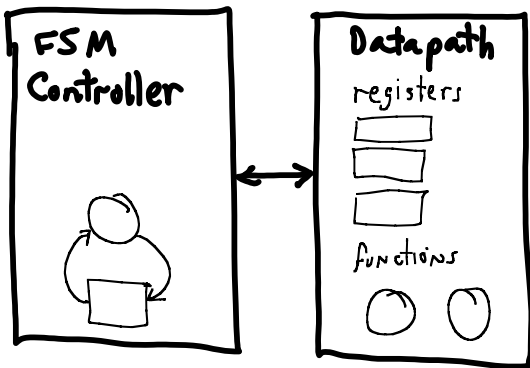 - (1) Other FSMs in same machine
- (2) Feedback loops





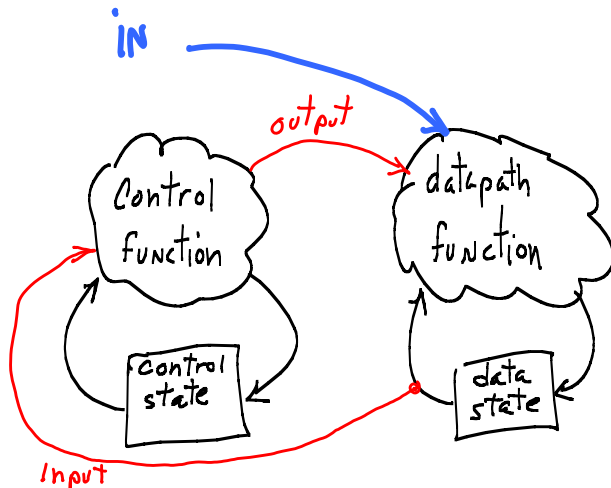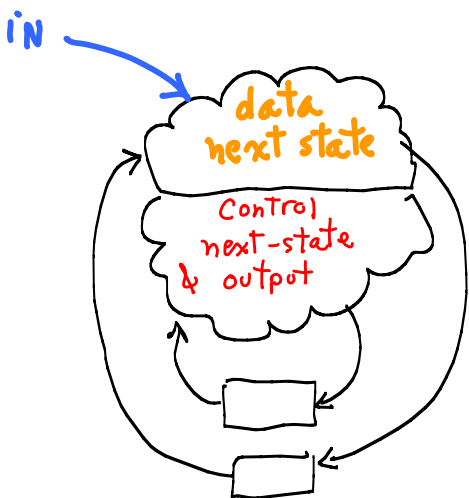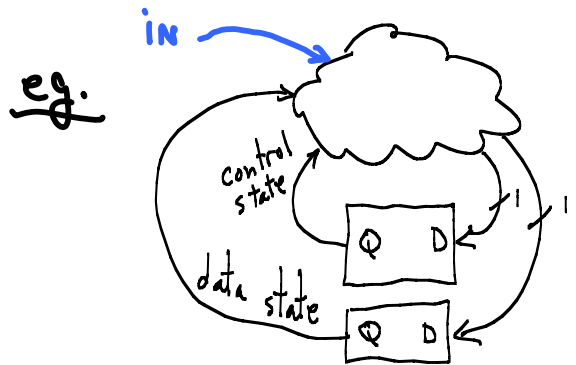We like to separate state into two "types", control and data state.  
 Eg., some state elements are for "control" state, and some are for "data" state.



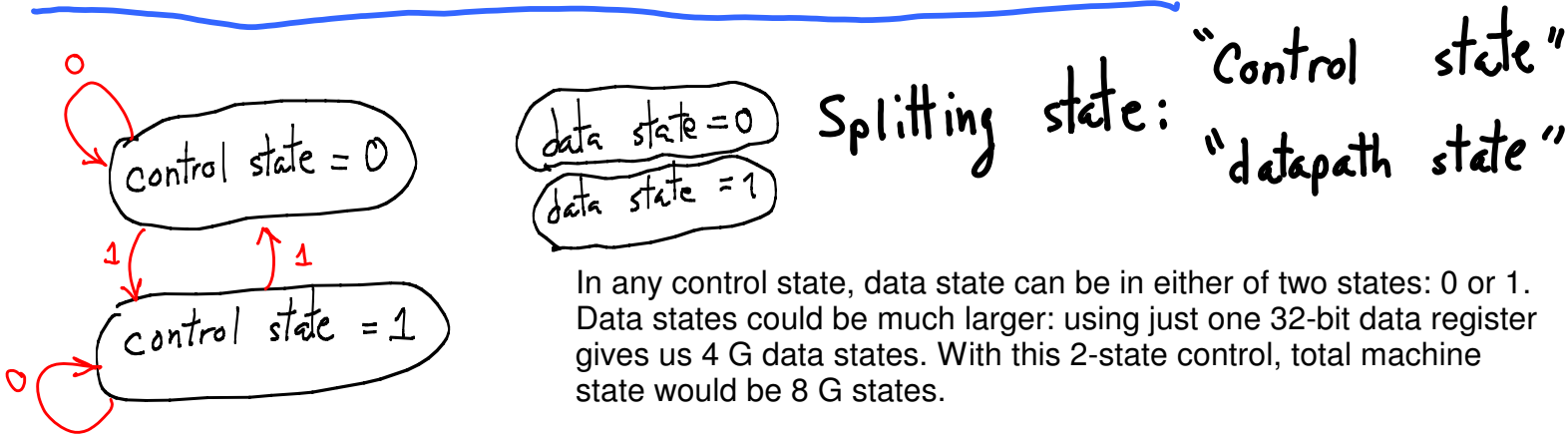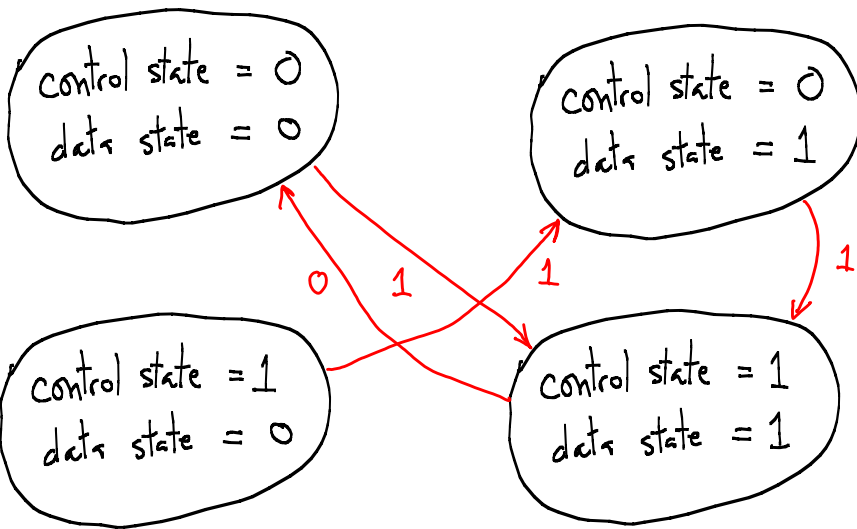
# Total machine state

Suppose a FSM with 1-bit control-state element and 1-bit data-state element. Total is 2-bits of state; 4-state machine. State diagram quickly becomes a mess. What if 2-bit data-state? 8-state total FSM, but only 2 control states.



## FSM - circuits, implementation example

## Serial parity bit machine

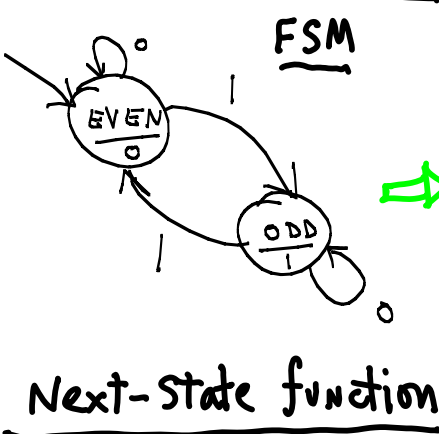


Q	IN	D = Q <sup>+</sup>
0	0	0
0	1	1
1	0	1
1	1	0

$0 \rightarrow 0 = m_1$   
 $1 \rightarrow 1 = m_2$

$$D = \bar{Q} \cdot IN + Q \cdot \bar{IN}$$

$$= Q \oplus IN$$

## Moore Machine

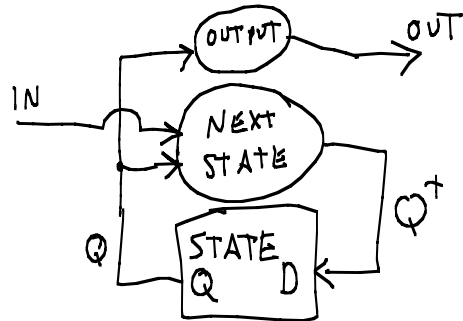

**STATE ENCODING**

EVEN	Q = 0
ODD	Q = 1


**OR**

EVEN	Q <sub>0</sub> = 1, Q <sub>1</sub> = 0
ODD	Q <sub>0</sub> = 0, Q <sub>1</sub> = 1

**OR**

EVEN	Q <sub>0</sub> = 1, Q <sub>1</sub> = 0
ODD	Q <sub>0</sub> = 0, Q <sub>1</sub> = 1

## Next-state circuit

 

## OUTPUT FUNCTION


Q	OUT
0	0
1	1

OUT = Q

## OUTPUT circuit



# STATE elements

 

Suppose A.out = 0  
 → B.out = 1  
 → A.out = 0  
 Stable!

A.out = 1  
 → B.out = 0  
 → A.out = 1  
 Stable


Q = 0

Q = 1


two states! hooray!

that was easy, but hey!  
 No inputs!


X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

 

can we use inputs?

 

forces 1, this is still a NOT

 


forces 1, now in other stable state!

hmm, if X=1, looks like NOT  
 hmm, if X=0, always gives 1

The state is latched (captured) when  $\bar{S} = \bar{R} = 1$ .  
 NAND-NAND latch


$\bar{S}$	$\bar{R}$	STATE
1	1	INV-INV Loop, 2 possible stable states: Q=0 or Q=1
0	1	1-INV Loop, 1 possible state: Q=1
1	1	INV-INV Loop, latched state Q=1
1	0	INV-1 Loop, one possible state: Q=0
1	1	INV-INV Loop, latched state Q=0

Yay! State element w/ input!

 

S = set  
 R = reset


Can we use this for a FSM state element?

 


Oh No!

any input change → to output → state change!

# CLOCKING, part 1: Gating D-Latch

 
 
$$\begin{array}{l} B=0 \\ Y=0 \\ B=1 \\ Y=A \end{array}$$




A	B	Y = A · B
0	0	0
0	1	0
1	0	0
1	1	1



*Note: A yellow box highlights the first two rows (0,0) and (0,1) with an arrow pointing to S=R=0. A blue box highlights the last two rows (1,0) and (1,1).*

Enable = 0, input is ignored  
 Enable = 1, input allowed through:  $R=R', S=S'$

S-R latch w/ Enable


 


conceptually simplify

  


D-latch w/ Enable

## 2-phase clocking, D-FF

 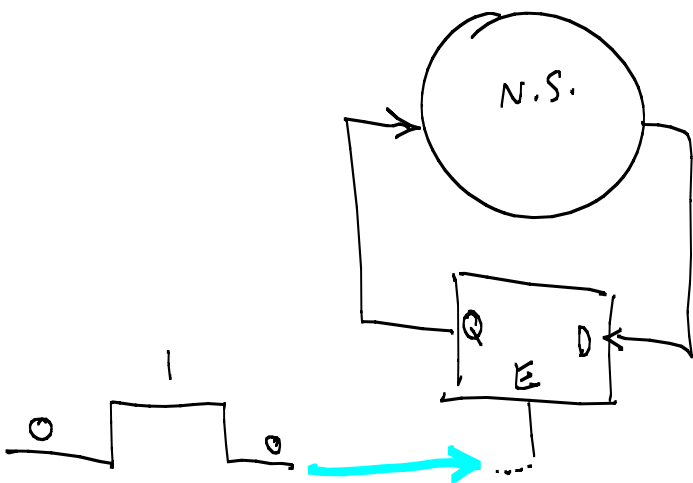


Transparent during this time, enough time to cause state change?

 
Make sure system never has an open feedback path.



# D-FF

 


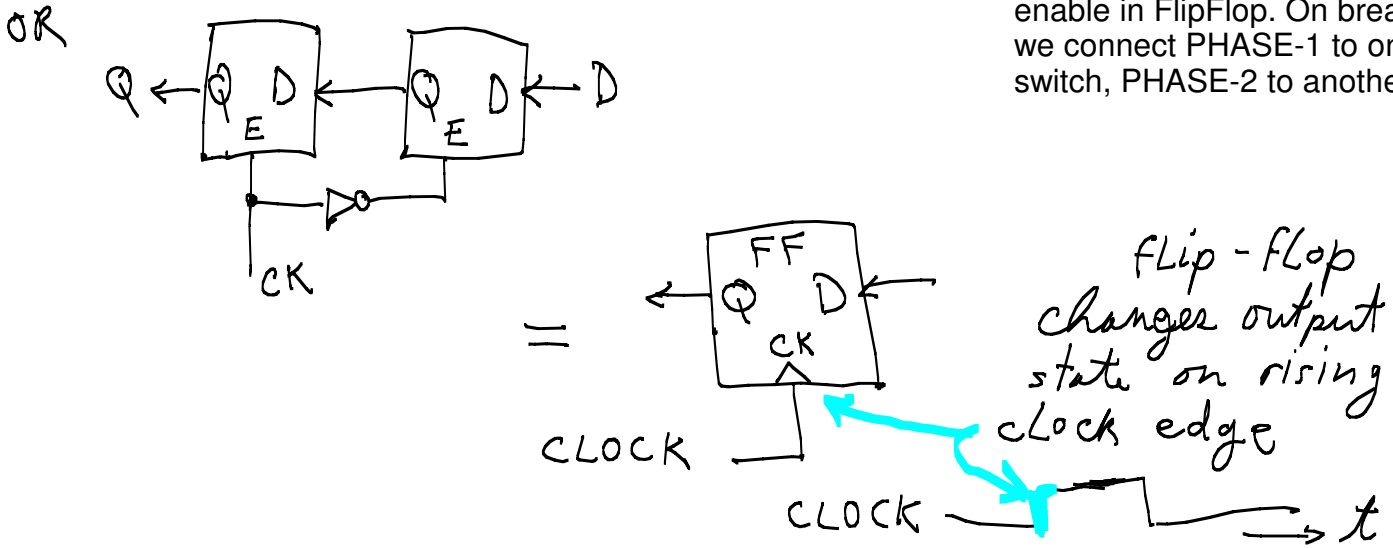Separate signals for each latch's enable in FlipFlop. On breadboard we connect PHASE-1 to one data switch, PHASE-2 to another.



 
## D-FF, Pos. edge triggered w/enable

We often want to control whether or not the FF will be written into when the clock pulse arrives: add an "enable" input. When enable is 0, the current state is written back into the FF. Otherwise, D is written.




If there is no feedback path from Q to D, we do not need a flip-flop, we can use a write-enable latch instead. Datapaths sometimes can use latches.

# Serial Parity, final implementation

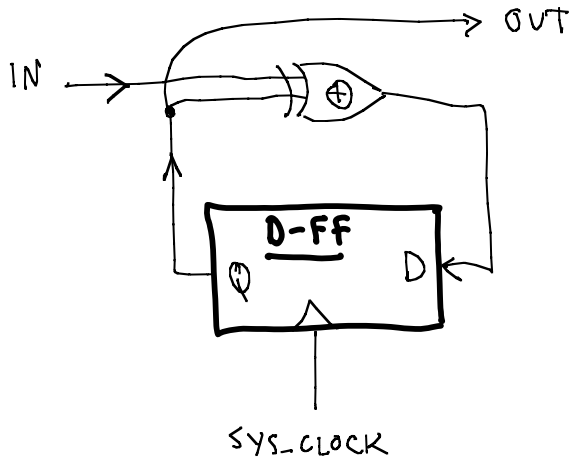

This is a FSM with non-trivial control state and next-state function, but a trivial datapath.

 Flipflop can be 2-phase clocked, in which case the "sys\_clock" signal consists of two wires.



FSM

STATE ENCODING	
EVEN	Q = 0
ODD	Q = 1

next-state

$$D = IN \oplus Q$$

output

$$OUT = Q$$

# FSM implementation, example | ADD-2, 2 serial inputs | reg. |

$$\begin{array}{r}
 c_4 \quad c_3 \quad c_2 \quad c_1 \quad c_0 \\
 X_3 \quad X_2 \quad X_1 \quad X_0 \\
 + Y_3 \quad Y_2 \quad Y_1 \quad Y_0 \\
 \hline
 S_4 \quad S_3 \quad S_2 \quad S_1 \quad S_0
 \end{array}$$

$$\begin{array}{r}
 \dots X_3 \quad X_2 \quad X_1 \quad X_0 \rightarrow X_{in} \\
 \dots Y_3 \quad Y_2 \quad Y_1 \quad Y_0 \rightarrow Y_{in} \\
 \text{Time} \leftarrow
 \end{array}$$

$$S_{out} \rightarrow \dots S_2 S_1 S_0$$

## FSM



state encoding:  $S_0 = 1$


next-state function:  $Q^+ = Q$

output function:  $out = Q$



OUT


## data path

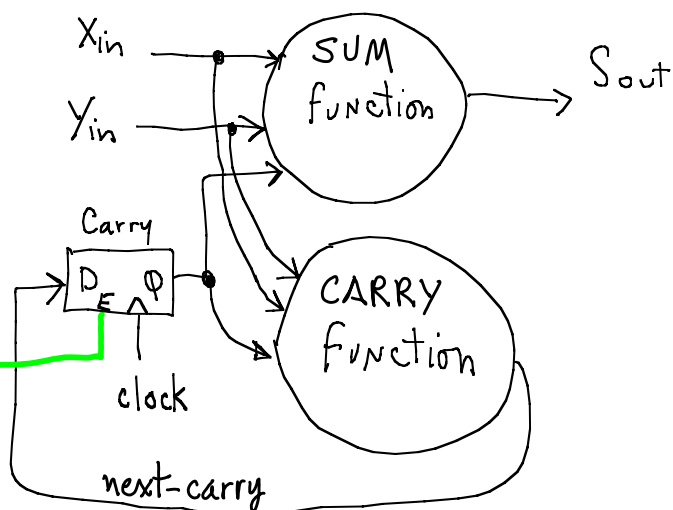


## Datapath functions, MUX

$$\begin{array}{r}
 c_i \\
 X_i \\
 + Y_i \\
 \hline
 c_{i+1} \quad S_i
 \end{array}$$

$c_i$	$Y_i$	$X_i$	$S_i$
$c_i = 0$	0	0	0
	0	0	1
	0	1	0
	0	1	1
$c_i = 1$	1	0	0
	1	0	1
	1	1	0
	1	1	1

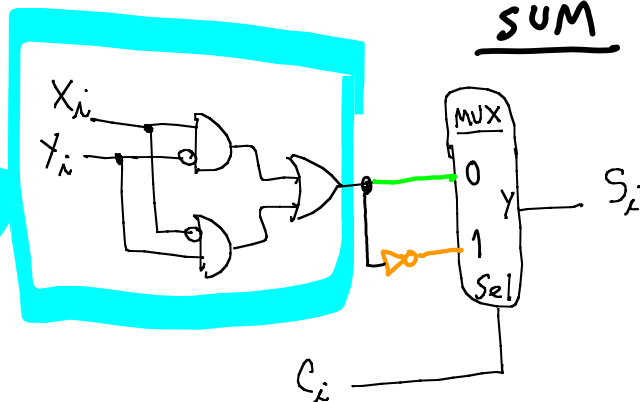


$c_i$	$Y_i$	$X_i$	$c_{i+1}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 



## MAJORITY

Select one of two inputs

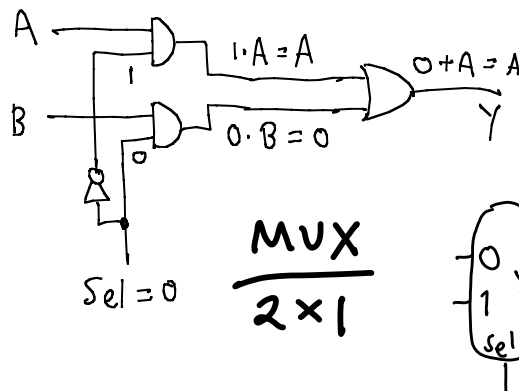

# Full Adder


## FA

 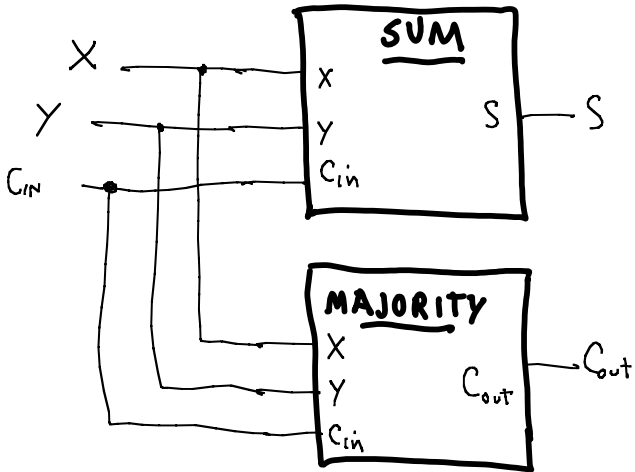

## Add-2, final implementation

This FSM has a non-trivial datapath consisting of datapath "state" registers and data processing "next-state" functions. But the control FSM is trivial.

## data path

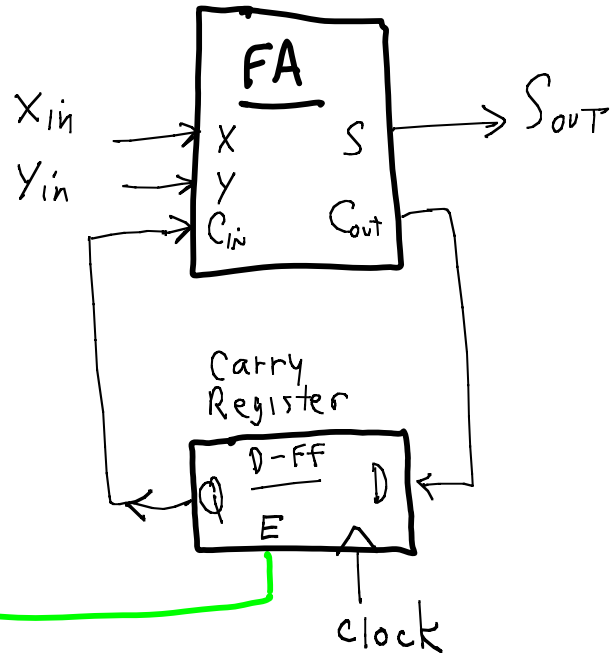


## FSM control

1




# FSM, Add-1 implementation

 


$$\begin{array}{r}
 C_2 C_1 C_0 \\
 X = X_2 X_1 X_0 \\
 + Y = Y_2 Y_1 Y_0 \\
 \hline
 S = \dots S_2 S_1 S_0
 \end{array}$$

And Now, a FSM with a non-trivial controller and non-trivial datapath.

## FSM control


 


## data path

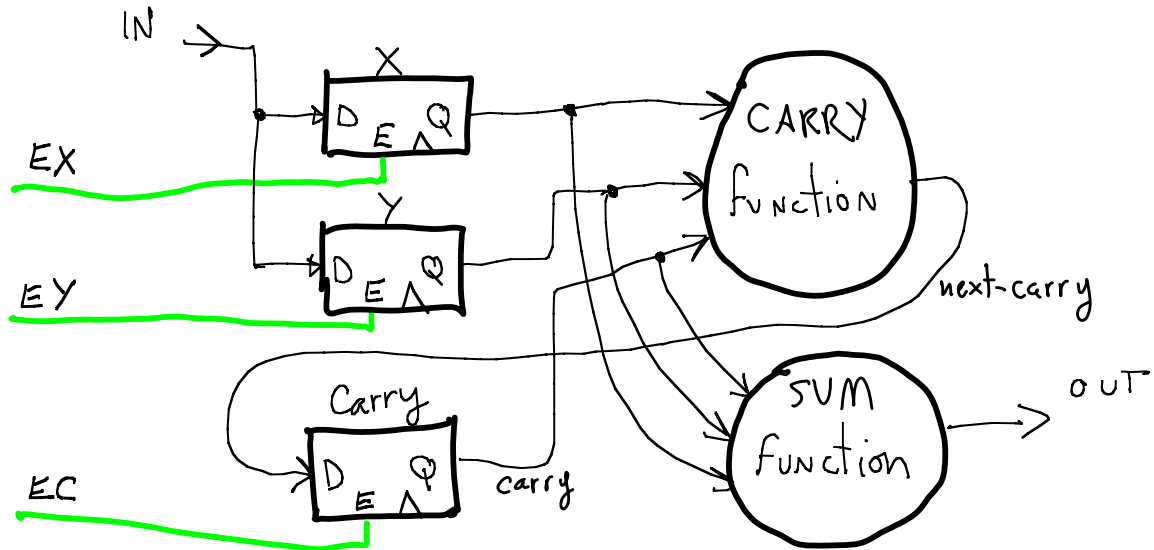

$\textcircled{x}$  means  $x=1$ , all others = 0

  
When is output valid? When should inputs be valid?



Function outputs are not valid until all inputs are available (valid).

X does not become valid until clock tick that ends state getX.

 
Output is only valid every 3rd clock period.





# Simplified FSM and datapath

If we can depend on the input to be stable, we can eliminate the Y data register: just use the data input when it is valid for Y. Eliminates one control state.


## data path

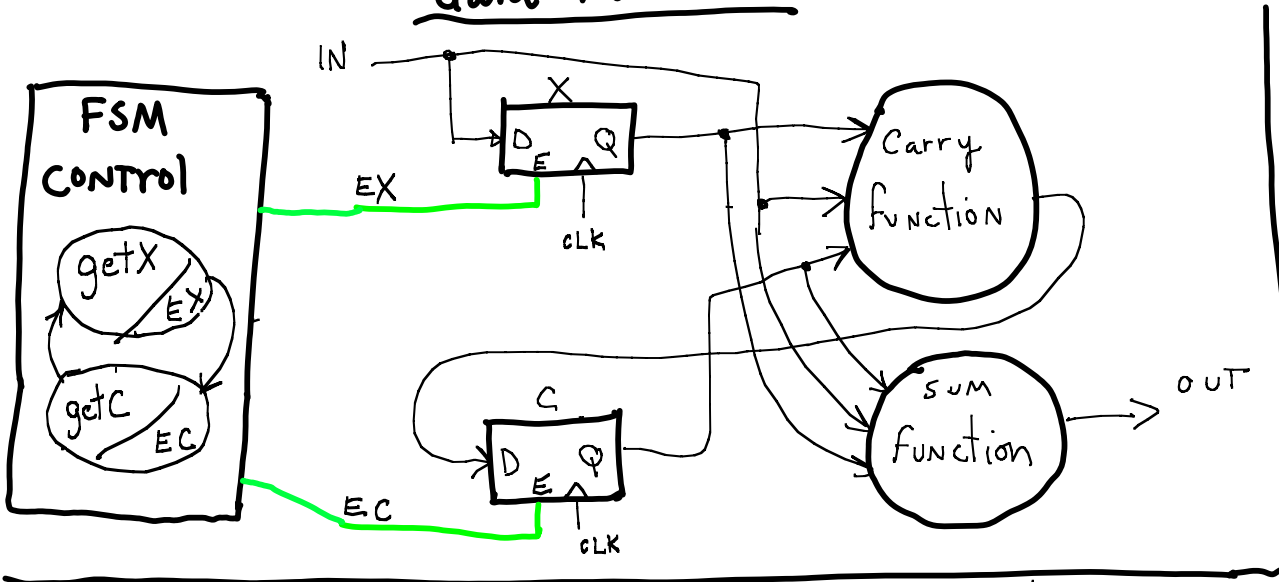


STATE	ENCODING
getX	0
getC	1

  

## FSM controller

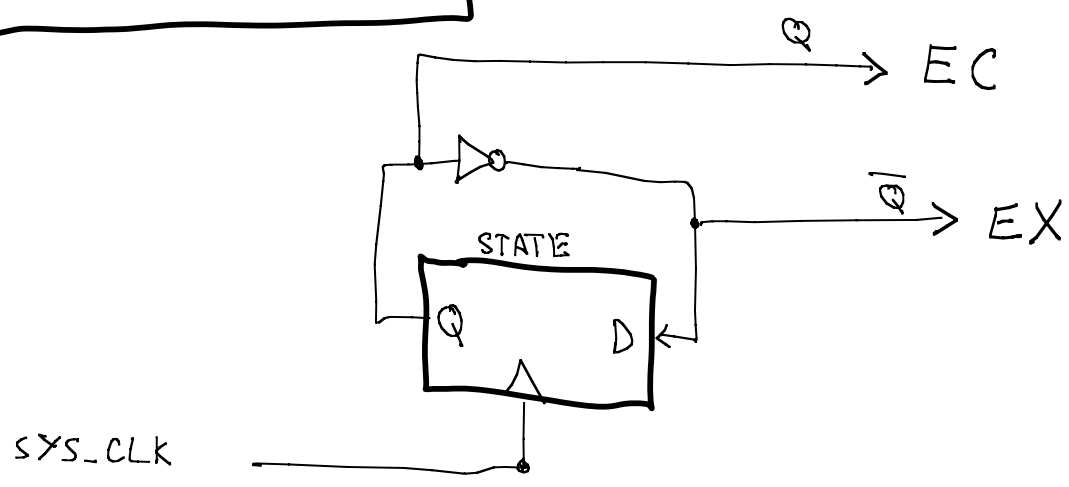



## Sum function

 

# Carry function, w/ Karnaugh map + algebra

X.Q	IN	C.Q	C.D (majority)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 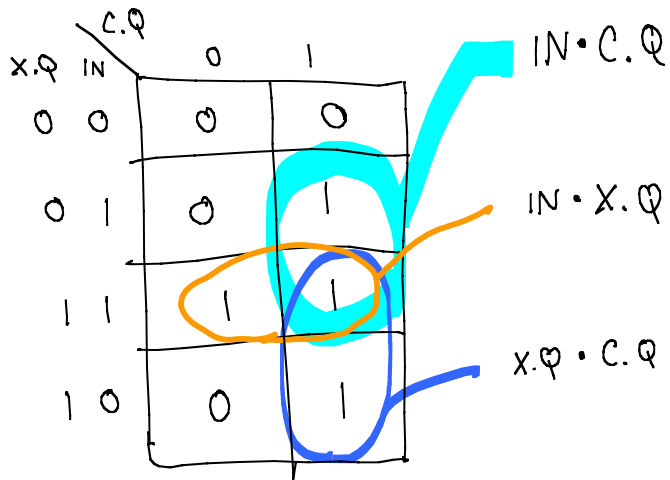(minterms)  
 $\downarrow$   
 8 AND  
 +  
 3 OR





$$C.D = IN \cdot C.Q + IN \cdot X.Q + X.Q \cdot C.Q$$

$$= IN \cdot (C.Q + X.Q) + X.Q \cdot C.Q$$

[eliminates 3-input OR]

$\Rightarrow$  (Convert to NAND/NOR)  
 $\bar{Q}$  is available.



## Full Adder (FA)

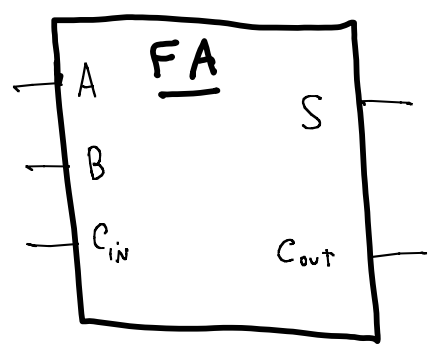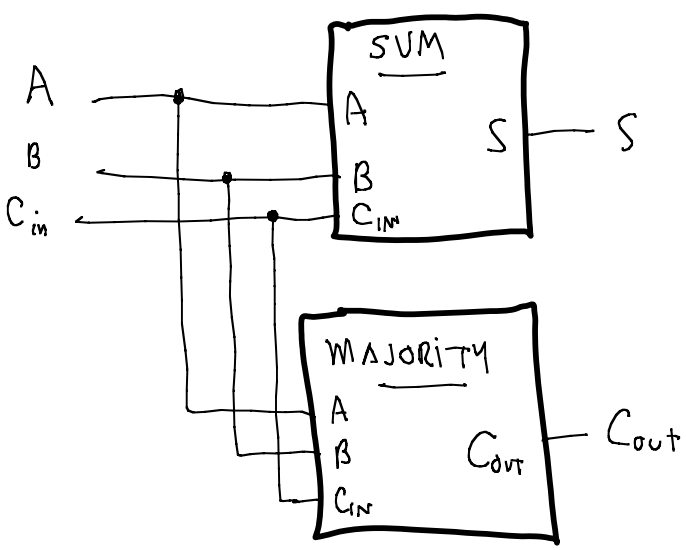


SMALLER FA circuit?

Can you find terms shared between MAJORITY and SUM?

# PLA

  

## 2x4 DEC

 


Programmable Logic Array consists of two parts:

PLA, part 1.

A decoder, which can be thought of in two ways:

 - a) a device that activates exactly on output depending on the code sent in.
- b) a device that simultaneously generates all minterms for its input.



AND-OR  
ckt. for any  $f, g$


PLA, Part 2.

A means of OR'ing minterms to produce function outputs.

Several ORs can share the same minterms: we can economically produce multiple functions at once.

The connections to minterm lines can be "blown" to disconnect them: this selects which minterms are included in the function.


# MUX

 



"gating"

Control = 0 :  $Y = 0$   
 Control = 1 :  $Y = \text{data}$

control	data	Y
0	0	0
0	1	0
1	0	0
1	1	1


 


A	B	f
0	0	0
0	1	0
1	0	0
1	1	1

  

4 words,  
 1-bit word  
 =  
 4x1 ROM

Logic  
 =  
 ROM

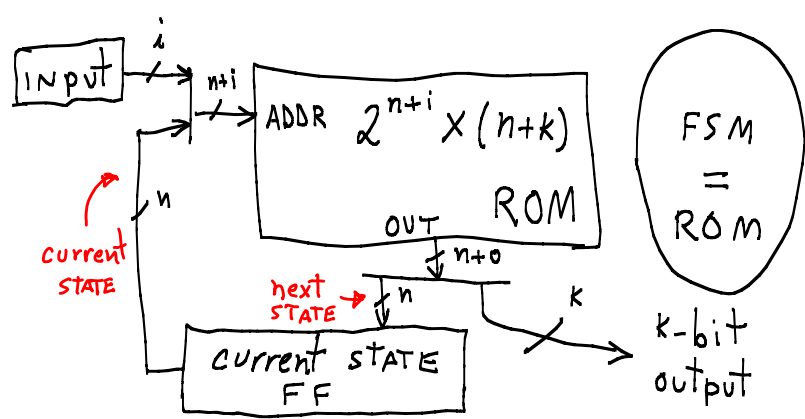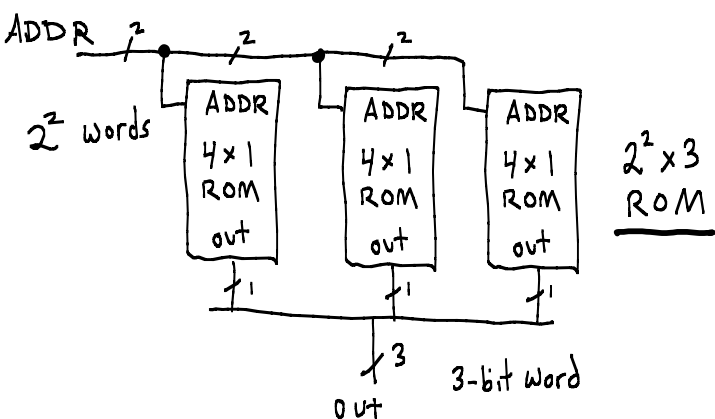

FSM in ROM ( n-bit state, i-bit input, k-bit FSM output )

(STATE, INPUT) is ROM address  
 n bits + i bits ==>  $2^{(n+i)}$  ROM locations

(NEXT-STATE, FSM-OUTPUT) is ROM output  
 n bits + k bits ==> (n+k) bits per location

==>  $2^{(n+i)}$  location by (n+k)-bit word ROM


ANY FSM (Mealy or Moore) can be built as a ROM

NOTE: A Moore machine's output depends only on state  
 ==> use n-bit addresses, one ROM location per state.


BUT, next-state depends on current-state+input. Encode part of next-state function in ROM word as NS-CODE, and use external logic to calculate next-state function:  $next-state = f( INPUT, NS-CODE )$ . This is what is done in the LC3's micro-coded controller.

Every possible FSM can be built as a ROM.

 ROM is very large since there is a word for every possible {state, input} combination.



address		ROM data word (ROW)	
STATE	INPUT	next-state	output
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	1

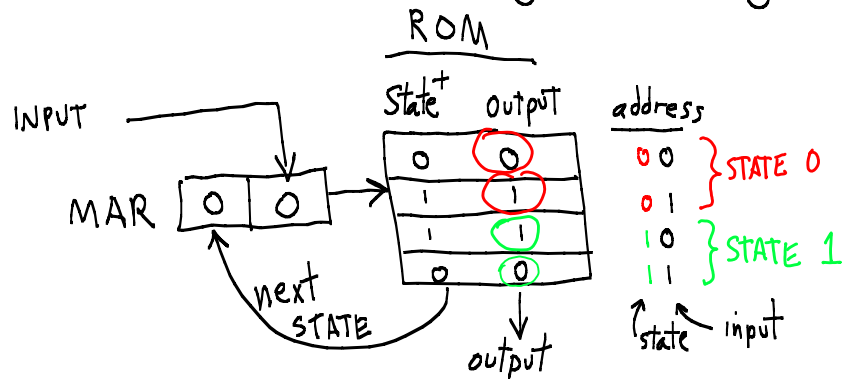

We can enumerate all ROMs (and consequently all TMs/digital-computers):

Concatenate ROM content from all words:

address	content
00	00
01	11
10	11
11	00

==> 01111000

at clock tick:

- { current state, current input } captured
- output changes to match captured state/input

-- Every state row has same output  
 ==> Moore Machine

-- Rows for state S have differing outputs  
 ==> Mealy Machine.

List all n = i = k = 1 machines:  
 FSM-0, FSM-1, ..., FSM-256

List all n = i = k = 2 machines:  
 FSM-257, FSM-258, ...

and so on.

