




Implement FSM controller

Implement uSeq's FSM's
 --- Next-state function
 --- Output function

We know:
 Any function can be implemented in AND-OR


I) implement logic w/ROM

| A | B | C | $f(A,B,C)$ |
|-----|-----|-----|------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| ... | ... | ... | ... |

   


k -bit inputs and n output functions (or n -bit word, or $i+j$ bit words, or...)

FSM functions in ROM (Moore Machine)

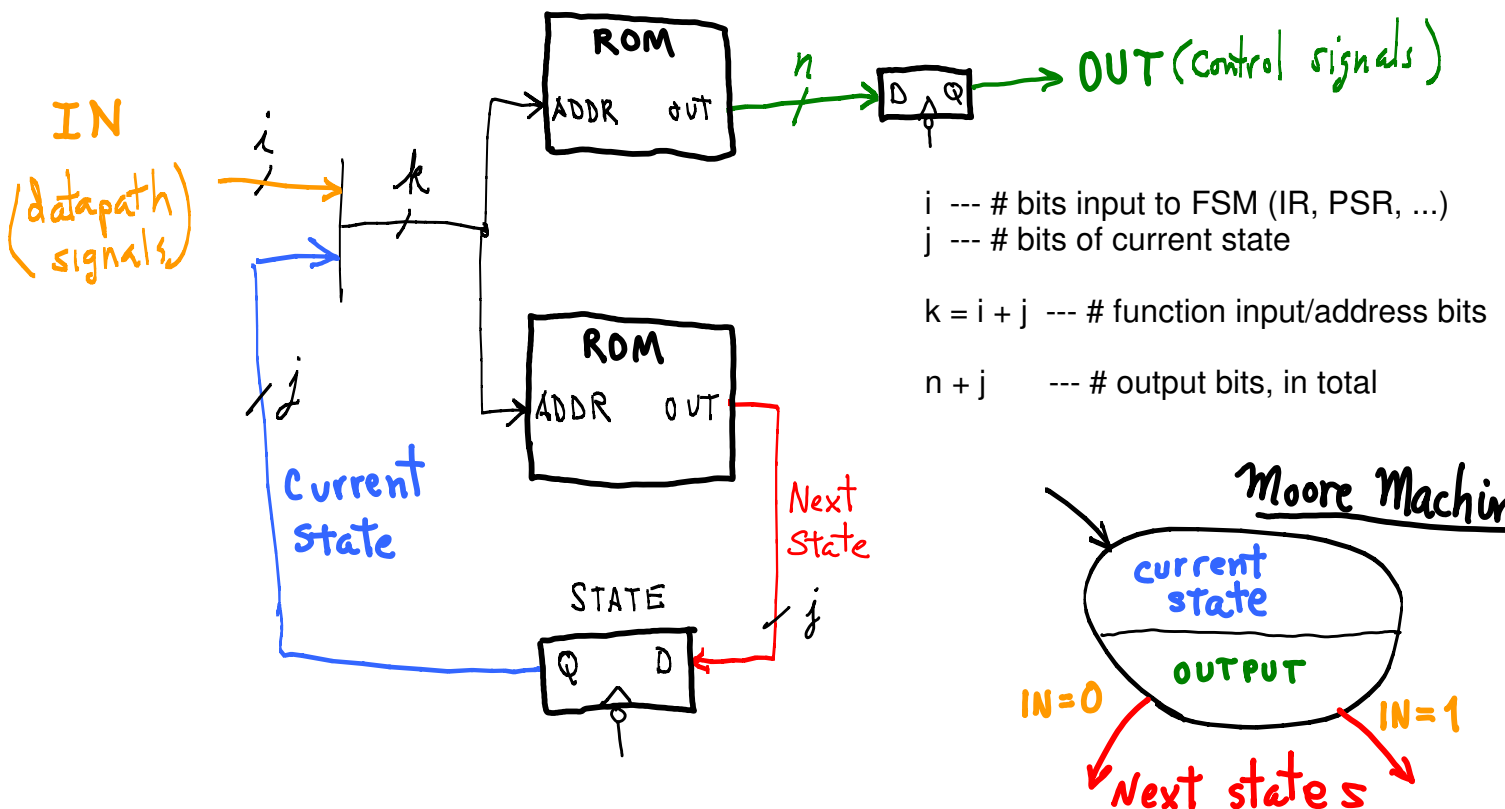

Combine as 1 ROM

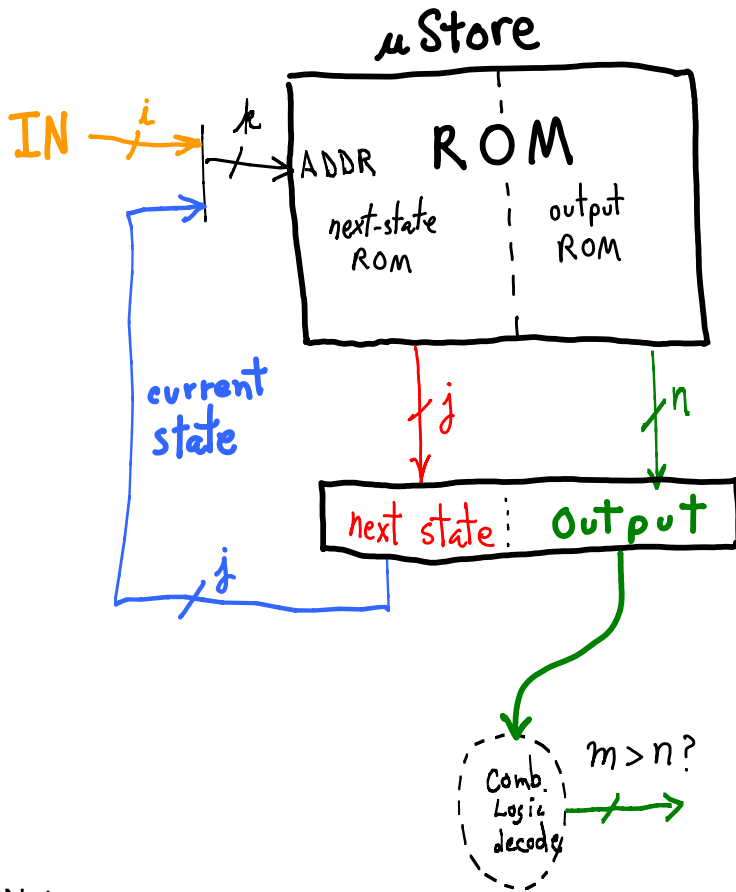

Note:
 Could use control "codewords".
 Decode to actual control signals.

OK, if not every control bit combo is used. Saves columns of ROM.

Wasted Space?

IN + current-state == (i+j)-bit address
 --- Many addresses ==> One LC3 state

LC3:

j = 6 ($2^6 = 64$ possible states, 59 used)
 i = 9 (bits input: IR, PSR, ...)

ONE LC3 state ==> ($2^9 = 512$) ROM rows.
 E.g., state-0, **BR**:



| state | IN | ROM address |
|--------|-----------|-------------|
| 000000 | 000000000 | x0000 |
| 000000 | 000000001 | x0001 |
| 000000 | 000000010 | x0002 |
| ... | ... | ... |
| 000000 | 111111111 | x01FF |

--- Uses 1-bit for next state (BEN).
 --- All other inputs ignored.

Next-state is either 18 or 22.
 No non-zero outputs.

--- 256 ROM rows contain
 010010 00000000...000 (6+40 bits)
 --- 256 ROM rows contain
 010100 00000000...000 (6+40 bits)


FSM in ROM, e.g.

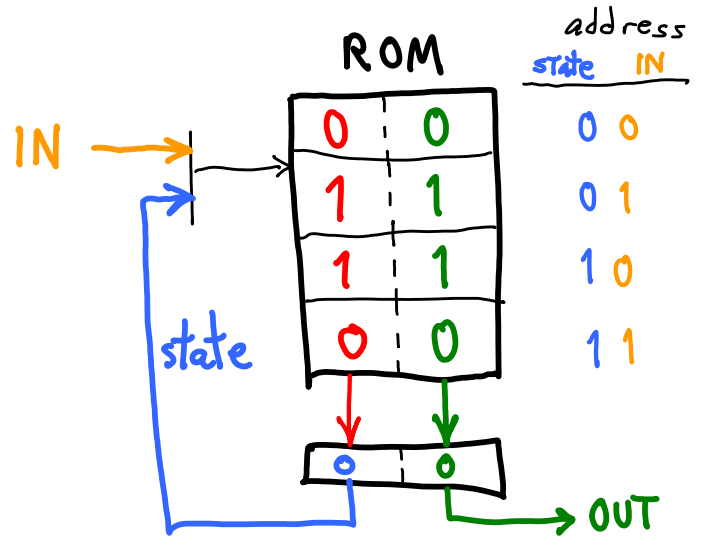 

Aside: If the next state is 0, then next output is 0 (rows 00 and 11). What if that wasn't so? Would this be a Mealy Machine?

LC3 micro-Sequencer, μ Seq

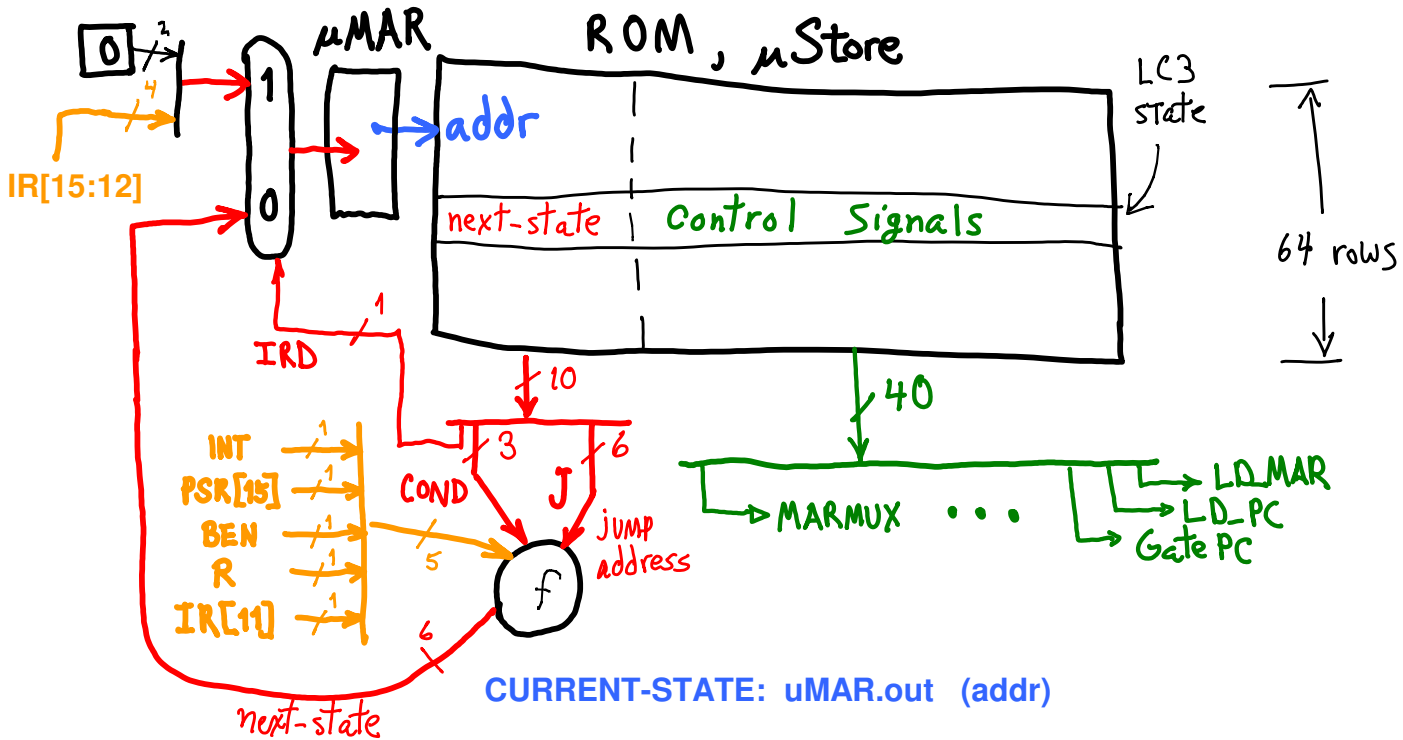59 states. We need 6 bits to designate state. $2^6 = 64$.



CURRENT-STATE: μ MAR.out (addr)

OUTPUT: All control signals, selected by addr.

NEXT-STATE: Not so simple! Determined by:

--- **IR.opcode**, if **IRD** == 1

μ MAR \leftarrow { 00, IR[15:12] } (e.g., 001001 for NOT instruction)
 (**IRD** is only set for state-32)

--- Otherwise

COND bits are mixed with **INT, PSR[15], BEN, R, IR[11]**
JUMP address is modified accordingly.

Note:



An instruction's 1st state in its execution control path is,

00xxxx,

where xxxx = IR[15:12] is its opcode.



No other states have 00 as a prefix.

e.g.

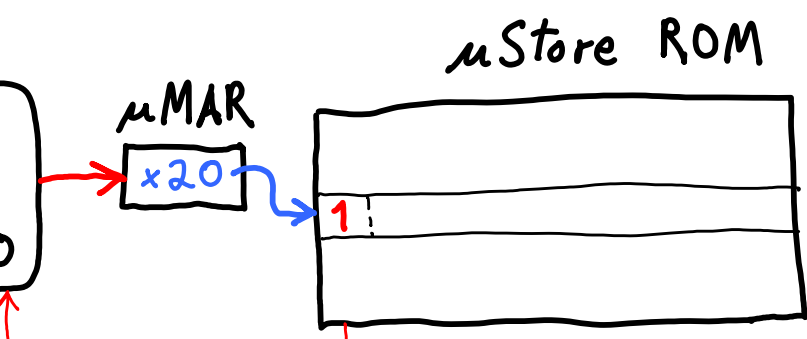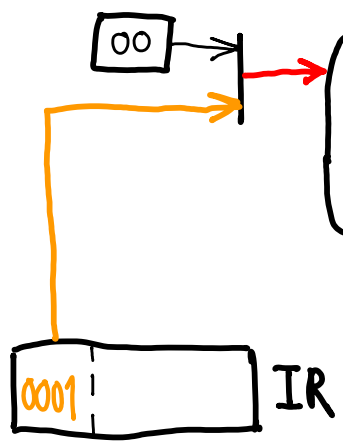


address state
x20 (32, Decode)

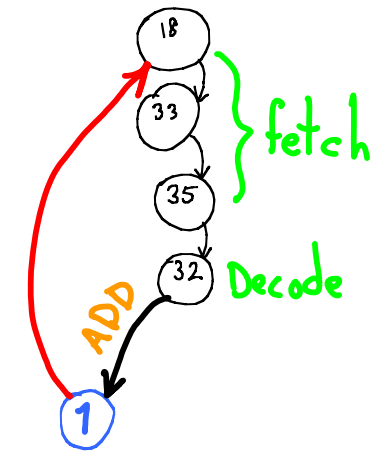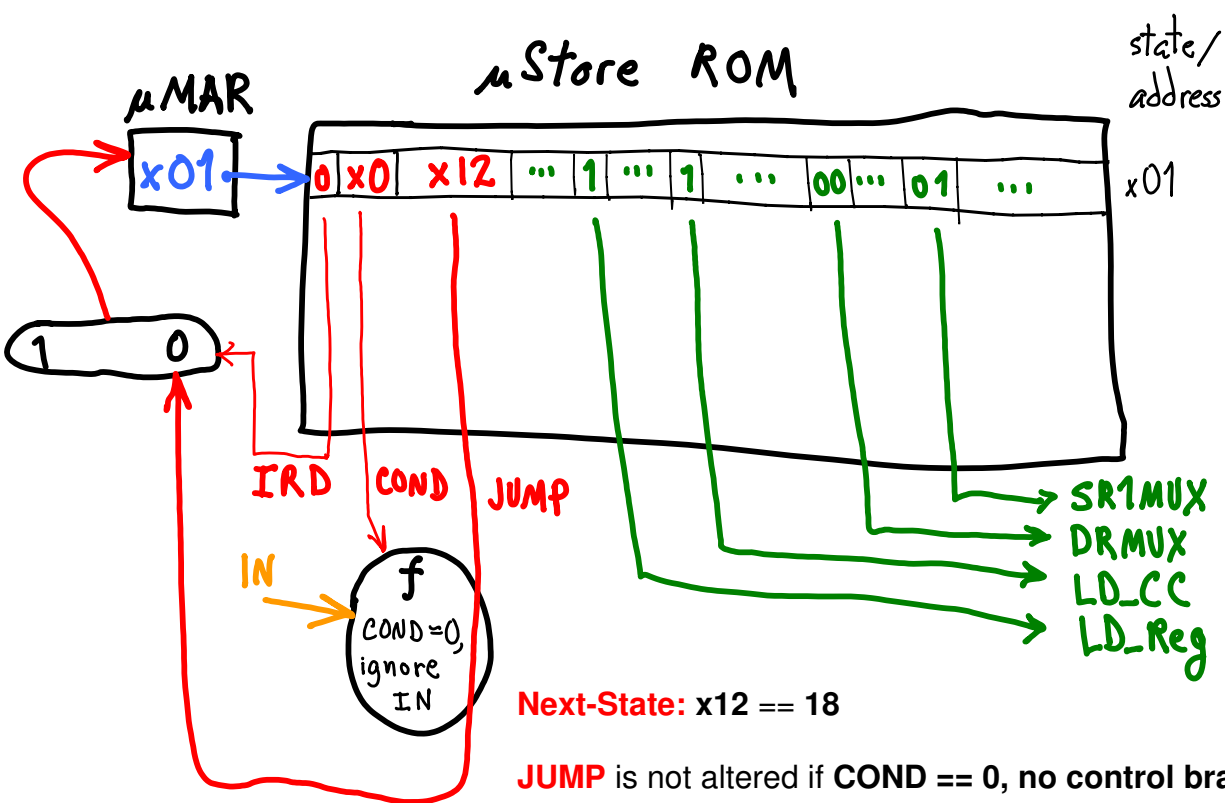Current-State == x20 == 32 (DECODE)
IRD == 1
IR[15:12] == 0001 (ADD)
Next-State == 000001 (state 1)



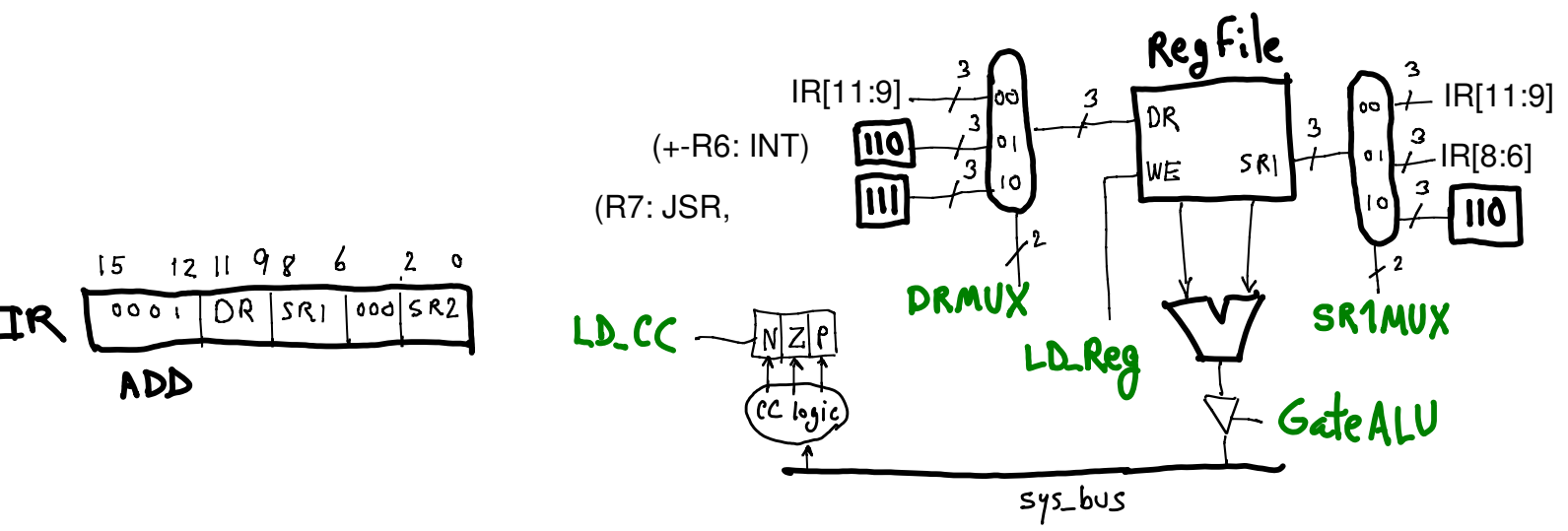Next-State: x12 == 18
JUMP is not altered if COND == 0, no control branching.





Control Branching in LC3

But first, an easier method.



Let's have 2-way branching (except state-32).

Fields for both targets.


1-bit of input determines next state.

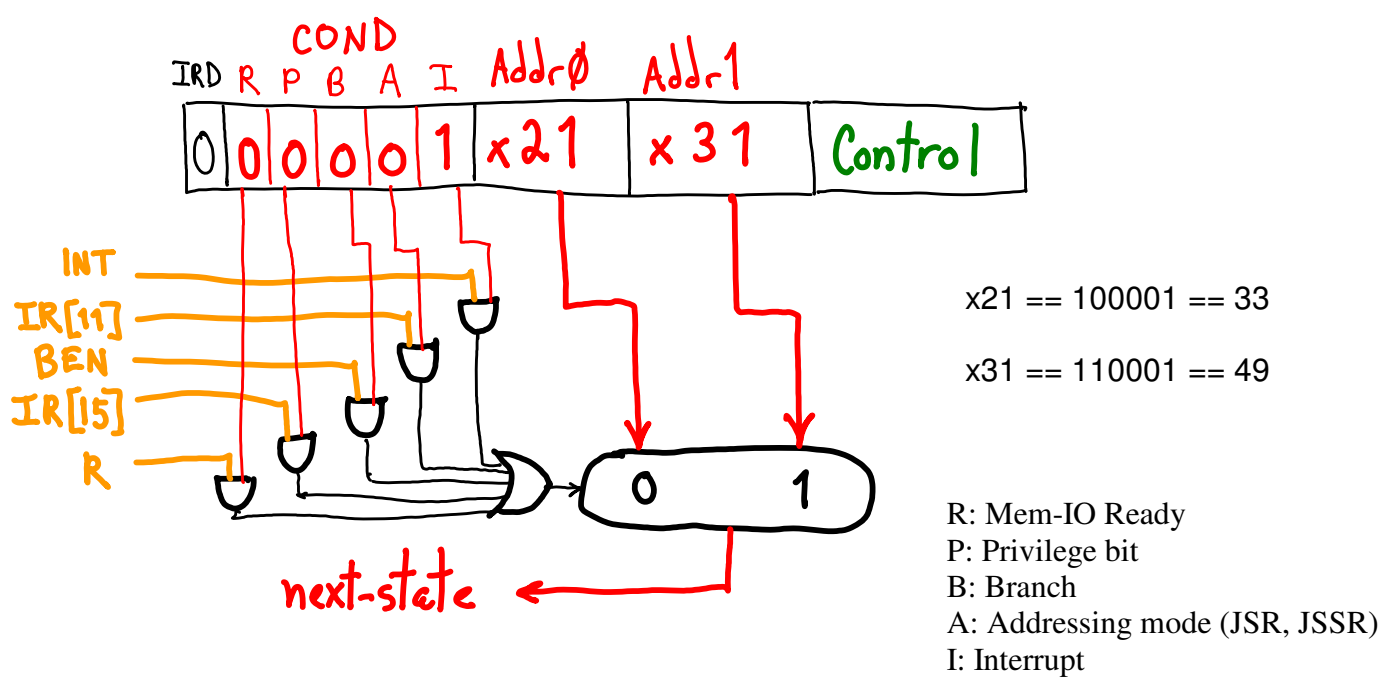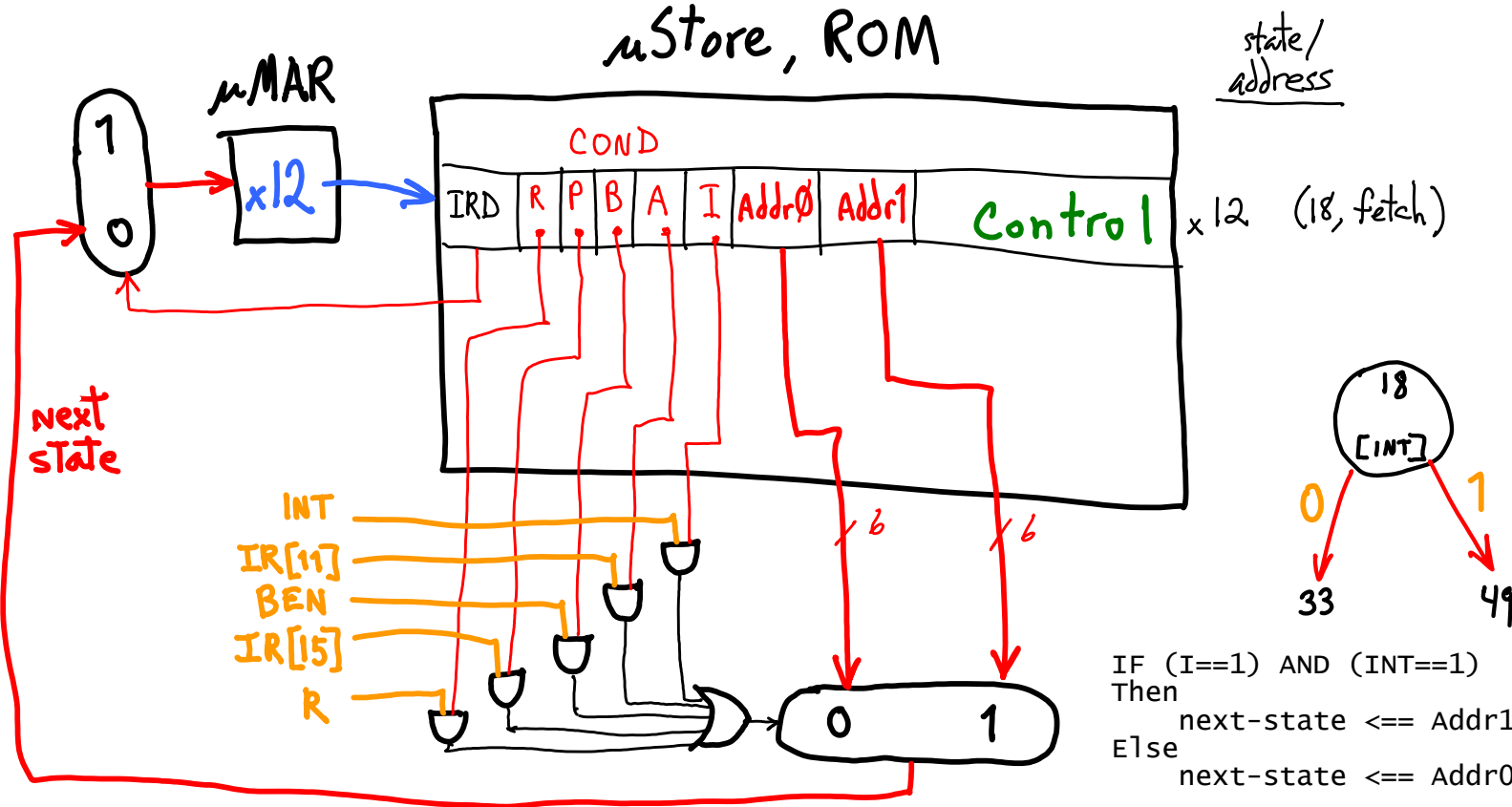

Actually, in P&P

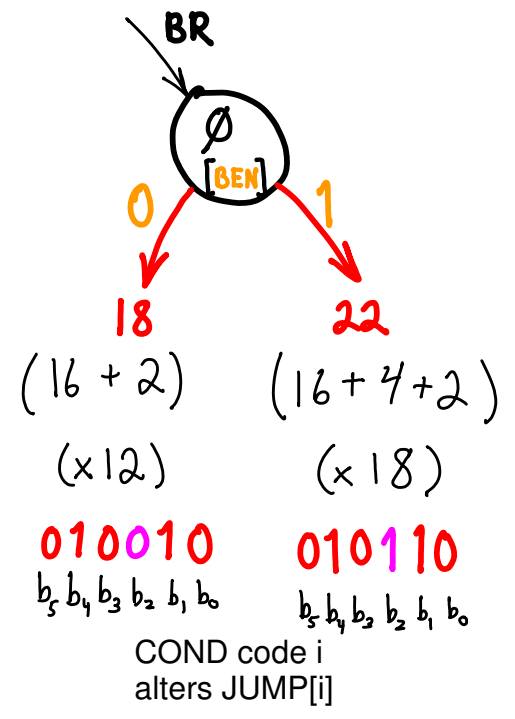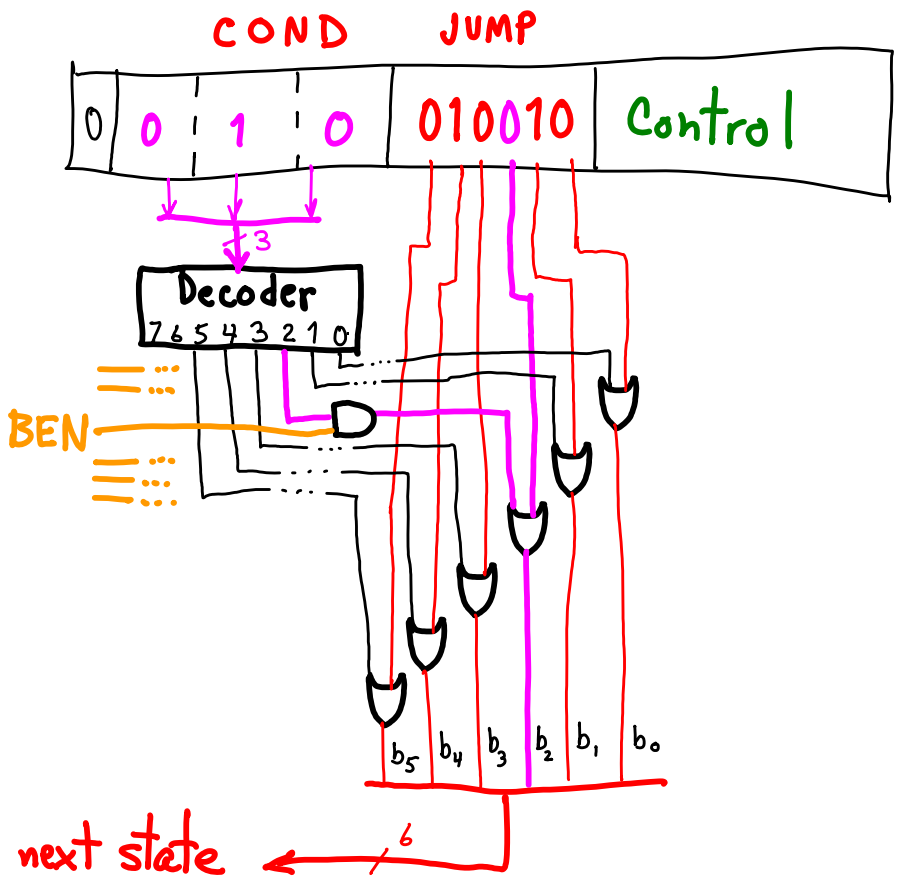

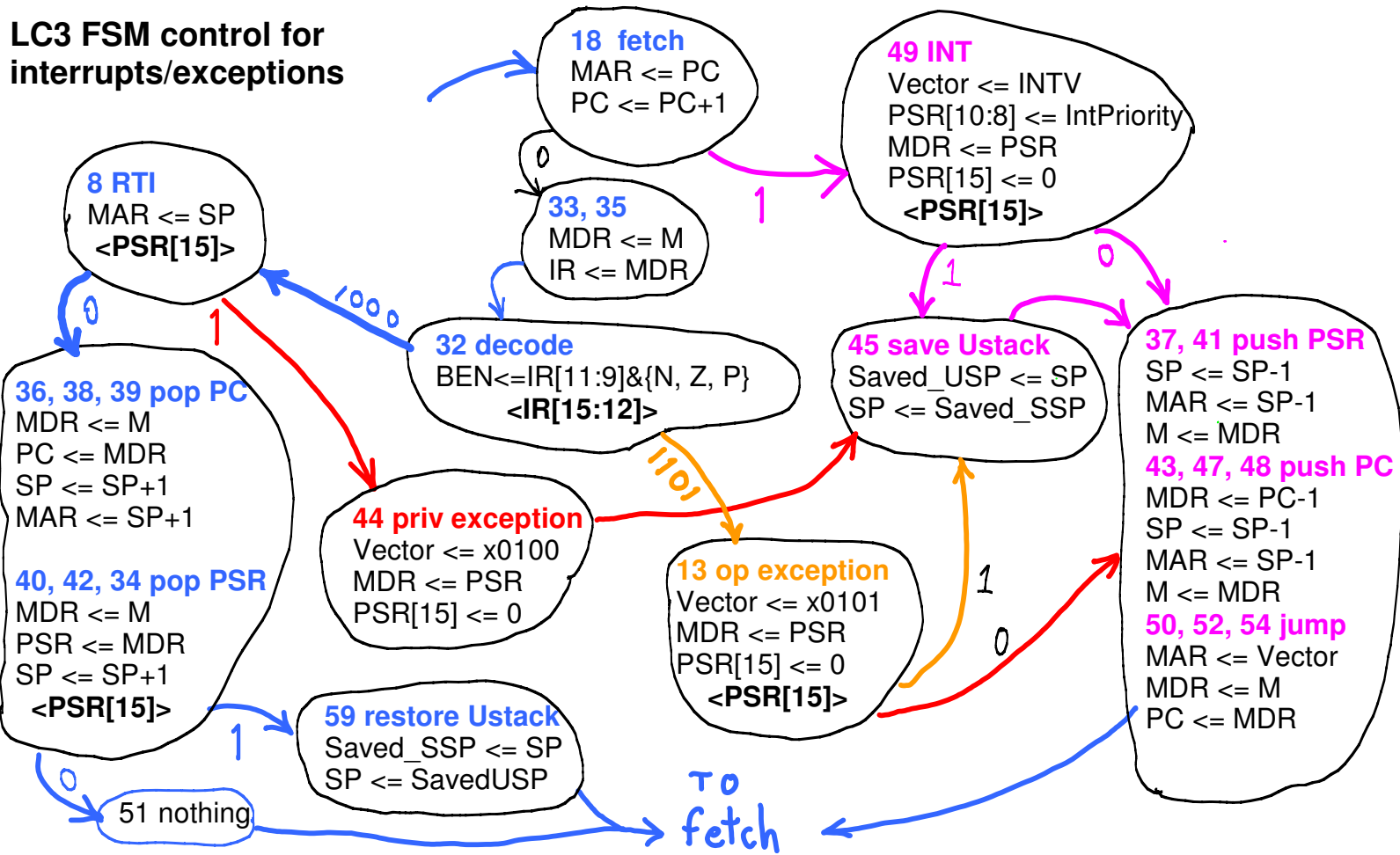LC3 FSM control for interrupts/exceptions



Hardware Additions (privilege + memory protection). (low-cost additions)

1. TRAP switches to supervisor mode.
2. Return switches back to user mode.

Have TRAP act like exception? Use RTI for return?

1.A TRAP's state-15 acts like state-13 (opcode exception), except for **jump**:

```

Vector <== sys_bus <== MARMUX <== ZEXT <== { x00, IR[7:0] }
MDR <= PSR
PSR[15] <= 0
    
```

1.B Branch on PSR[15]: same as state-13's:
to 37 or 45 (into interrupt chain). [Unused states: 15, 28, 30.]


1.C mux Vector's input:

select = 0: the usual input
select = 1: **sys_bus**

Control logic?

Don't redesign uStore to have more columns?

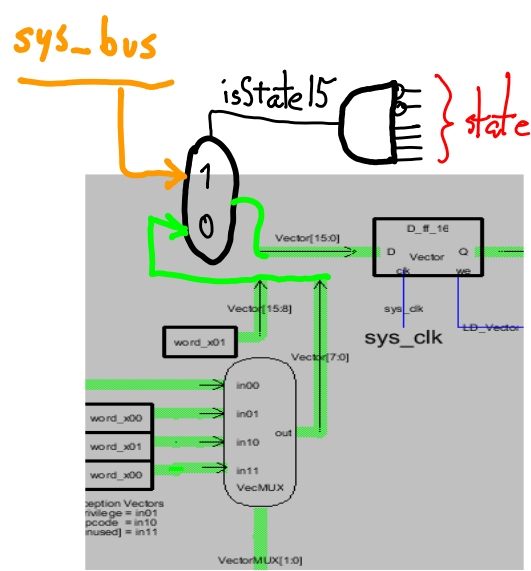- a. Add uSeq output "state" (controller's current state).
- b. **select == AND(x0F, state)** [6-bit AND: select == 1 if state-15]
- c. caveat: a problem for pipelining?



2. **RTI** returns to calling code (restores privileges).

MORE ADDITIONS (low cost?)

Disable INTERRUPTS?

- A. handler needs time to set up its state before allowing a new interrupt.
- B. handler needs to disable multiple interrupts on same device.

We have:

- Interrupt: PSR.Priority $\leq 2b'111$
- Priority Comparator: (IntPriority > PSR.Priority)
- Effect: All interrupts are disabled initially on interrupt.

We can:

- mask interrupts: device-status-register[14] $\leq 1b'0$
- LDI R1, KBSR
- LD R2, BIT_14_MASK
- AND R1, R1, R2 ;--- There is also an "OR" macro, see src/lc3pre.
- STI R1, KBSR
- ...
- KBSR: .FILL xFE00
- BIT_14_MASK: .FILL xBFFF ;--- (1011 1111 1111 1111)

Oh, ok, we've already handled this.

Memory Protection?

- Privileged status is nice.
- Useless unless memory is protected.

Need:

- Hardware to detect address + protection bits
- Exception for access violation


Add:

- MPR, Memory Protection Register?

16-bit addresses, 16-bits in MPR,

- divide into 16 "pages", one bit in MPR per page: $(2^{16})/(2^4) = (2^{12}) = 4k$ words per page.
- 0: super only, 1: user or super.
- Large-end 4 bits of address determines "page number"

| | |
|------------------|-----------------|
| 0000: OS space | (x0000 - x0FFF) |
| 0001: OS space | (x1000 - x1FFF) |
| ... | |
| 0011: User space | (x3000 - x3FFF) |
| ... | |
| 1110: User space | (xE000 - xEFFF) |
| 1111: OS space | (xF000 - xFFFF) |

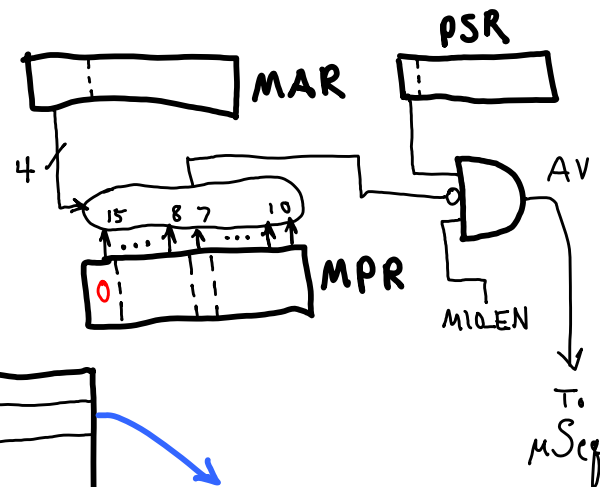

- R/W protection: More than one bit per page?
- Multiple users: Owner bits?

Mapping Addresses?

- virtual MAR
- physical MAR

==> runtime independence

