
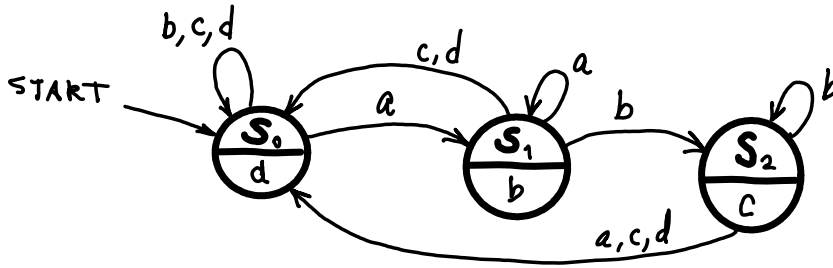


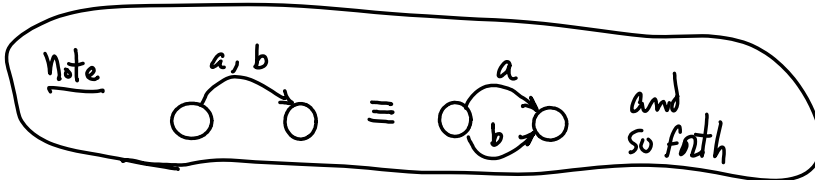Implement a FSM for the Moore machine described by the state-transition diagram below. Use 1-bit D flipflops and 2-input Boolean logic gates {AND, OR, NOT}.



a Moore machine:
output is only dependent on state




Preliminary steps:

Q. Define a Boolean encoding of the input symbol set {a, b, c, d}; that is, show how to implement a 4-symbol set using 2-bits. Also, define a binary encoding of the machine's states. Complete the tables at right.

symbol	code b ₁ b ₀
a	0 0
b	0 1
c	1 0
d	1 1

state	code Q ₁ Q ₀
S ₀	0 0
S ₁	0 1
S ₂	1 0

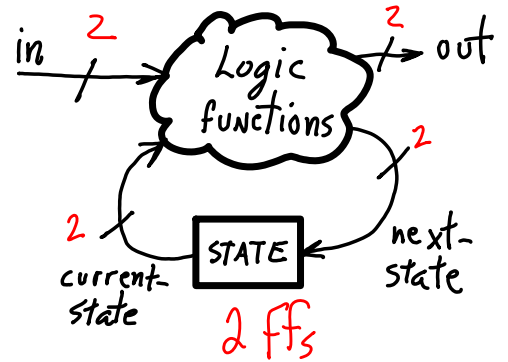Q. Complete the general FSM implementation diagram at right. Specify the number of wires (bits) on each signal paths, "in", "out", "current-state", and "next-state". Specify the number of state elements (1-bit D FFs).



Q. Specify the next-state and output logic functions: complete the tables below.


in b, b ₀	current-state Q ₁ Q ₀	next-state Q ₁ ⁺ Q ₀ ⁺
0 0	0 0	0 1 ← m ₀
0 1	0 0	0 0
1 0	0 0	0 0
1 1	0 0	0 0
0 0	0 1	0 1 ← m ₁
0 1	0 1	1 0
X X	1 1	X X

Don't care

in b, b ₀	current-state Q ₁ Q ₀	next-state Q ₁ ⁺ Q ₀ ⁺
1 0	0 1	0 0
1 1	0 1	0 0
0 0	1 0	0 0
0 1	1 0	1 0 ← m ₂
1 0	1 0	0 0
1 1	1 0	0 0
X X	1 1	X X

current-state Q ₁ Q ₀	out b, b ₀
S ₀ 0 0	1 1 ← Q ₁ , Q ₀
S ₁ 0 1	0 1 ← Q ₁ , Q ₀
S ₂ 1 0	1 0
X 1 1	X X ← Don't care

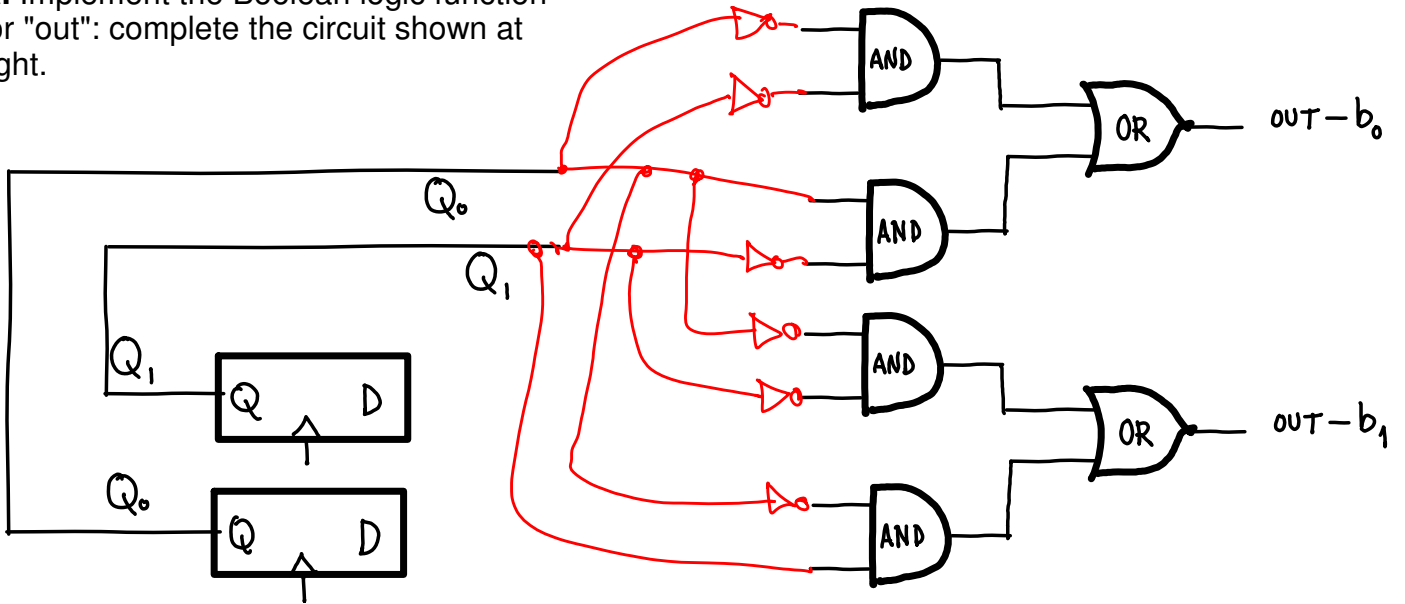Q. Implement the Boolean logic function for "out": complete the circuit shown at right.



Q. Implement the Boolean logic function for "next-state": complete the circuit shown below.

