

# Verilog

## Electric Window

## shell commandline





## shell

Tools. Simulation.  
Write Verilog Deck

`$ iverilog bar.v`

`$ vvp q.out > bar.out`

Electric

    

lib / foo.jelib

run / bar.v

run / a.out

run / bar.out

# Verilog Code Structure from Electric Cells




T.jelib

L.jelib

cell "test{sch}"

cell "foo{sch}"

cell "bar{sch}"

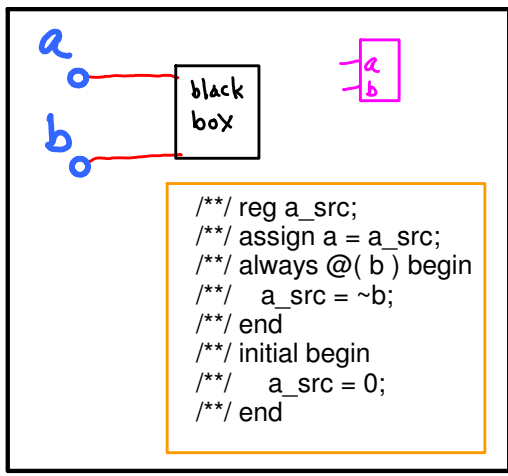  

- = verilog code box
- o = Export
- = wire
- = icon
- = instance

```

module test();
  wire res;
  reg sig;

  L__foo foo0( res, sig );

  initial begin
    sig = 0;
    #100 $finish;
  end

  always begin
    #1 sig = ~sig;
  end
end module
    
```

```

module L_foo( x, y);
  output x; wire x;
  input y; wire y;
  wire net1;

  L__bar bar0( x, net1);
  L__bar bar1( net1, y);
endmodule;
    
```


```

module L_bar( a, b);
  output a; wire a;
  input b; wire b;

  /**/ reg a_src;
  /**/ assign a = a_src;
  /**/ always @( b ) begin
  /**/   a_src = ~b;
  /**/ end
  /**/ initial begin
  /**/   a_src = 0;
  /**/ end
endmodule
    
```

Electric...WriteVerilogDeck saved as, "run/test.v"

Cell "add16 {sch}"

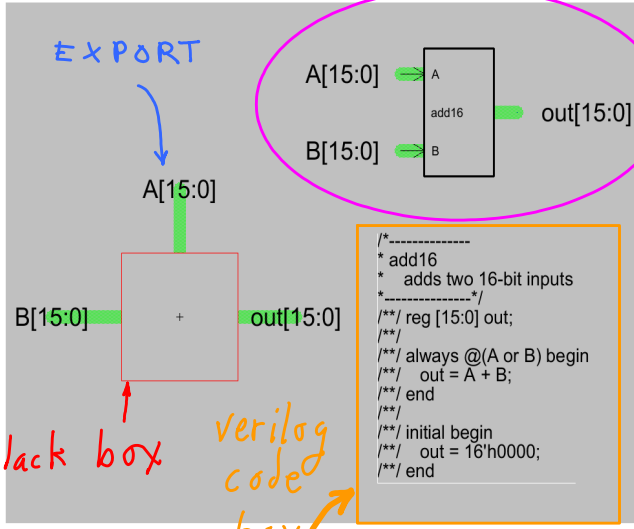

```

/*-----
 * add16
 * adds two 16-bit inputs
 *-----*/
/**/ reg [15:0] out;
/**/
/**/ always @(A or B) begin
/**/   out = A + B;
/**/ end
/**/
/**/ initial begin
/**/   out = 16'h0000;
/**/ end

```

icon "add16 {ic}"

Electric.  
Tools.  
Simulation.  
Write Verilog

/\* Verilog for cell 'parts:add16{sch}' from library 'parts'\*/

```

module add16(A, B, out);
input [15:0] A;
input [15:0] B;
output [15:0] out;

```

/\* user-specified Verilog code \*/  
/\*-----\*/

```

* add16
* adds two 16-bit inputs
*-----*/
/**/ reg [15:0] out;
/**/
/**/ always @(A or B) begin
/**/   out = A + B;
/**/ end
/**/
/**/ initial begin
/**/   out = 16'h0000;
/**/ end


```

endmodule /\* add16 \*/

Cell

"add16-test {sch}"

icon = instance of add16

 

```

/*-----
 * Drive adder inputs
 *-----*/
/**/ reg[15:0] Asrc;
/**/ reg[15:0] Bsrc;
/**/ assign A = Asrc;
/**/ assign B = Bsrc;
/**/ initial begin
/**/   #0 Asrc = 16'h0000;
/**/   #0 Bsrc = 16'h0000;
/**/   #7000 $finish;
/**/ end
/**/
/**/ always begin
/**/   #1 $display(" %d + %d = %d", Asrc, Bsrc, out);
/**/   #1 Bsrc = Bsrc + 7;
/**/   #1 $display(" %d + %d = %d", Asrc, Bsrc, out);
/**/   #1 Asrc = Asrc + 17;
/**/ end

```

```

module parts__add16(A, B, out);
input [15:0] A;
input [15:0] B;
output [15:0] out;

```

```

/* user-specified Verilog code */
/*-----*/
* add16
* adds two 16-bit inputs
*-----*/
/**/ reg [15:0] out;
...
/**/ end

```

endmodule /\* parts\_\_add16 \*/

```

module add16_test();

```

```

wire [15:0] A;
wire [15:0] B;
wire [15:0] out;

```

Top-level, no args

```

/* user-specified Verilog code */
/*-----*/
* Drive adder inputs
*-----*/
/**/ reg[15:0] Asrc;
...
/**/ end

```

```

parts__add16 ADDER(.A(A[15:0]), .B(B[15:0]), .out(out[15:0]));
endmodule /* add16_test */

```

BUS

instance of add16

Export BUS

# Structural vs. Behavioral

Structural  $\leftrightarrow$  wire, gates, devices: wire, reg, AND, or, ...

Behavioral  $\leftrightarrow$  if( ) then( ), while, wait, ..., case, ...

"Helper" Language

integer, ..., while, ...


## Gate-level

STRUCTURAL

via  
"primitives"

```
module foo ( y, x, b );
    input x, b;
    output y;
    wire y, x, a, b;

     and and_0( y, x, a );
    or or_0( a, b, x );
endmodule
```



OR via  
"continuous assignment"

```
module foo ( y, x, b );
    input x, b;
    output y;
    wire y, x, b;

    assign y = ( x & ( x | b ) );
endmodule
```

## Delays

at what simulation time does

- a become 0?
- b become 0?
- c become 0?

possible signal values

- x == don't know
- z == disconnected
- 0
- 1

```
module f();
    reg a, b, c;

    initial begin
        #1 a = 0;
        #1 b = 0;
        #1 c = 0;
        #1 $finish;
    end

    always @(a or b or c) begin
        $display("--- t=%0d ---", $time);
        $write("a=%b ", a);
        $write("b=%b ", b);
        $write("c=%b ", c);
        $write("\n");
    end
endmodule
```

at what time do these events occur?  
Are they ordered, i.e., blocking?

```
--- t=1 ---
a=0 b=x c=x
--- t=2 ---
a=0 b=0 c=x
--- t=3 ---
a=0 b=0 c=0
```

# Event Queue

All "initial" and "always" statements execute in parallel.


```

initial begin
  a = 0;
  * 1 a = ~a;
end
  
```

```

always @(a) begin
  c = ~a;
end
  
```

# event queue

 

T=0

initial begin

where? ← event

b = 1;

end

T=1

where?

initial begin

event \$display(..a)

end

Where does this event go in queue?

What is the value printed by \$display("a=%d", a)?

What timestamp does the event \$display() have?

Events cause other events: signal "a" changes, creates event that changes "c".

Events placed in queue, pulled from queue for current step, new events added, until no events left in this time step.

← no ordering of events \*

Discrete Event Simulation

(versus Discrete Time Simulation)

# Ordering of Events


```

input c;
wire c;
output a, b;
reg a, b;
  
```

blocking assignment

```

 
initial begin
  a = 0;
  b = 0;
end
always @(c) begin
  a = c;
  b = a & c;
end
  
```



a's new value used for b.

```

c = 0
a = 0
event: c ← 1
  
```

 


non-blocking assignment

```

input c;
wire c;
output a, b;
reg a, b;
  
```

```

 initial begin
  a = 0;
  b = 0;
end
always @(c) begin
  a <= c;
  b <= a & c;
end
  
```



a's old value used for b

RHS evaluated in order, after preceding LHS assignment

RHS evaluated in parallel, globally, before LHS assignment

# Ports by name

```

module A;
    wire a, b, y;
    Bar foo( .in1(a), .in2(b), .out(y) );
endmodule


module Bar( out, in1, in2 );
    out <= #1 (in1 & in2);
endmodule
    
```

connect by name:  
order doesn't matter

Should def'n of bar be inside def'n of A?

How deep can nesting be?

One level.

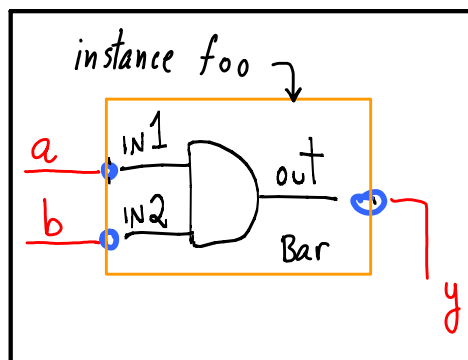

OR *order matters*

```
Bar foo(y, a, b)
```

# BUSES, Arrays


```

wire [7:0] busA;
wire [3:0] busB;
reg busAsrc;
assign busA = busAsrc;
assign busB = busA[7:4];

initial begin
    busAsrc = 8'd255;
end
//-- busAsrc = 8'hff;
//-- busAsrc = 8'b11111111;
    
```

wire order assumed →

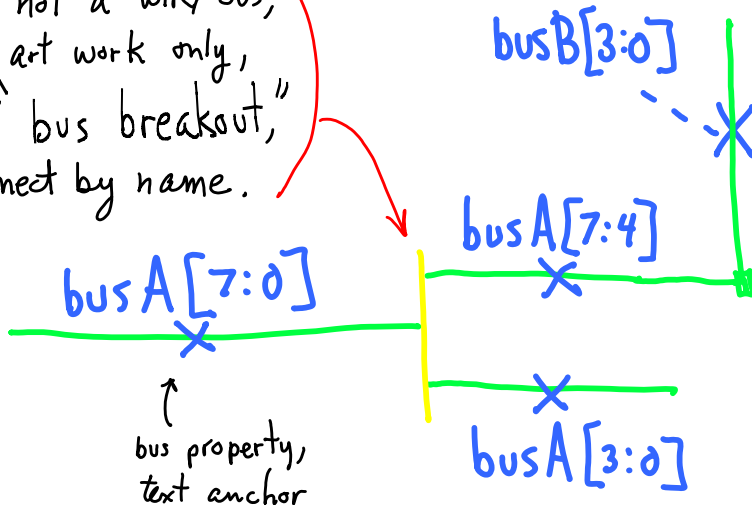not a wire/bus, art work only, "bus breakout," connect by name.



(See, Edit.SelectObject)

<u>nums</u>	<u>format</u>	<u>size(*bits)</u>	<u>format</u>	<u>number</u>
8	d		d	255
			h	FF
			b	1111 1111

( d = decimal format  
h = hex format  
b = binary format )

Combining busses

```


input [3:0] a, b;
output [15:0] y;

assign y = { 3 { a[3:0] }, b[3:2], 2'b00 };
    
```

*concatenate* (arrow pointing to the curly braces)

*duplicate and concatenate* (arrow pointing to the '3' and the first 'a[3:0]')

what is connected to:

 

# definitions, parameters

```

`define BUSWIDTH 16
reg [(`BUSWIDTH - 1) : 0] busA;

```

macro substitution.

(put defs in a header file and `include it)

`include header.vh  
(these are " " ie., back single quote)

# Parameters

```

module F();
  parameter WIDTH = 8;
  reg [ (WIDTH - 1) : 0] busA;
  ...
endmodule

```

seems redundant, but here's how we use it.

```


module H();
  defparam foo.WIDTH = 32;
  F foo;
  F #(16) bar;

```

set (override) parameter explicitly  
or set implicitly by order parameters were declared, e.g., #(10, 16, 2) sets parameters P1 = 10, P2 = 16, P3 = 2

# Arrays

```
reg [7:0] regWords [15:0];
```

 

e.g.,

```

regWords[1] = 8'b01010000;
regWords[1][0] = 1'b1;

```

What's in regWords[1]?

→ 01010001

# Tasks = methods

```

module memory(...);
  ...
  reg [7:0] regWords [15:0];
  integer i;

  task clear;
  begin
    for (i = 0; i < 15; i = i + 1)
    begin
      regWords[i] = 8'd0;
    end
  end
endtask

endmodule

```

Task


```

module top ();
  memory mem;
  initial begin
    mem.clear;
    mem.regWords[0] = 8'b000111;
  end
endmodule

```

invoke Task

# Naming in hierarchy

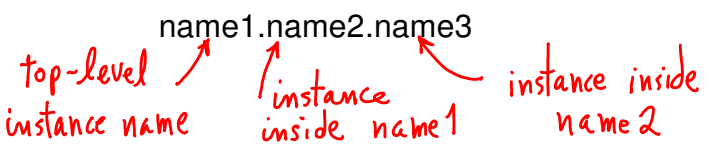

# Pre-defined Tasks

`$display( "...", ... );`

— has eoln

`$write( "...", ... );`

— no eoln

`$time;`

— simulation time step

`$monitor( "...", ... );`

`$strobe(...);`

} — like `$display`, but w/ implicit "always @(x)"  
(broken?)

`$fopen( ... );`

`$fwrite( ... );`

} — uses Multi-Channel Descriptor: multiple files,  
or use a File-Descriptor: 1 file

`$readmemb( "filename", dataArray);`

— (reads data into model,  
text file contains binary notation)

`$readmemh( "filename", dataArray, ...);`

— (reads data into model,  
text file contains hex notation)

`$dump(...);`

— dumps every signal @ every change, use w/ GTK wave

`$stop;`

— goes into interactive mode, then enter "`$finish`" to quit.  
NB - entering `ctrl-c` during simulation also goes to interactive mode.

`$finish;`

— quit simulation

# More Signal propagation delays

\*2 A = B } B sampled and A changes both at  $t+2$

A = \*2 B } B sampled at  $t$ ,  
A changes at  $t+2$

and \*(3,2) and1(y, A, B) } A or B changes, causing Y change      Y changes @

↑ implicit set parameters

Y → 1	t+3
Y → 0	t+2
Y → 3	t + min(3,2)

wire A  
assign \*2 A = B & C } B + C sampled at  $t$   
A changes at  $t+2$   
(unless b, c change → canceled)

wire \*2 A;  
assign A = B & C } wire A takes 2 ticks to see (B&C),  
same as above.

```

always @(posedge clk) begin
    a = b;
    @(negedge clk)
    a = ~b;
    @(c or clk)
    a = 0;
end
    
```

} What's in "a" if c doesn't change?



How many times does c change?

always begin

```
wait(a);
#1
c = ~c;
```

end

only waits if  
 $a \neq 1$  (0, x, z)  
 $\cong$  wait-until (a==1)

initial begin

```
c = 0;
a = 0;
#3
a = 1;
#3
a = 0;
#1
$finish;
```

end

→ easy way to

find the answer :


always @(c) begin

```
*1 $display("%b", c);
end
```

what happens to Q1, Q2?

```
always @(posedge clk) Q1 = D;
always @(posedge clk) Q2 = Q1;

 initial begin
    @(posedge clk) D = 0;
    @(negedge clk) D = 1;
end
```



MODELS

STRUCTURAL

and A(y, x, z)  
 or B(z, y, x)

Dataflow

assign z = (y | x);  
 assign y = (x & z);

Behavioral

```
if (x == 0)
    z = 1;
    y = 0;
```

## Other language elements

---- Looping (forever, while, for)

These can appear inside an "initial" or "always", and can thus start at times other than 0. Conditionals are T if they evaluate to 1, F if they evaluate to 0, x, or z. "Forever" is the same as "while(1)".

---- Control (fork, join)

Creates parallel event streams that synchronize at the "join": all enclosed "begin-end" blocks run in parallel and the last to finish exits the "fork-join". E.g.,

```
fork
  begin ... end
  begin ... end
join
```