
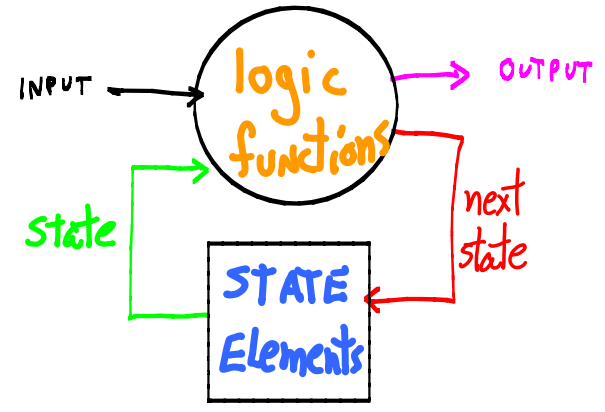


TM Implementation

 


To build any TM, WE NEED:

- (1.) FSM:
 - state
 - logic functions (output and next-state)
- (2.) Tape: methods to R/W symbols, we'll use registers (RAM).
- (3.) Symbol set = a set of fixed length bit strings, e.g.,
 - S = {0,1} (2 symbols)
 - S = {00, 01, 10, 11} (4 symbols)
 - S = {000, 001, 010, 011, 100, 101, 110, 111} (8 symbols)

Build FSM

even-odd parity

 

{symbols} = {0, 1}
 {states} = {A, B} $\xrightarrow{\text{encode}}$ {0, 1}

functions {
 OUT: {states} x {symbols} \rightarrow {symbols}
 next-state: {states} x {symbols} \rightarrow {states}

OUT		OUT
(A, 0) \implies 0	$\xrightarrow{\text{encode}}$	(0, 0) \implies 0
(A, 1) \implies 1		(0, 1) \implies 1
(B, 0) \implies 1		(1, 0) \implies 1
(B, 1) \implies 0		(1, 1) \implies 0

next_state		next_state
(A, 0) \implies A	$\xrightarrow{\text{encode}}$	(0, 0) \implies 0
(A, 1) \implies B		(0, 1) \implies 1
(B, 0) \implies B		(1, 0) \implies 1
(B, 1) \implies A		(1, 1) \implies 0

We Need:

- functions
- STATE ELEMENTS

- in hardware for simulator/computer/UTM.
- in description language for any TM.

Boolean functions

Universal (able to simulate any TM)

- language to describe any TM,
- Simulator that understands that language.




LANGUAGE

- able to describe:
- Arbitrary set of states, including regs (= vars)
 - Arbitrary set of symbols
 - Arbitrary branching (via binary trees)
 - RW to tape
 - Arbitrary functions (next-state, output)

UTM/simulator/computer

- current state (PC and vars)
- read tape (LDR)
- OUT: ADD, AND, NOT ...
- next-state: ADD, AND, NOT ...
- write tape (STR)
- change state PC++, JMP, BR
- STR ==> new data state (vars)
- STR ==> new control state

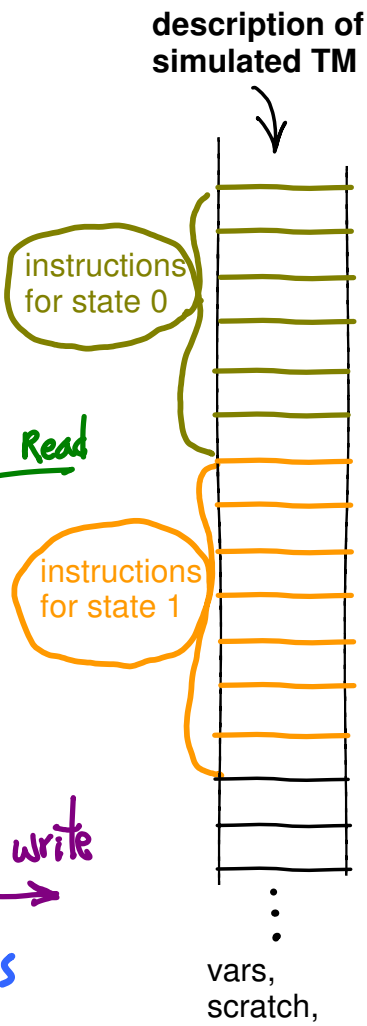  Description uses small pieces, "instructions" are "executed"



control signals (pink arrows)
data signals (blue arrows)


FSM Controller uses registers (e.g., PC) to remember:

- simulated machine's state (control + data states)
- simulated symbols read (RegFile)
- simulated write symbols (RegFile)
- step of simulation (UTM's controller's state)
- partial steps of function evaluations (next-state, output) data registers, PSR, on tape, ...

STATE ELEMENTS

pos. edge-triggered
FF


Problem:
*Katy bar
the door*

 


Feedback loop:

state change,
NS change,
state change,
NS change, ...


①

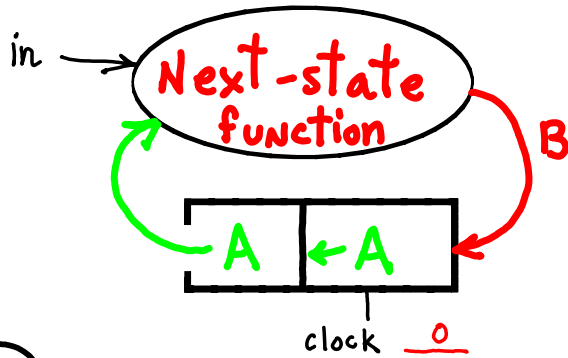

②

 


③

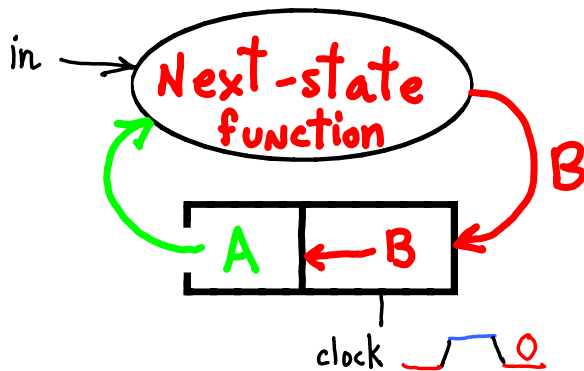


input "sampled"
"latched"

4

 


rising clock = state change

5

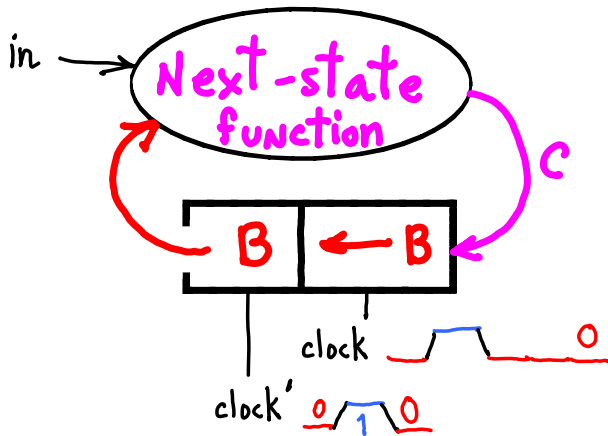

Back at ①

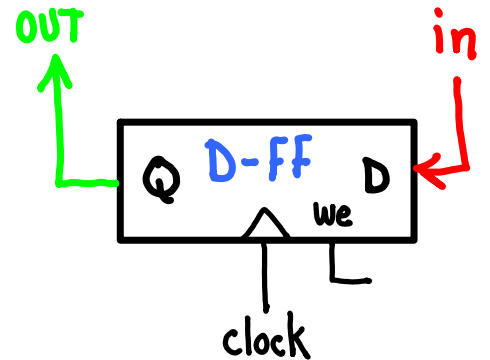This is what we need for implementing STATE.



Describing Functions

Two Ways

(A) for any x
describe how to evaluate $f(x)$ E.g. $f(x) = 2x$

(B) provide a table giving $f(x)$ for any x
E.g.

x	$f(x)$
0	1
1	0

(B) microcoded controller next-state & output functions


A-Reg == controller's **current state**
addresses **uCode ROM**
gives memory **word at output**

ROM **Word** == datapath **control bits**
C-Reg has **current control word**
controls datapath


next-state fields of **C-Reg**
Part of Controller's **next-state** function

Control branching (the rest of **next-state** function)
-- 2-way, **NS1** or **NS2**
-- $MUX.select = f(STATE, IR, \dots)$

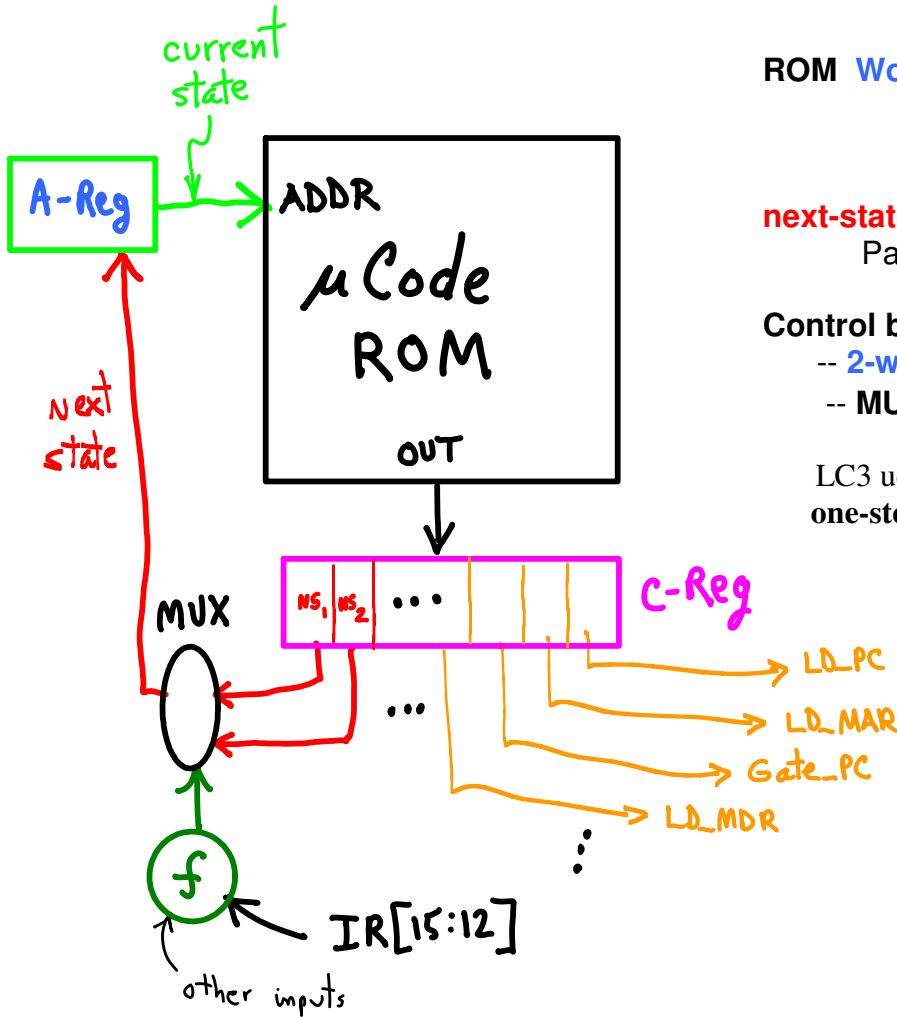LC3 ucode branching also includes
one-step, 16-way branching (DECODE).



As a general FSM,
it looks like this,

 

Advantages of ucode controller:

- easier to **change**
- easier to **figure out**
- easier to **expand**
install bigger ROM.

Advantages of "random logic" controller:

- **faster**
- **smaller** (?)
- **distributed** throughout machine


Caveat: The C-Reg is just to
make the picture clearer, it
doesn't actually exist in LC3.

WE HAVE (suppose for now)



- 1-bit state elements
- 1-bit function elements

HOW to put them together?

A mod-3 machine

 

STATE ENCODING

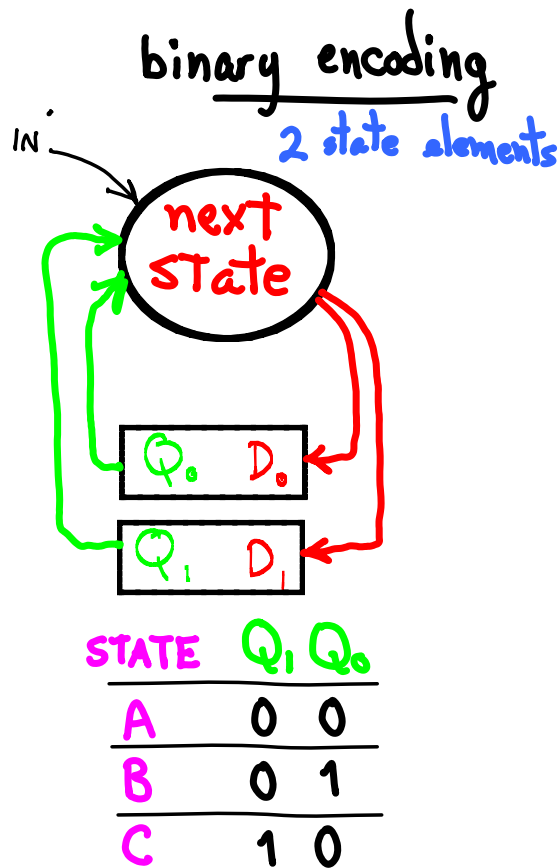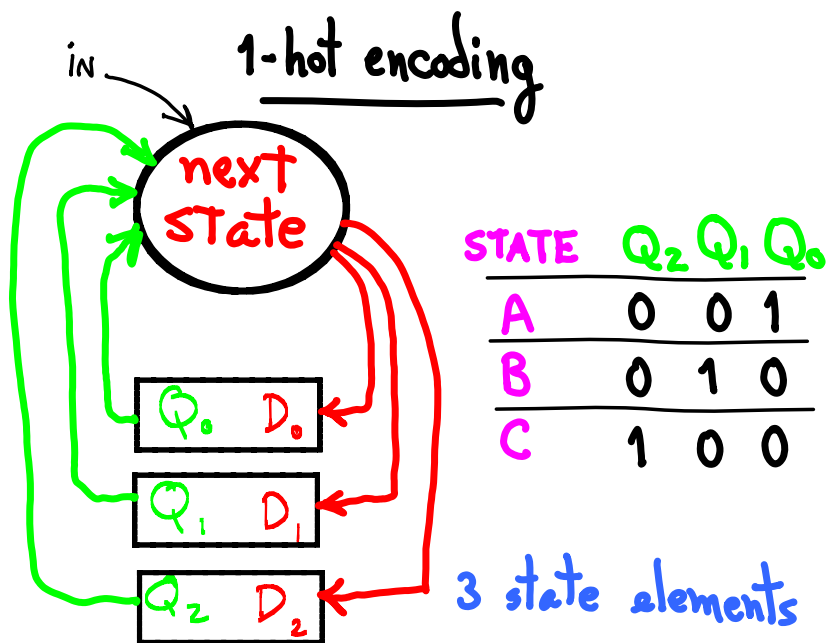



Describe next-state function

IN	Q ₂	Q ₁	Q ₀		D ₂	D ₁	D ₀	
0	0	0	1	(A)	0	0	1	(A)
1	0	0	1	(A)	0	1	0	(B)
0	0	1	0	(B)	0	1	0	(B)
1	0	1	0	(B)	1	0	0	(C)
0	1	0	0	(C)	1	0	0	(C)
1	1	0	0	(C)	0	0	1	(A)
*	*	*	*		X	X	X	

x				$f(x)$	
IN	Q ₁	Q ₀		D ₁	D ₀
0	0	0	(A)	0	0
1	0	0	(A)	0	1
0	0	1	(B)	0	1
1	0	1	(B)	1	1
0	1	1	(C)	1	1
0	1	1	(C)	0	0
*	*	*		X	X

* rows not shown, don't matter?
X is for **don't care**, either 0 or 1.

* rows cannot be reached.

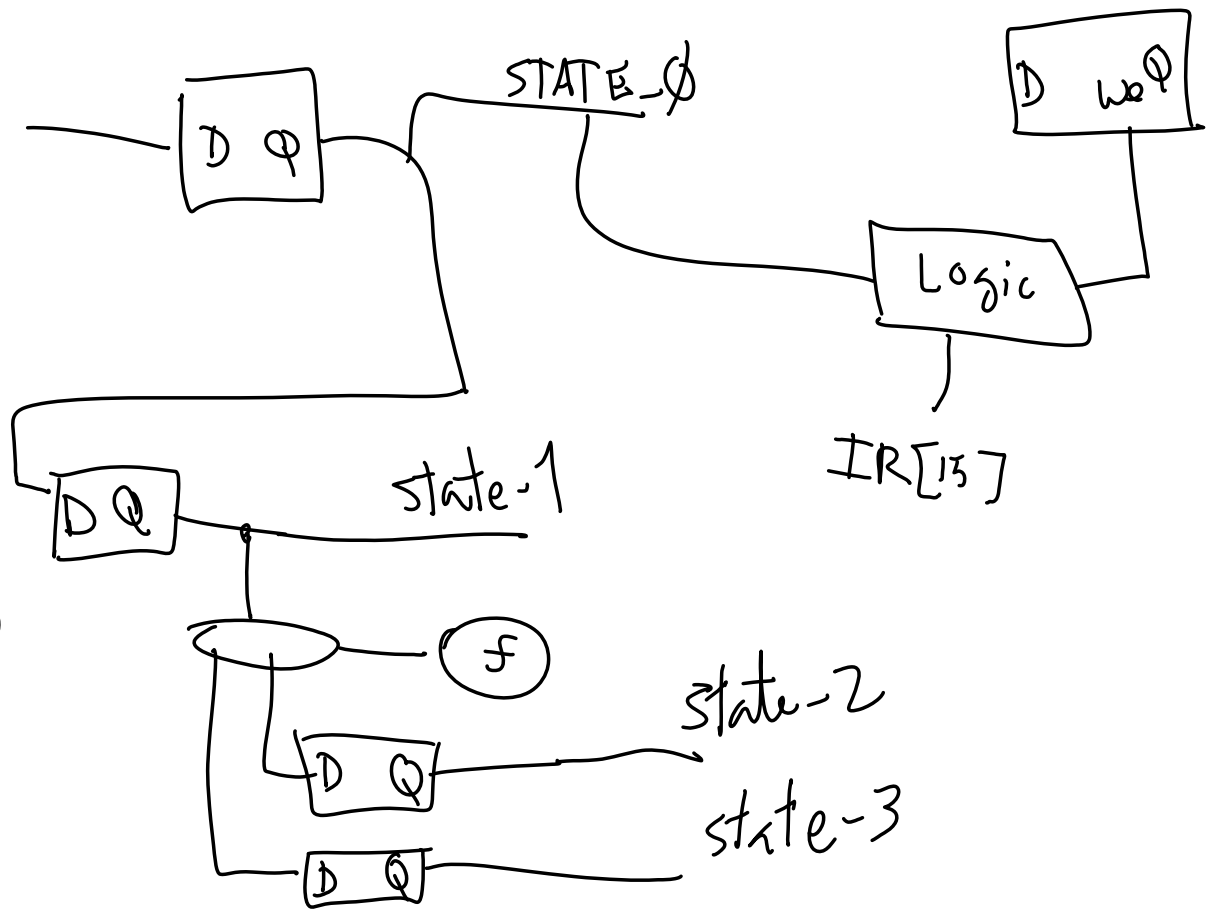 

IF we have a **universal language** (able to describe **any TM**)

All we need to know is **How To Build**:

--- **1-bit state elements**?

--- **1-bit functions**?

