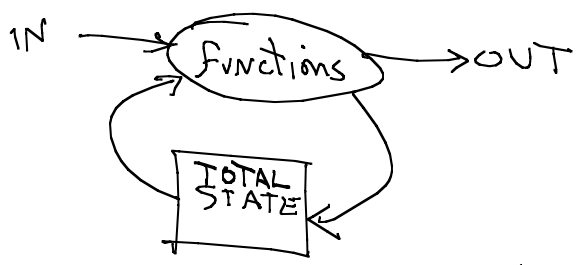


FSM implementation



- need to build
1. Symbols
 2. functions
 3. State
 - (4. tape, for UTM/computer)

Any technology will do!


mechanical: Babbage, etc.

electro-mechanical ← we start here


electronic

?

Electrons and heat

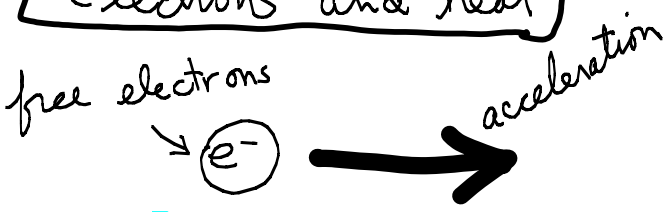

$E_{lec. field} \approx gravity$

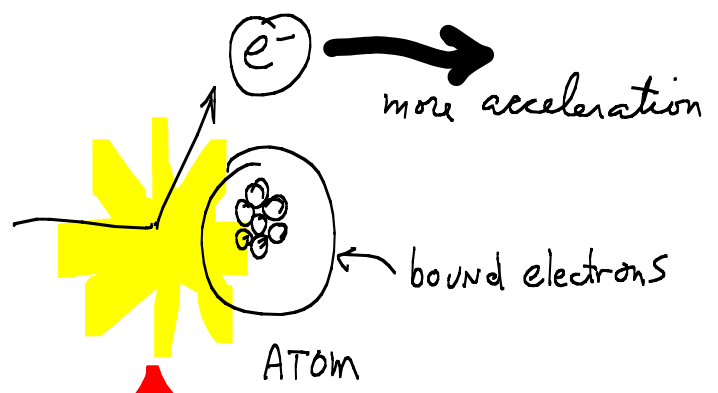

$E \times distance = Voltage$


Collision transfers energy to atoms of material, e.g. wire.
 Atom motion = heat.
 ~ All collision energy goes to heat.

High current = Lots of moving e^-
 High voltage = Lots of acceleration







High Voltage + High current = Lots of Heat = $\frac{energy}{sec} = Power = I \cdot V$

Ohm's Law, conductors, ...


$R \stackrel{\text{def.}}{=} V/I$

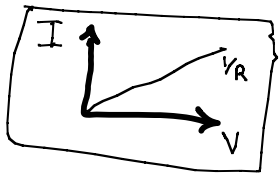

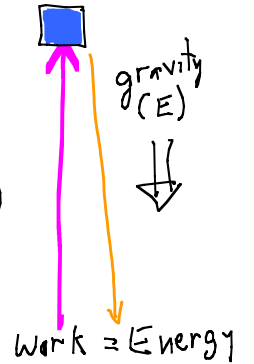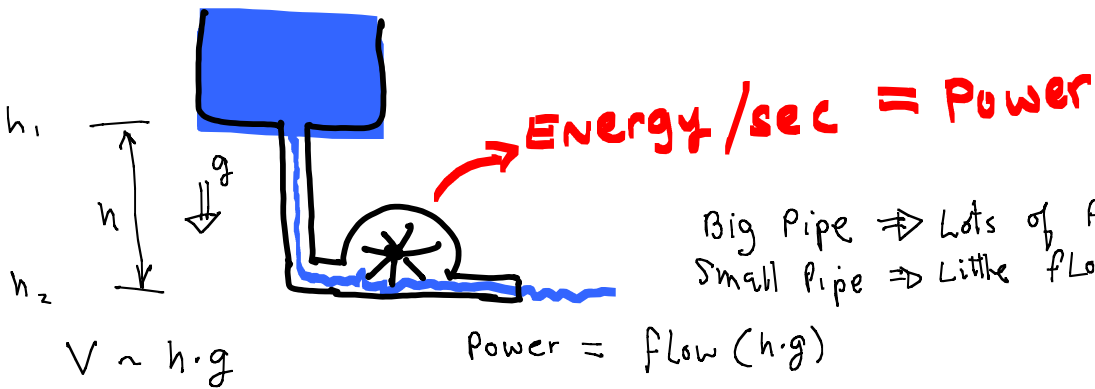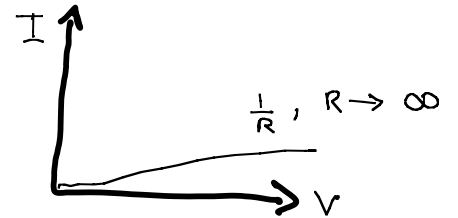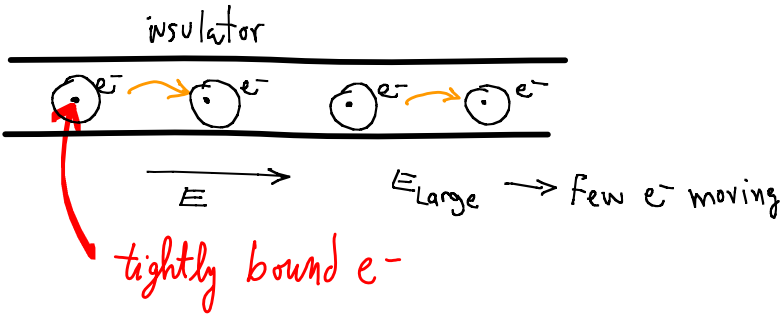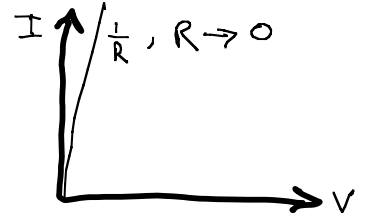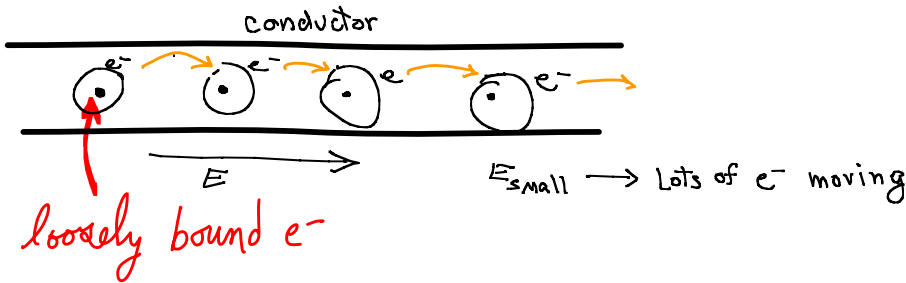$\Rightarrow I = (1/R)V$ $\Rightarrow V = IR$
 (if relationship is linear, then Ohm's Law Resistor) OR Linear device.



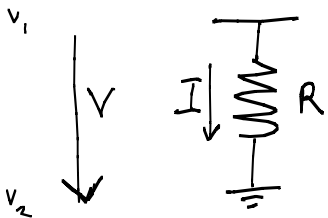$V = E \times \text{distance}$
 \sim Tower height \times gravity



$V = IR$


fix V: as $R \rightarrow 0$ then $I \rightarrow \infty$
 as $R \rightarrow \infty$ then $I \rightarrow 0$


$V = V_1 - V_2$

Power = $I V$
 ← Energy over distance per e^-
 ← $\times e^-$ per second

power = energy/sec
 $= I \cdot V = I \cdot (I \cdot R) = I^2 \cdot R$
 $= I \cdot V = (V/R) \cdot V$

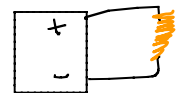$R \rightarrow 0$ then Power $\rightarrow \infty$
 $R \rightarrow \infty$ then Power $\rightarrow 0$



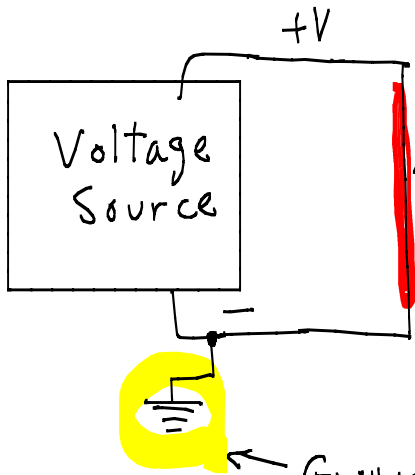


What if this is wire, ie., R is nearly 0?
Voltage source holds constant V voltage difference.

Then current $I = V/R$ goes to infinity.

Then power dissipated to heat = $I*V$ goes to infinity.

Infinite release of ENERGY! BOOM! (Actually, wire and/or supply melts, Ohm's Law not a good approximation at that point.)

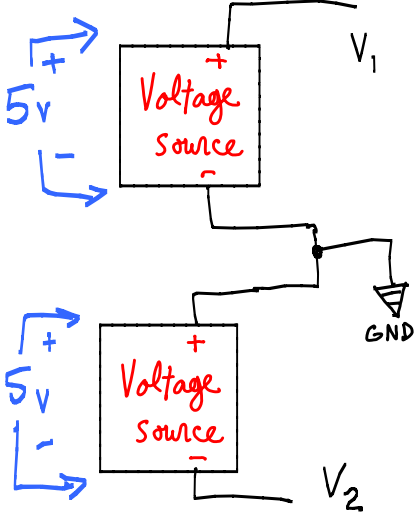Ground symbol $\equiv 0$ volts, by definition





Measure voltage difference from voltage point at GROUND.

What voltage do we call V1?

What voltage do we call V2?

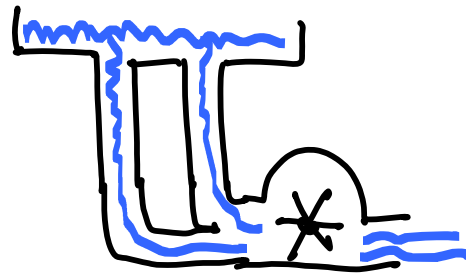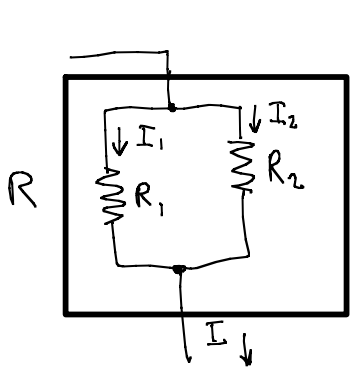V1 = +5v relative to GND
V2 = -5v relative to GND



Resistors connected in PARALLEL.

Same as two water pipes in parallel: less resistance to flow, total flow is sum of flow in both.

Water pressure, voltage, is same for both paths.


$i = i_1 + i_2$

If $R_1 = R_2$ Then $i_1 = V/R_1 = i_2$

$i = i_1 + i_2 = 2*V/R_1$

What is total R?


$R = V/i = V/(2V/R_1) = 1/2 R_1$

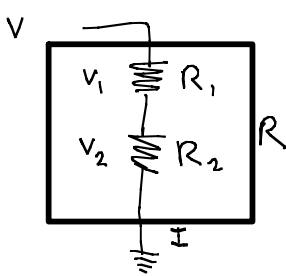

Resistors connected in SERIES.

Same as two pipes end-to-end: more resistance, less flow, same flow in both.

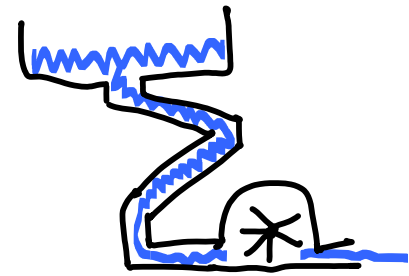
$R = V/i = (V_1 + V_2)/i$
 $V_1 = i*R_1$ $V_2 = i*R_2$
 $R = (i*R_1 + i*R_2)/i = (R_1 + R_2)$



We need Signal-Restoring, Non-Linear Logic. Ohm's Law devices are LINEAR.


Suppose we had only linear devices (or something very nearly linear), then signal output has errors proportional to input errors.

Errors/noise :

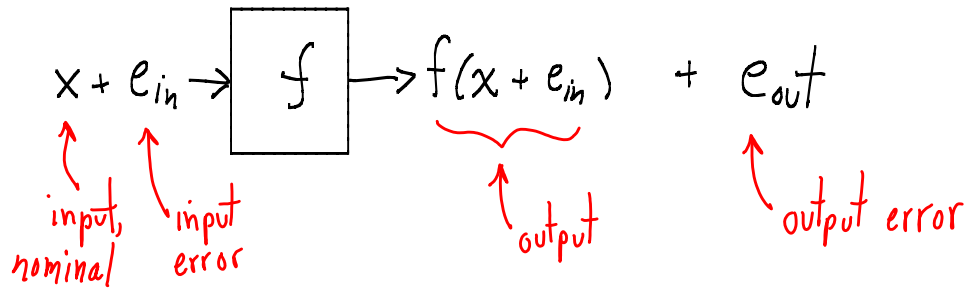


Linearity:
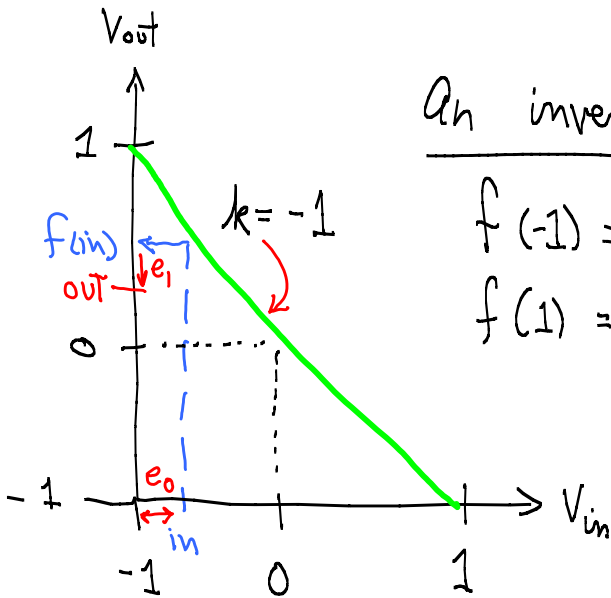
$$f(v + e_{in}) = k(v + e_{in}) + e_{out} = kv + \underbrace{ke_{in}}_{\text{Total error}} + e_{out}$$



Suppose we connect 2 in series

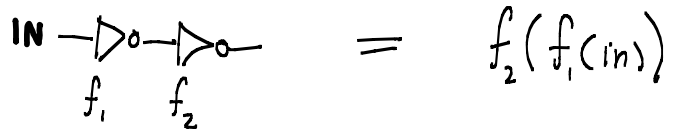

$$\begin{aligned}
 f_1(in) &= f_1(v + e) = kv + ke_0 + e_1 \\
 &= (-1)(-1) + (-1)e_0 + e_1 \\
 &= 1 - e_0 + e_1
 \end{aligned}$$

(v is nominal signal: ± 1)

$$\begin{aligned}
 f_2(f_1(in)) &= f_2(1 - e_0 + e_1) \\
 &= -1 + e_0 - e_1 + e_2
 \end{aligned}$$

k stages $\Rightarrow 1 + \sum_{i=0}^k e_i (-1)^i$


The errors include signs = random walk with random size steps.

Errors independently random w/ average 0 \Rightarrow variance increases w/ k.
 Total error grows w/o bound!

Take random step (either in the -1 or +1 direction).
 How far from 0 can you expect to be after k steps? About $k^{1/2}$ away.
 With probability 0 you will be at 0, and error gets unboundedly large.

We must Reduce error at each stage ==> exponentially decreasing effect in later stages.

Non-Linear

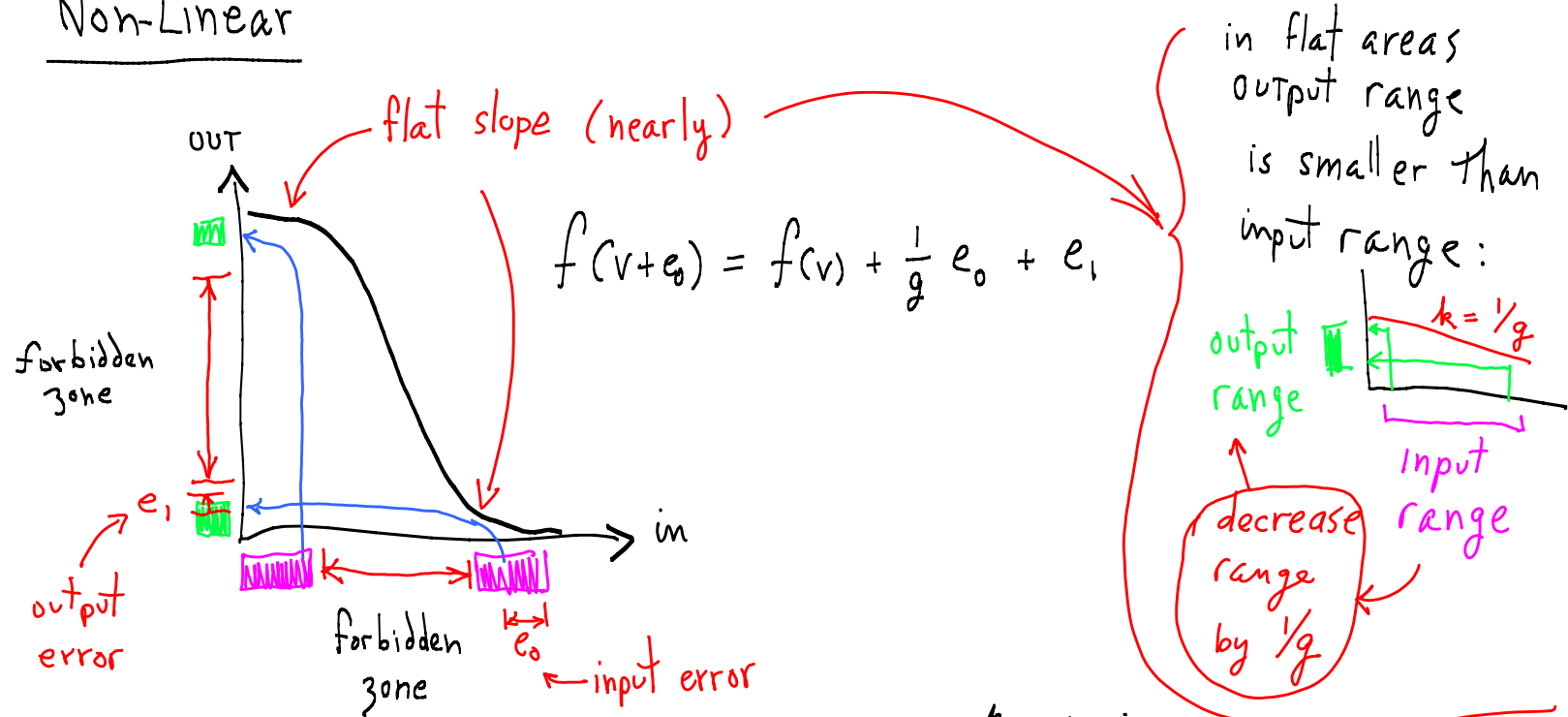

after k stages:
$$= 1 + \sum_{i=0}^k \left(\frac{1}{g}\right)^i e_i$$

Converges!

If g is large enough (flat areas of curve are flat enough),

and

if output error size is not too big,

Then



output after k stages never hits FORBIDDEN ZONE.

So, if we plan to have a circuit with long device chains, we must have non-linear devices w/ suitable response curves.



Do we plan to have long chains? YES:

- (1) feedback in system,
- (2) chained data operations: $D1 \implies D2 \implies D3 \implies D4 \dots$
- (3) 1 Billion devices per cpu

Devices

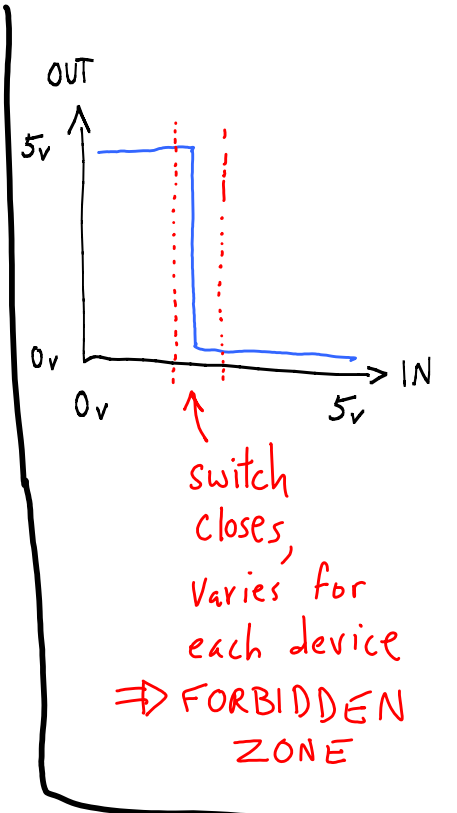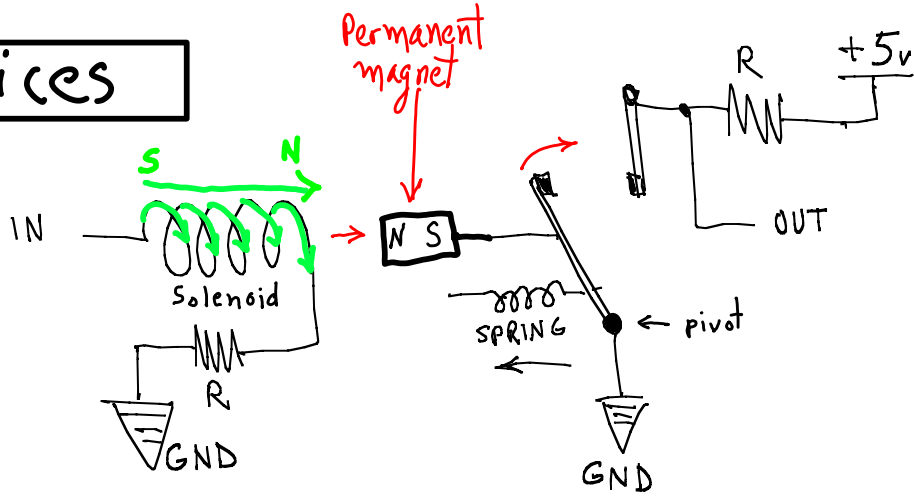


$V = IR$

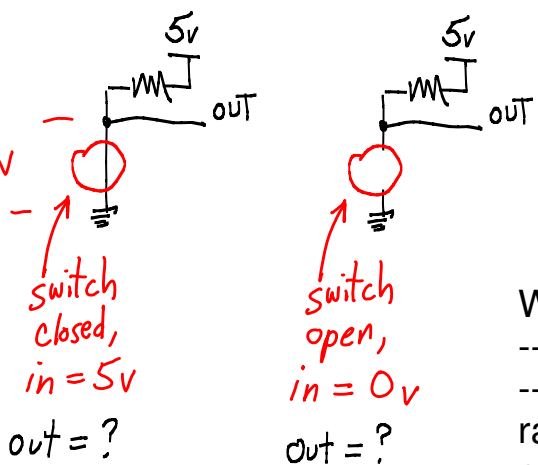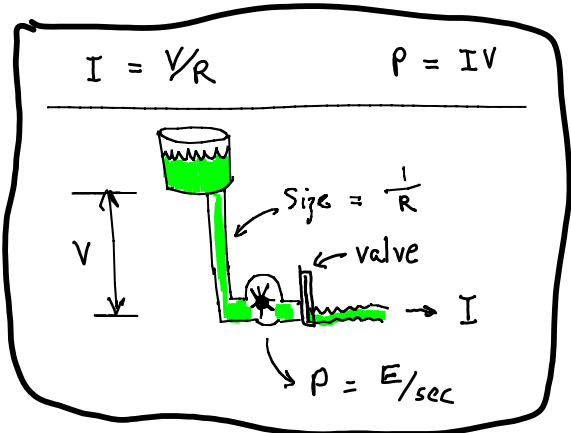

What is the function?
 --- non-linear response
 --- any voltage in allowed range will yield "clean" output. Easy to prevent input voltages in forbidden zone.


Electronic Switches: Vacuum Tubes

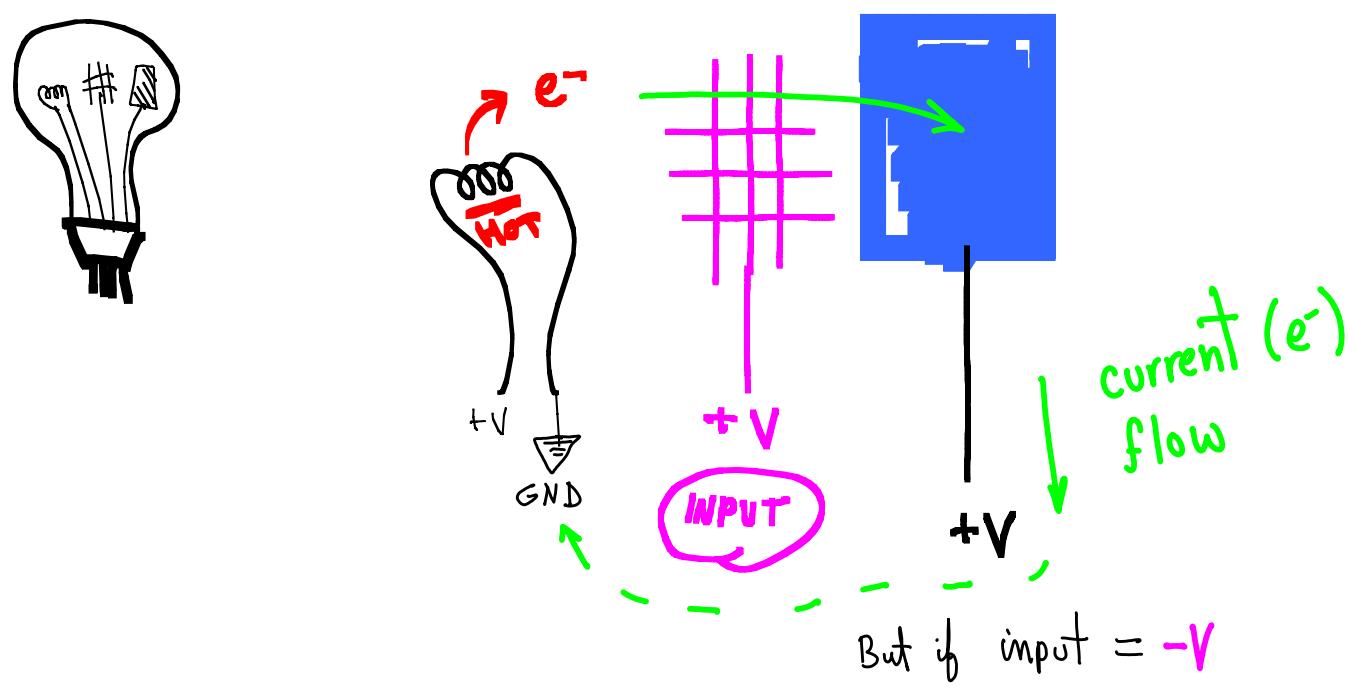

Voltage Controlled Switch
 faster, more reliable, less power

Solid state devices - Semiconductors

Silicon Crystal

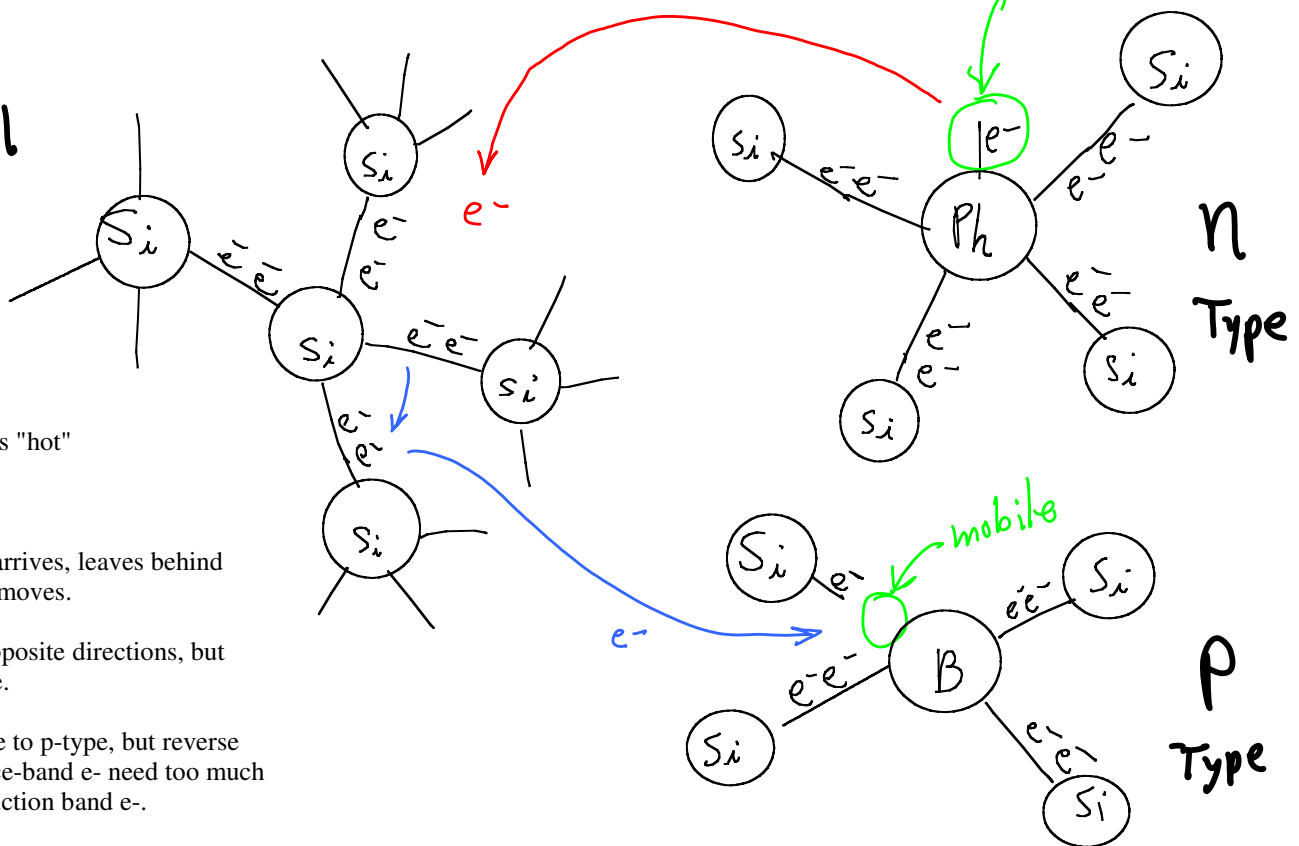



Phosphorous impurity:
e- leaves easily, becomes "hot" conduction-band e-.

Boron impurity:
"cold" valence-band e- arrives, leaves behind +valence "hole" which moves.

Holes and e- move in opposite directions, but current direction is same.

Easy e- flow from n-type to p-type, but reverse flow hard: "cold" valence-band e- need too much energy to become conduction band e-.


MOSFET n-type

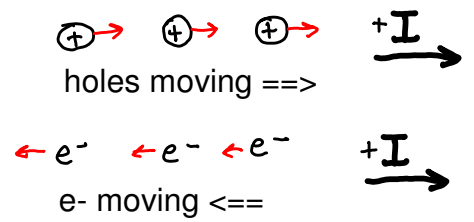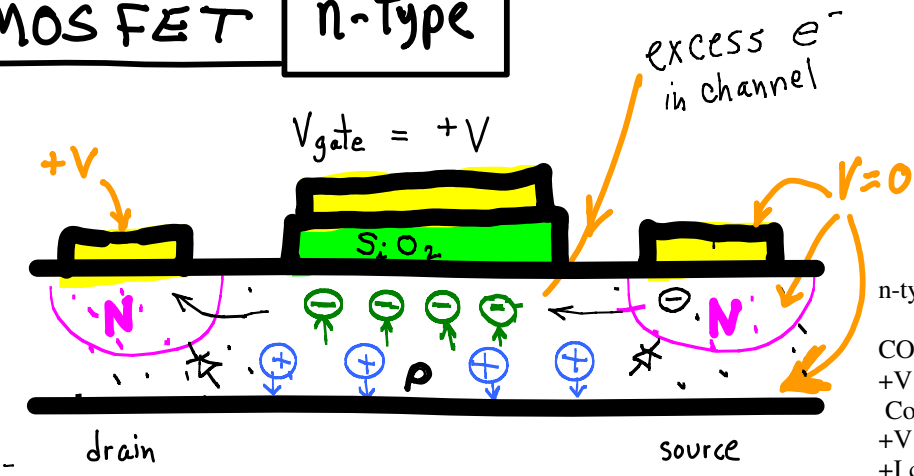

n-type MOSFET (n-transistor)



CONDUCTING (V_{gate} = +V, R_{drain-source} ≈ 0):
 +V on gate drives holes away from P-type channel.
 Conduction-band e- move from source N-type well.
 +V on drain pulls conduction-band e- off.
 +I current flows left-to-right.

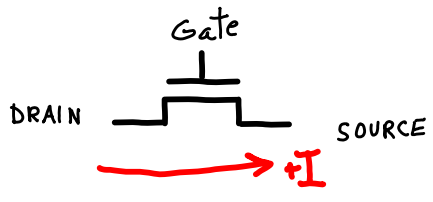NOT-CONDUCTING (V_{gate} = 0, R_{drain-source} = BIG)
 V_{gate} = 0, holes populate channel.
 Source N-well e- drop into valence band in channel.
 +V at drain cannot pull valence-band e- from P-type to N-type.




n-type transistor

V _{gate}	R _{drain-source}	State
0	∞	not conducting
+V	0	conducting

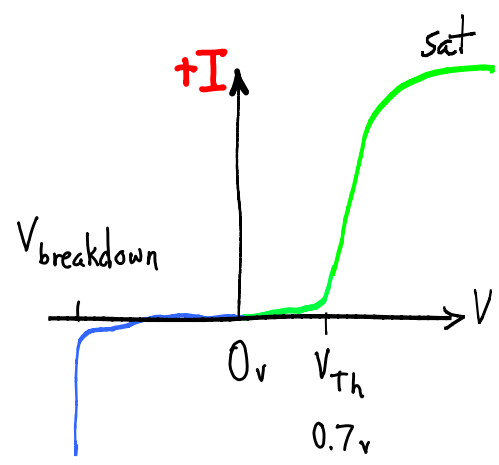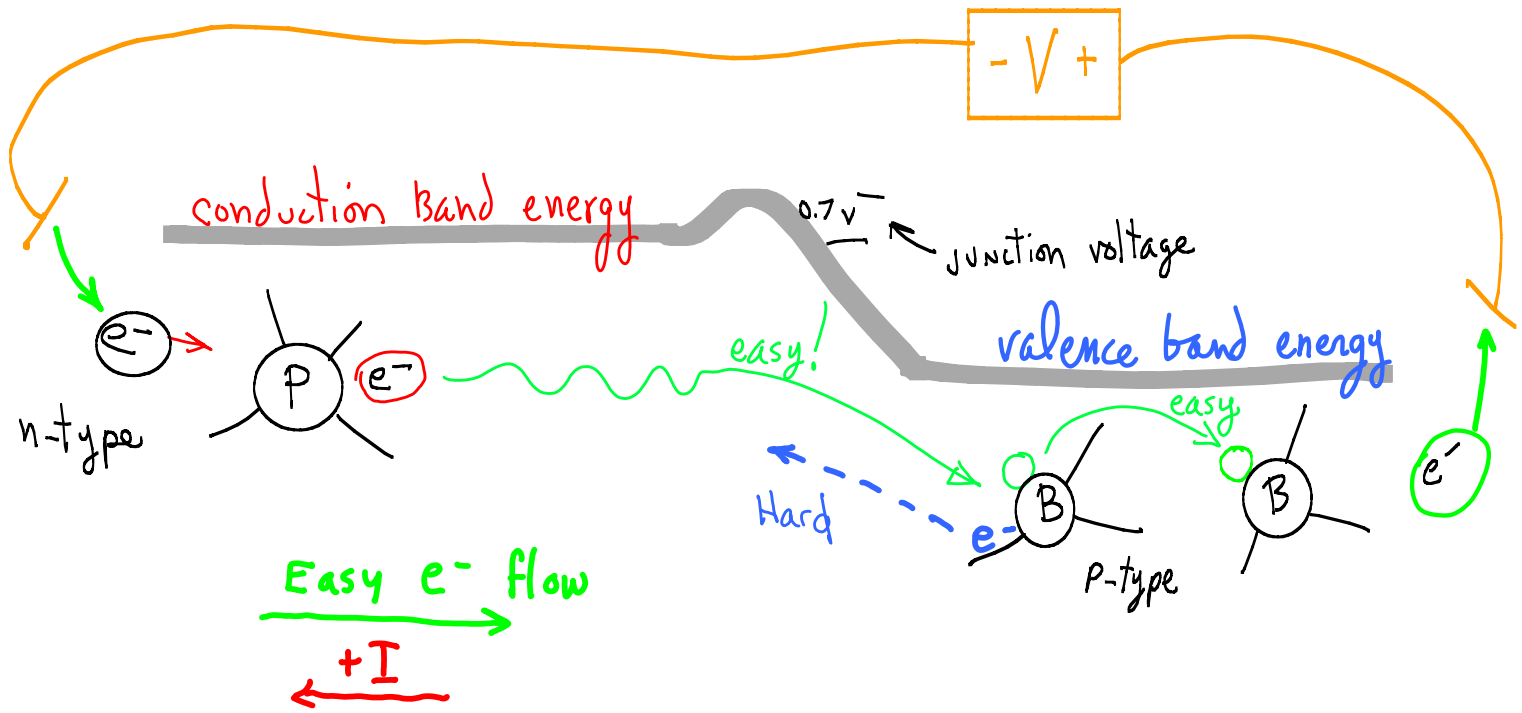



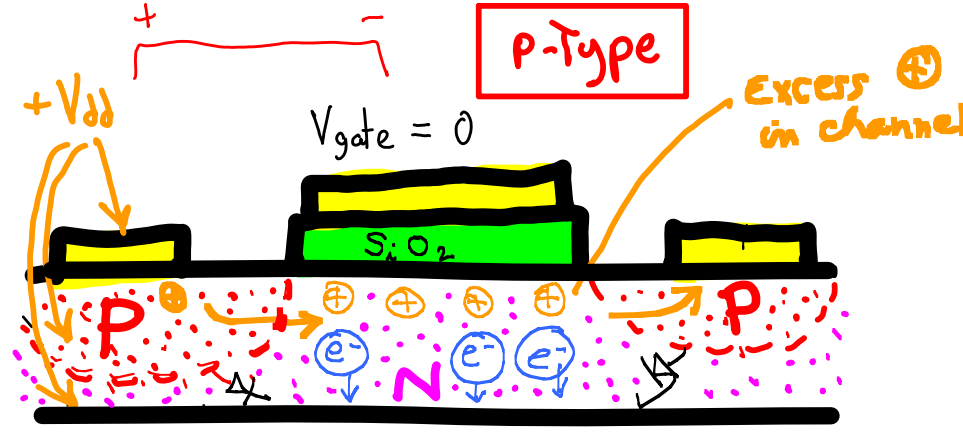
Just what we want: nice non-linear switch.





P-type (n-channel) transistor


$V_{gate} = 0$:
 $V_{gate} = -V_{dd}$ wrt to base,
 pushes e^- away from channel, leaves
 excess holes, current flows.
 $R = 0$, conducting.

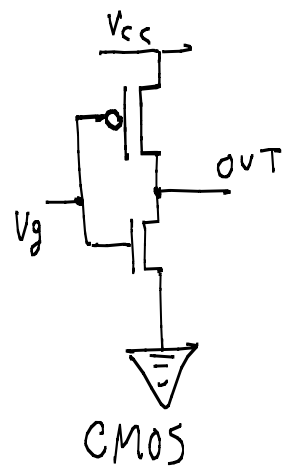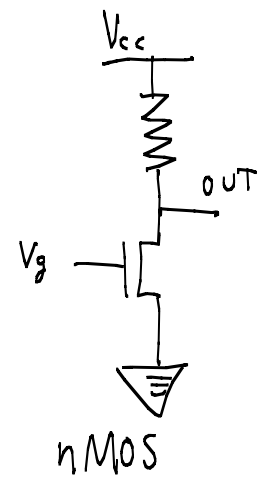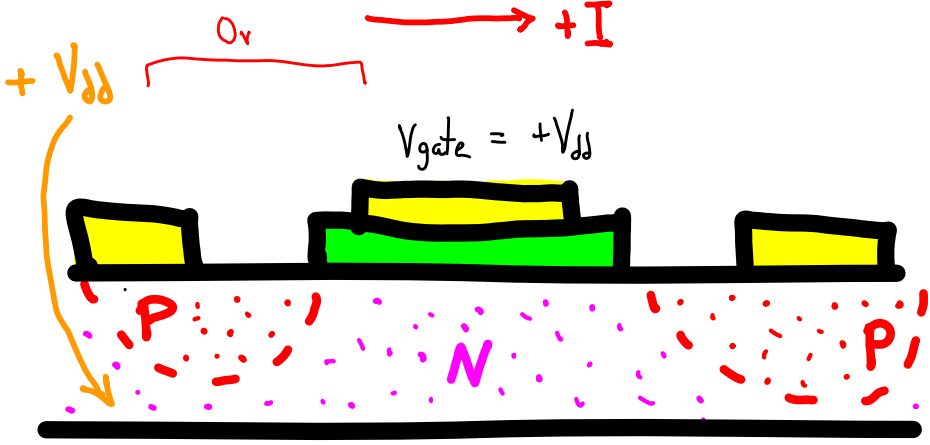$V_{gate} = V_{dd}$:
 $V_{gate} = 0$ wrt to base
 channel is neutral
 only random thermal e^- available for
 current flow.
 $R = \text{infinity}$, not conducting





chip fab.

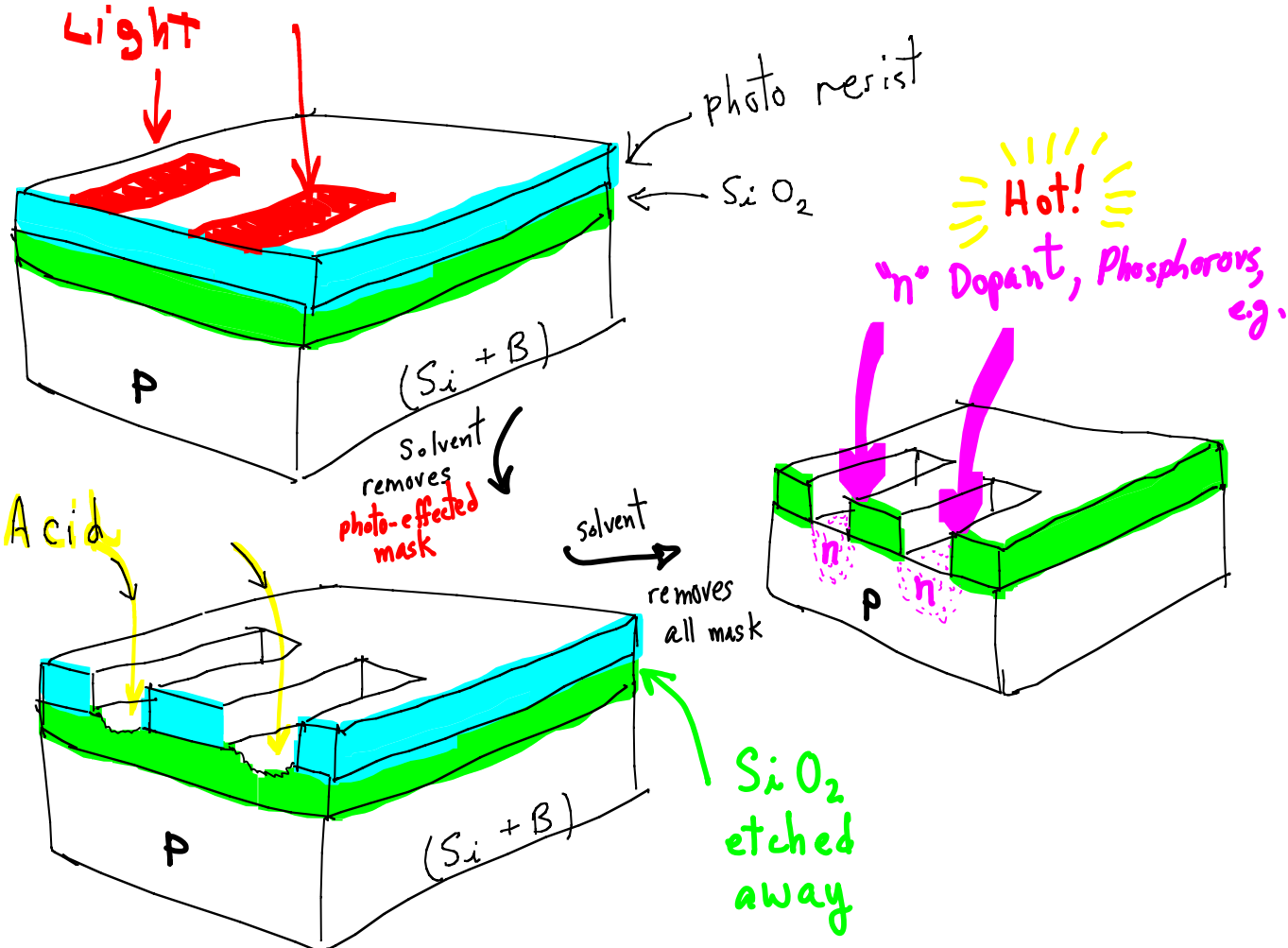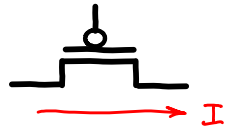


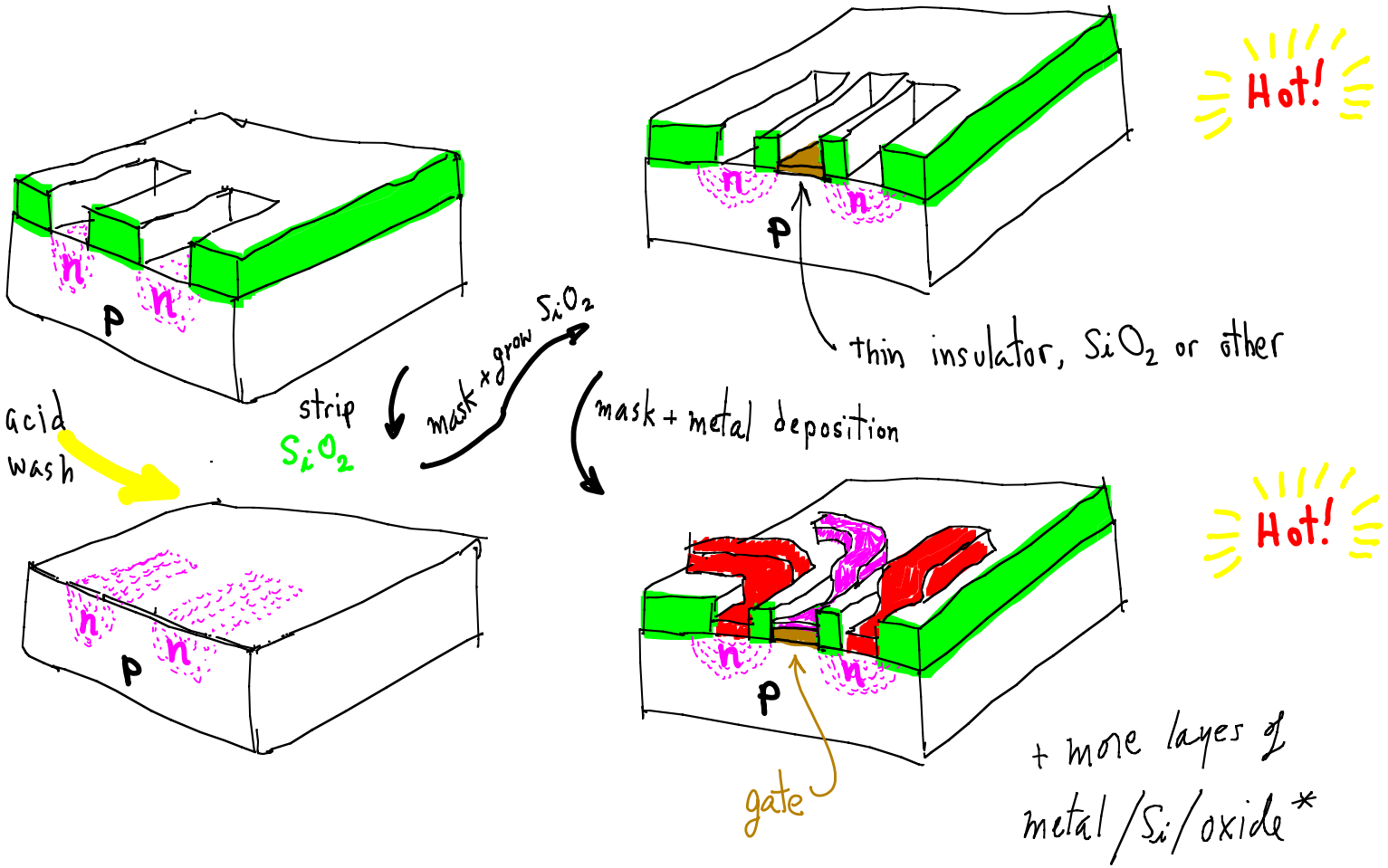

Line Sizes

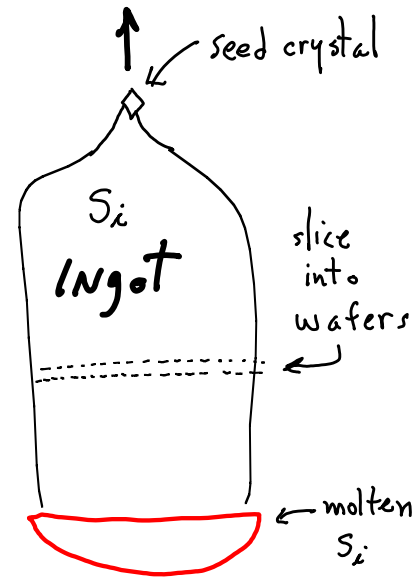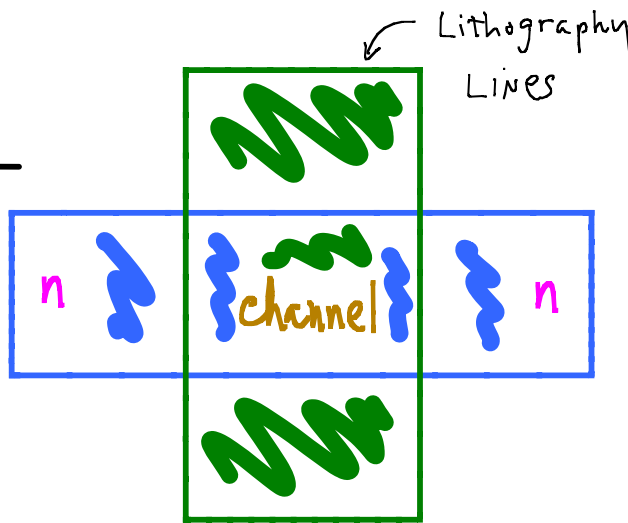

Wafer

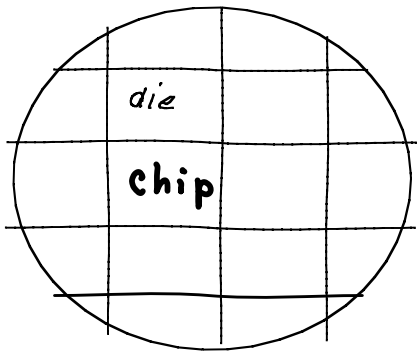

Better Process
more expensive equipment +\$

lines shrink



10nm

faster switching
→ faster clock


- more transistors
- more function
- more usage
- more sales
- same price

smaller features → more defects, lower die yield, but smaller die → Moore's Law

Basic Logic Gates

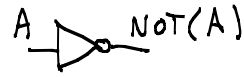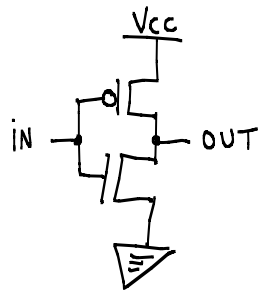

A	NOT(A)
0	1
1	0

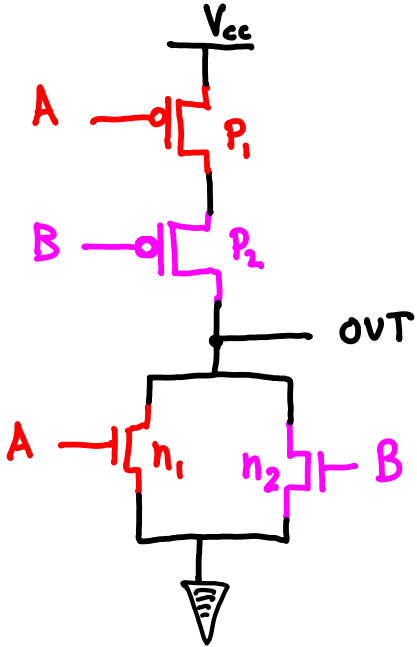

A	B	P ₁	P ₂	N ₁	N ₂	OUT
0	1		✗	✗		0 _v
1	0	✗			✗	0 _v
0	0			✗	✗	V _{cc}
1	1	✗	✗			0 _v

NOT(OR)

A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

NOR

not conducting

Logic Circuits



Two kinds of logic circuits:

- (1) w/ feedback, SEQUENTIAL: can hold STATE
- (2) w/o feedback, COMBINATORIAL: realize FUNCTIONS



Basic logic gates: NOT, 2-input NOR, 2-input NAND.

That's all we need for both sequential and combinatorial circuits.

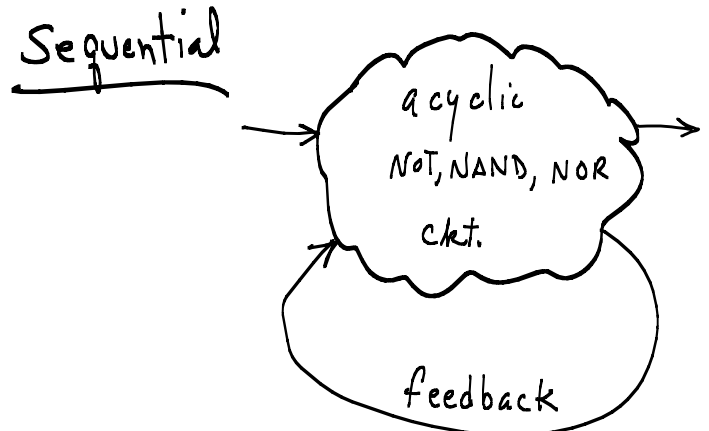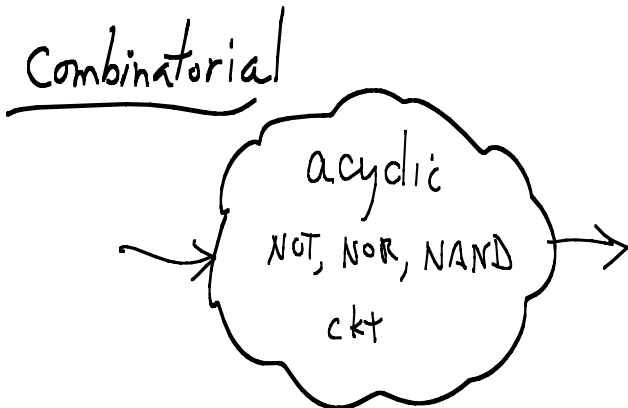(NAND alone is sufficient, also NOR alone is sufficient.)







State feedback

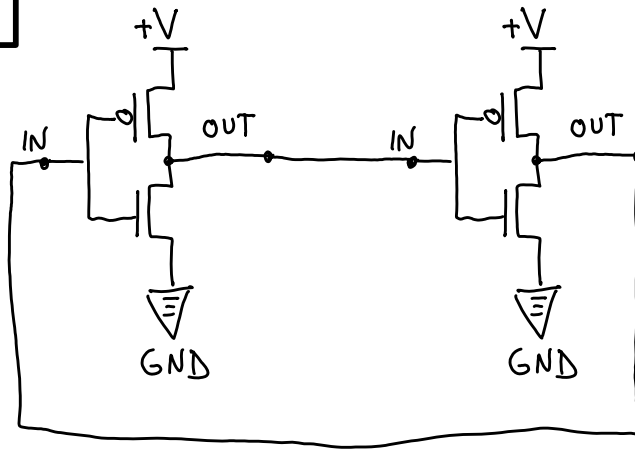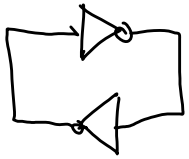

what are the voltages?

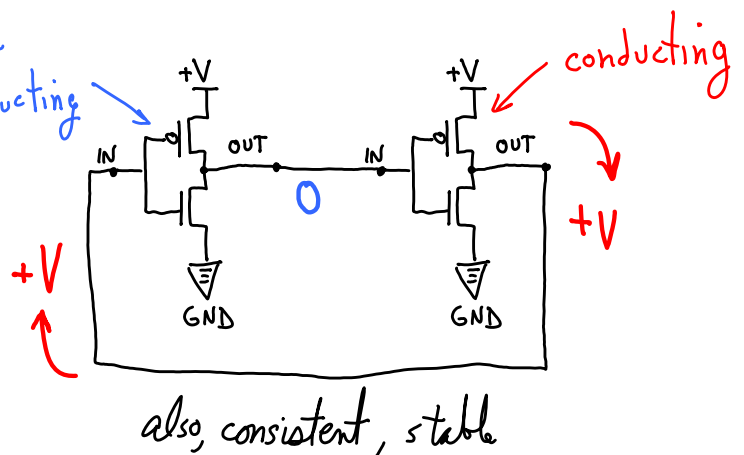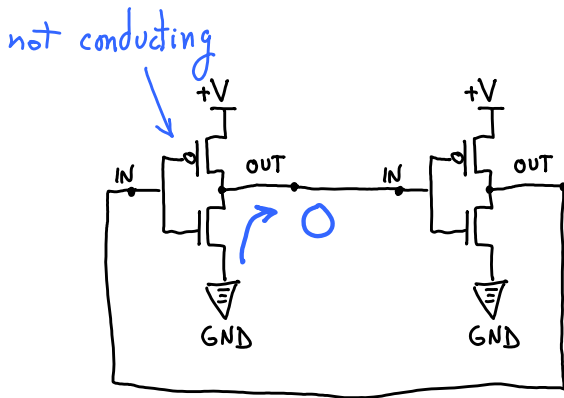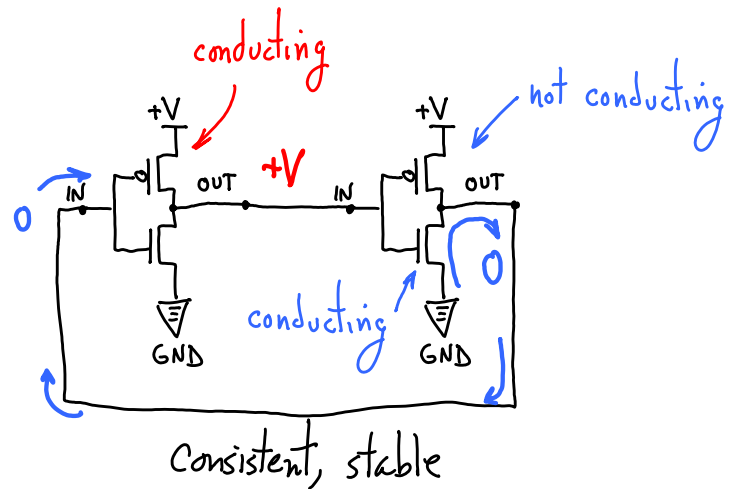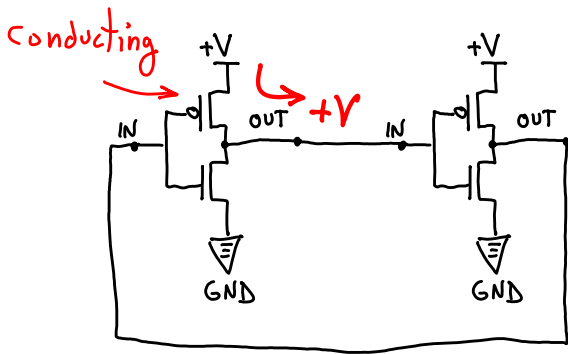Assume state \rightarrow see if consistent




Circuit has two stable states: aka, meta-stable, bi-stable.


What state when power is first turned on? Unknown, random.

Can we set the state, using voltage inputs? No, useless!?!

Basic Sequential elements

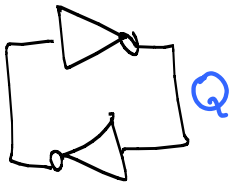


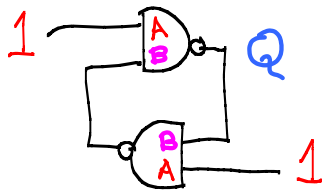not-not loop stores data, but we want control.





NAND

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

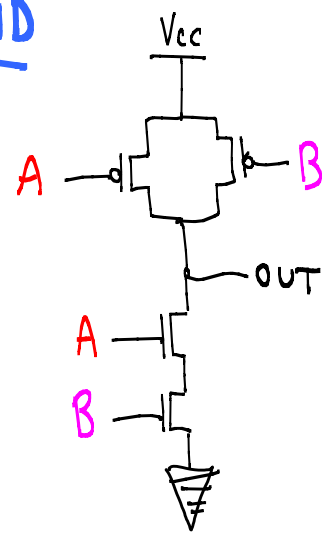

When $A=1$


$$Q = \text{NOT}(B)$$

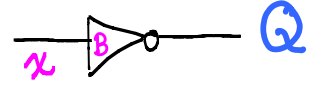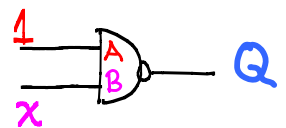

CIRCUITS W/ STATE

NOT-NOT circuit is stable in either of two states: BISTABLE element.

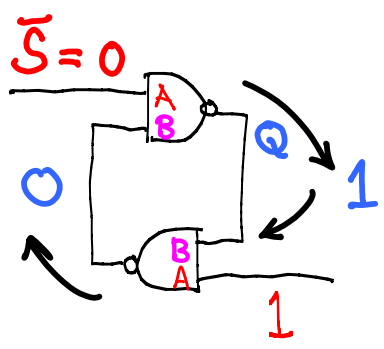
NAND-NAND circuit with both A inputs = 1, same as a NOT-NOT circuit.



NAND

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

$A=0 \Rightarrow Q=1$

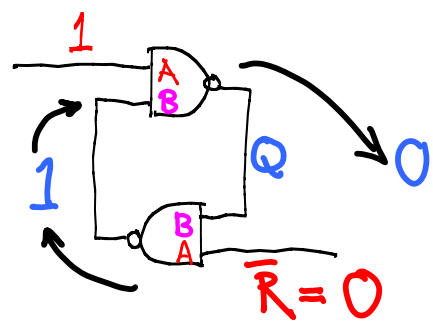

- $\bar{S} \quad \bar{R}$
- 1 1 stable
- 0 1 set $Q=1$
- 1 0 reset $Q=0$

