
 


# TM-implementation


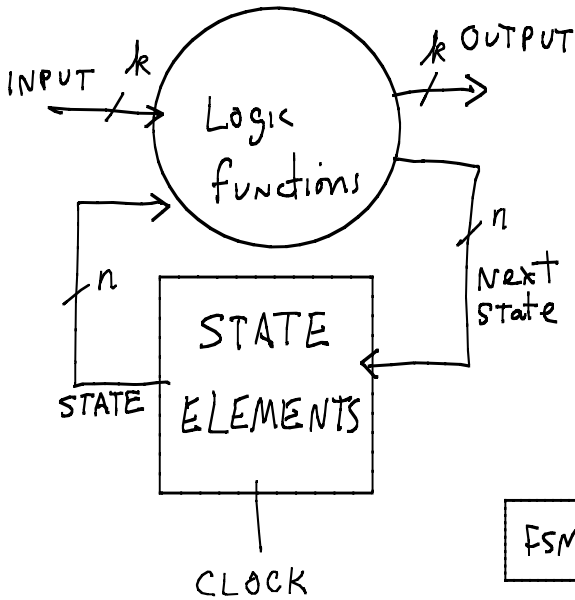


$k$ -bit symbols  
 e.g.,  $\Sigma = \{000, 001, \dots, 111\}$







FSM has input/output, but from/to where?

  
- (1) Other FSMs in same machine
- (2) Feedback loops



  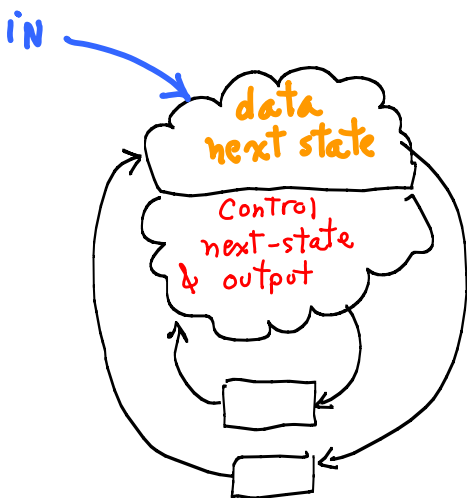 We like to separate state into two "types", control and data state.  
 Eg., some state elements are for "control" state, and some are for "data" state.




# Basic Sequential elements

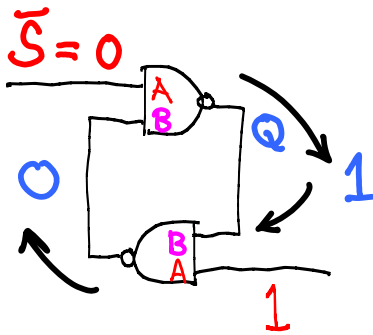



NAND

A	B	Q
0	0	1
0	1	1
1	0	0
1	1	0


$A = 0 \Rightarrow Q = 1$

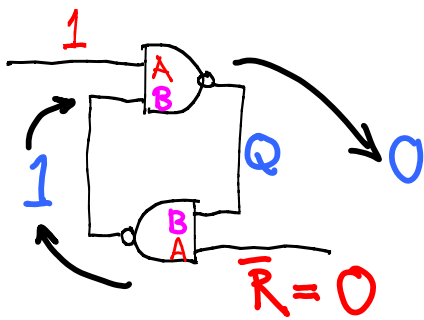

$\bar{S}$	$\bar{R}$	State
1	1	stable
0	1	set $Q = 1$
1	0	reset $Q = 0$

  


SR latch

 


a basic element  
for state

# CLOCKING, part 1: Gating D-Latch

 

 
$$\begin{array}{l} E=0 \\ \hline Y=0 \\ E=1 \\ \hline Y=A \end{array}$$





E	A	Y = E · A
0	0	0
0	1	0
1	0	0
1	1	1

E = 0 : input ignored

E = 1 : input passed

 

simplify

  


$$\begin{array}{l} D=0 : S=0, R=1 \rightarrow Q=0 \\ D=1 : S=1, R=0 \rightarrow Q=1 \end{array} \left. \vphantom{\begin{array}{l} D=0 \\ D=1 \end{array}} \right\} \begin{array}{l} \text{if} \\ E=1 \end{array}$$



# 2-phase clocking, D-FF



Fix Problem

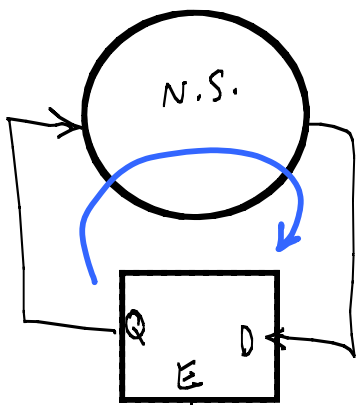


⇒

  



Transparent during this time, enough time to cause state change?  
 Make sure system never has an open feedback path.

⇒

 


# D-FF

D-FF

 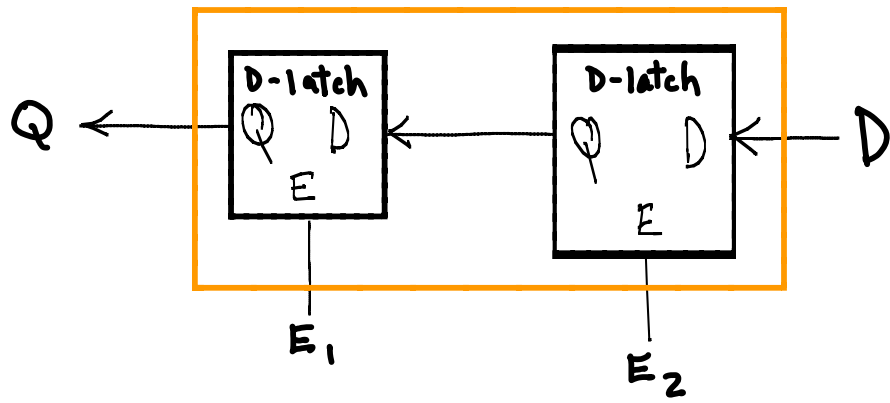


2-Phase Clocking

Separate signals for each latch's enable in FlipFlop. On breadboard we connect PHASE-1 to one data switch, PHASE-2 to another.

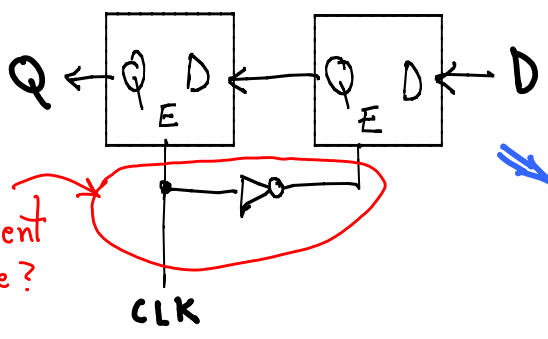

implement 2-phase?

 


flip-flop changes output state on rising clock edge



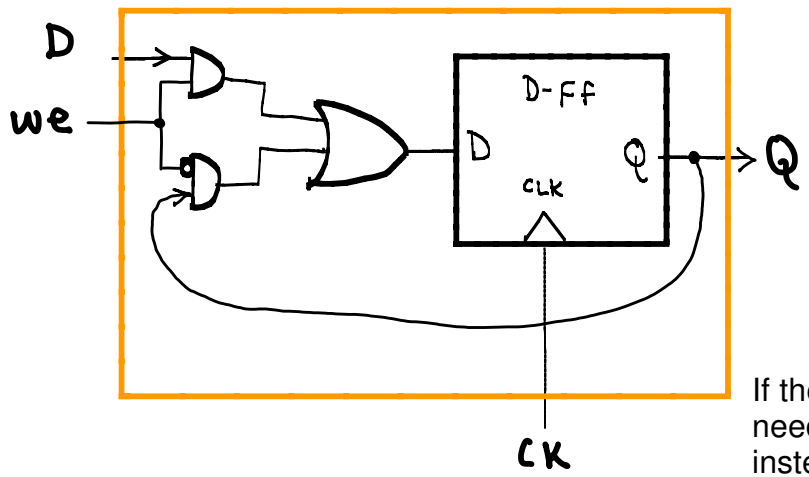
# D-FF, Pos. edge triggered w/enable

We often want to control whether or not the FF will be written into when the clock pulse arrives: add an "enable" input. When enable is 0, the current state is written back into the FF. Otherwise, D is written.



⇒

 

D-FF pos-edge triggered w/ write enable

If there is no feedback path from Q to D, we do not need a flip-flop, we can use a write-enable latch instead. Datapaths sometimes can use latches.


# PLA

Programmable Logic Array consists of two parts:

PLA, part 1.

A **decoder**, can be thought of as:

 - a) **activates exactly one output** from **input code**.
- b) **generates all minterms** from **input**.




PLA, Part 2.


A means of **OR'ing minterms** to produce function outputs.

Can **share the same minterms**: we can economically produce multiple functions at once.

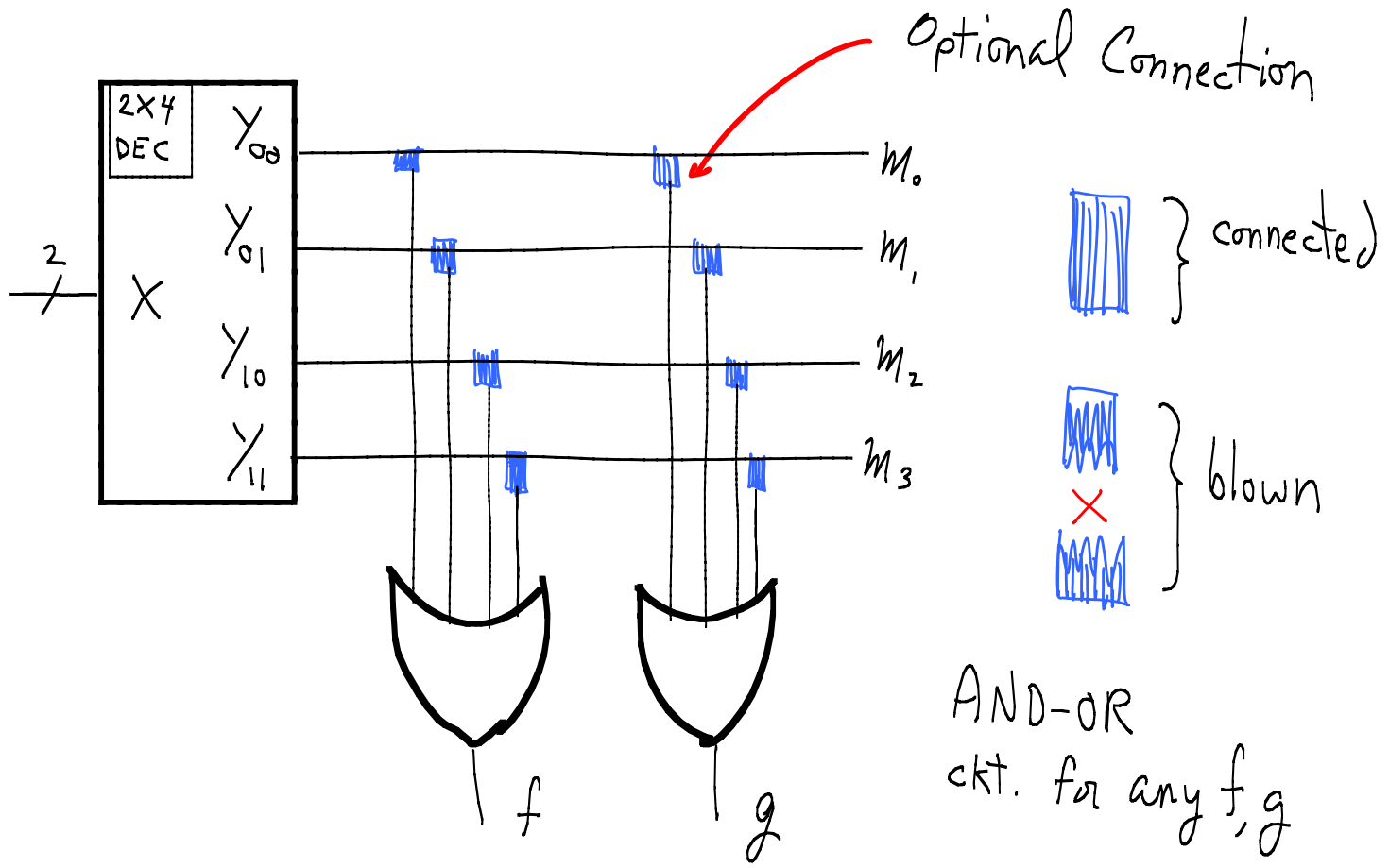Programmable: minterm **lines can be "blown" to disconnect** them: **selects minterms** included in the function.



MUX

 


"gating"

Control = 0 : m = 0


Control = 1 : m = data

control	data	m
0	0	0
1	0	0
1	1	1

 

1-bit  
(4-input) x (1 output)  
MUX



1-bit  
4x1 MUX

 


# IMPLEMENTING FUNCTIONS as ROM

Logic = ROM = MUX + bits

A	B	f
0	0	0
0	1	0
1	0	0
1	1	1

  


4 words,  
1-bit word  
= 4x1 ROM

 


## Bigger ROM

$2^2 \times 3$   
ROM

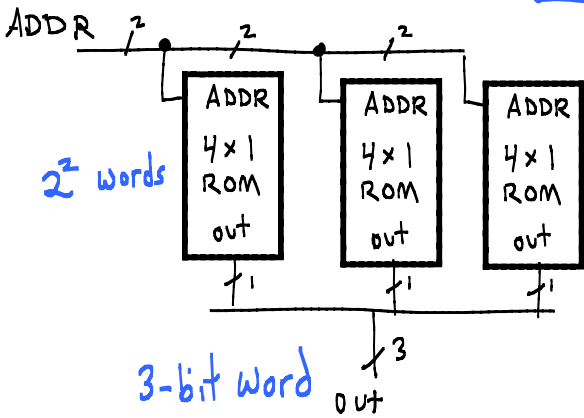

## FSM = ROM + STATE

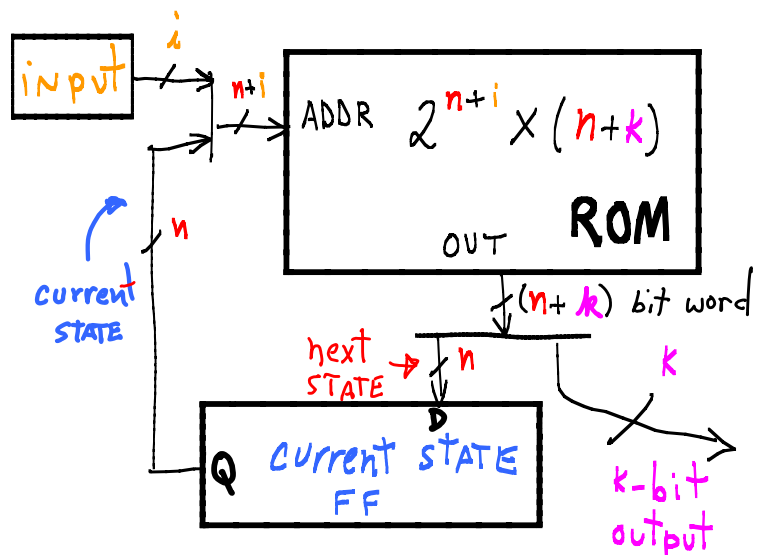

### FSM functions in ROM

- i** input bits to FSM
- k** output bits
- n** state bits ( $2^n$  states)

possible (state, input) pairs ==  $2^{(n+i)}$

====>  $2^{(n+i)}$  words in ROM  
n+i address bits

ROM word == (next-state, output)

====> (n + k)-bit word size

FSM in ROM ( n-bit state, i-bit input, k-bit FSM output )

(STATE, INPUT) is ROM address  
 n bits + i bits ==>  $2^{(n+i)}$  ROM locations

(NEXT-STATE, FSM-OUTPUT) is ROM output  
 n bits + k bits ==> (n+k) bits per location

==>  $2^{(n+i)}$  location by (n+k)-bit word ROM


ANY FSM (Mealy or Moore) can be built as a ROM

NOTE: A Moore machine's output depends only on state  
 ==> use n-bit addresses, one ROM location per state.


BUT, next-state depends on current-state+input. Encode part of next-state function in ROM word as NS-CODE, and use external logic to calculate next-state function:  $next-state = f( INPUT, NS-CODE )$ . This is what is done in the LC3's micro-coded controller.

Every possible FSM can be built as a ROM.

 ROM is very large since there is a word for every possible {state, input} combination.



address		ROM data word (row)	
STATE	INPUT	next-state	output
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	1

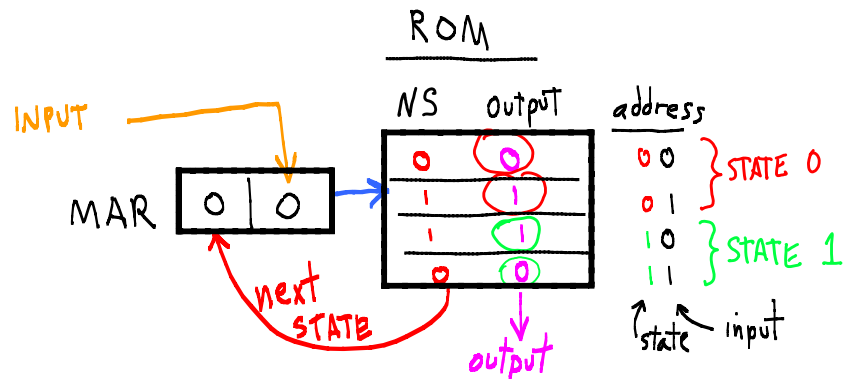


at clock tick:

- { current state, current input } captured
- output changes to match captured state/input

- Every state row has same output  
 ==> Moore Machine

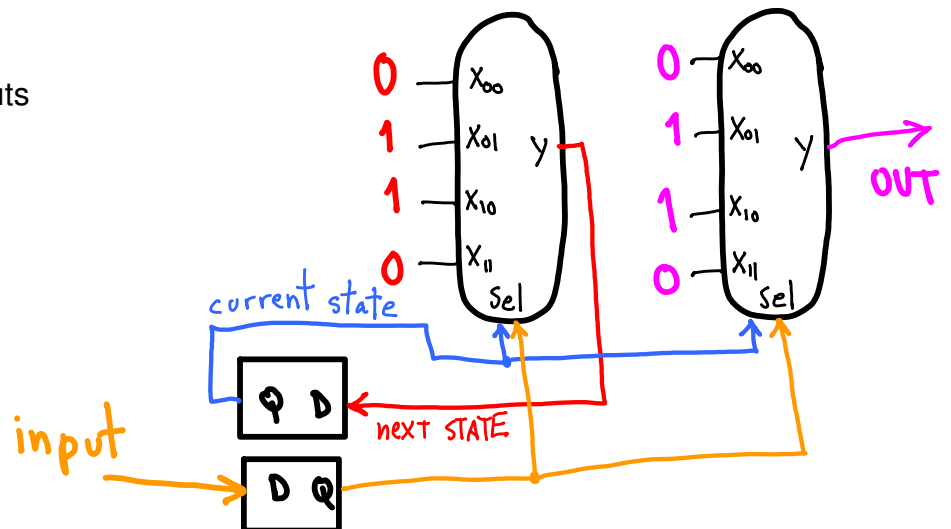- Rows for state S have differing outputs  
 ==> Mealy Machine.





We can enumerate all ROMs (and consequently all TMs/digital-computers):

Concatenate ROM content from all words:

address	content
00	00
01	11
10	11
11	00

==> 01111000

List all  $n = i = k = 1$  machines:  
FSM-0, FSM-1, ..., FSM-256

List all  $n = i = k = 2$  machines:  
FSM-257, FSM-258, ...

and so on.

