
 


Verilog

 1. Produce a Verilog file: `foo.v`
2. compile it for simulation: `iverilog foo.v`
3. simulate system: `vvp a.out > testResult.txt` → output to file
4. see what happened: `vi testResult.txt` → see content


Discrete Event Simulation

- create an event which occurs at time t
- check what that event will cause to happen:
 - create new events at t (zero delay)
 - create new events at $t + d$ (d delay)



Event Processing
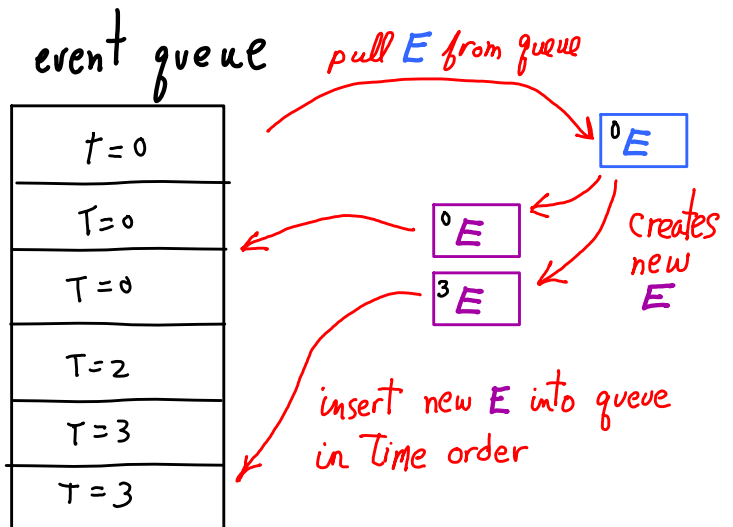
```
WHILE(1)
  --- get earliest event E from queue
  --- E creates new events, insert into queue
  --- delete E
end_WHILE
```





Q. Which $t=0$ event is processed first?

Verilog statements, making things happen / creating events

Only two types of "action" statements:

- initial
- always

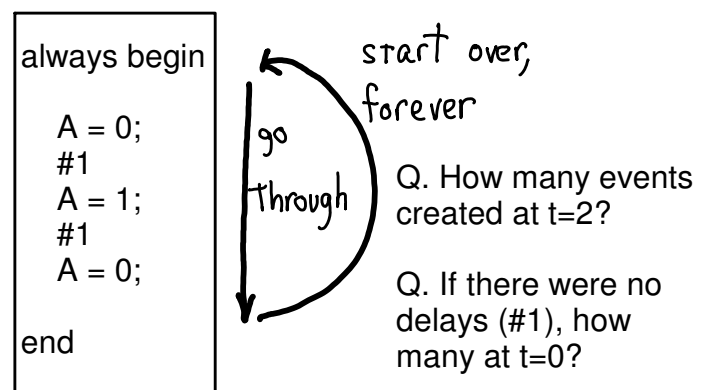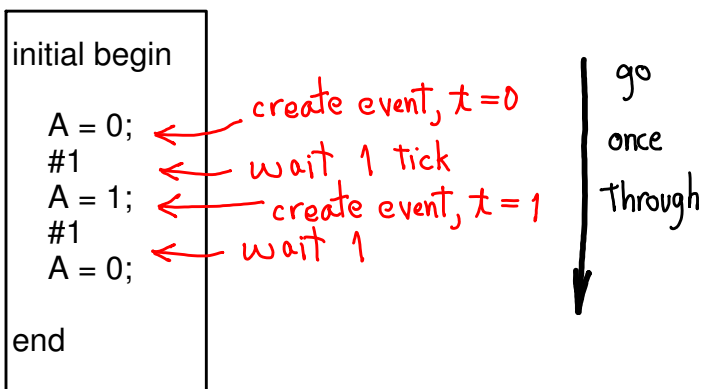all initial and always statements run in parallel
They all start creating events at $t=0$



```

reg clock;

initial begin
  clock = 0;
end

always begin
  #10 clock = ~ clock;
end

```

*This is a free running clock.
 Starts = 0 at $t=0$.
 Switches to 1 at $t=10$,
 back to 0 at $t=20$,
 ...
 forever*

```

always @( clock ) begin
  $display( "time=%d", $time );
  $display( "clock = %b", clock );
end

```

*This waits for clock to change.
 Then creates two events to call
 system functions \$display + \$time.*

Q. At what simulation time will the first \$display occur? The second? The third? Which \$display runs first?

Signal Values

*All wires are x or z
 until some event changes it
 to 1 or 0.*

Verilog knows three signal values:


- 0, logic 0 (~ GND)
- 1, logic 1 (~ +5v for us)
- x, unknown logic value; wire is driven, but cannot determine value.
- z, high-impedance, nothing driving the wire to a specific value.

```

initial begin
  A = 0;
  $display( "A = %b", A );
  #5
  $display( "time=%0d", $time );
  ...


```

 *what value makes sense for
 y in each case?*



Q. What value will \$display show for A?


what value makes sense for y?

 

Verilog reasons it this way:

$$\text{NOT}(0) == 1 == \text{NOT}(0)$$



 
Which, works out electrically as well: $y = 1$.



$$\Delta V \text{ across } R = i R = 0 R = 0$$

$$y = +5v$$

what value makes sense for y?

   

As a logical statement, the NOT-NOT circuit says this,

NOT(0) == NOT(1)

This does not make sense, mathematically.

Electrically, the value of y might be a perfectly good logic value near 0v. But that depends on the device's characteristics (see at right).

Verilog will simply say it cannot guess: y = x.

actually, $i_2 = i_1 + i_1 = 2i_1$

$$\Delta V_2 = i_2 R_2 = 2i_1 R_2$$

$$i_1 = (5v - \Delta V_2) / R_1$$

$$\Delta V_2 = (5v - \Delta V_2) 2R_2 / R_1$$

$$\Rightarrow \Delta V_2 = 10R_2 / (R_1 + 2R_2)$$

if $R_2 \ll R_1$, then $\approx 0v$
but, what happens in real device?
measure it!

How to stop the simulation:

```
initial begin
    #1000 $finish;
end
```

This runs in parallel w/ other statements.
It waits until $t = 1000$, then calls \$finish

Other Verilog Language Elements


- Definitions, e.g., reg A, assign, ...
- Helper code, helps you write actions using less text
integer, for, ...
- Behavioral modeling
while, if, then, ...

documentation:
see projects/LC3trunk/docs/verilog
or google "verilog tutorial"


Work Flow

Electric Window


shell commandline

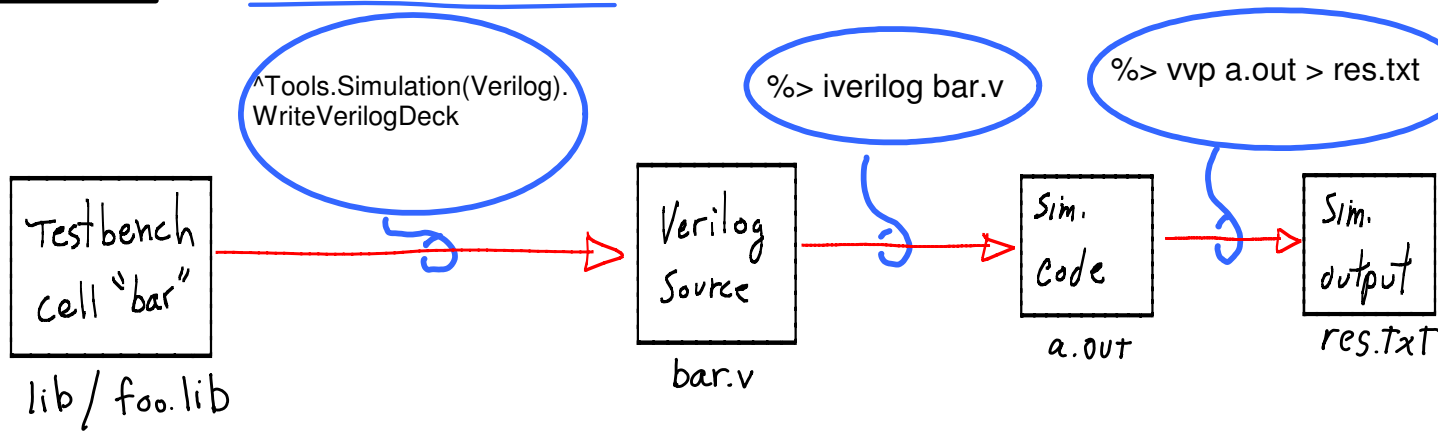

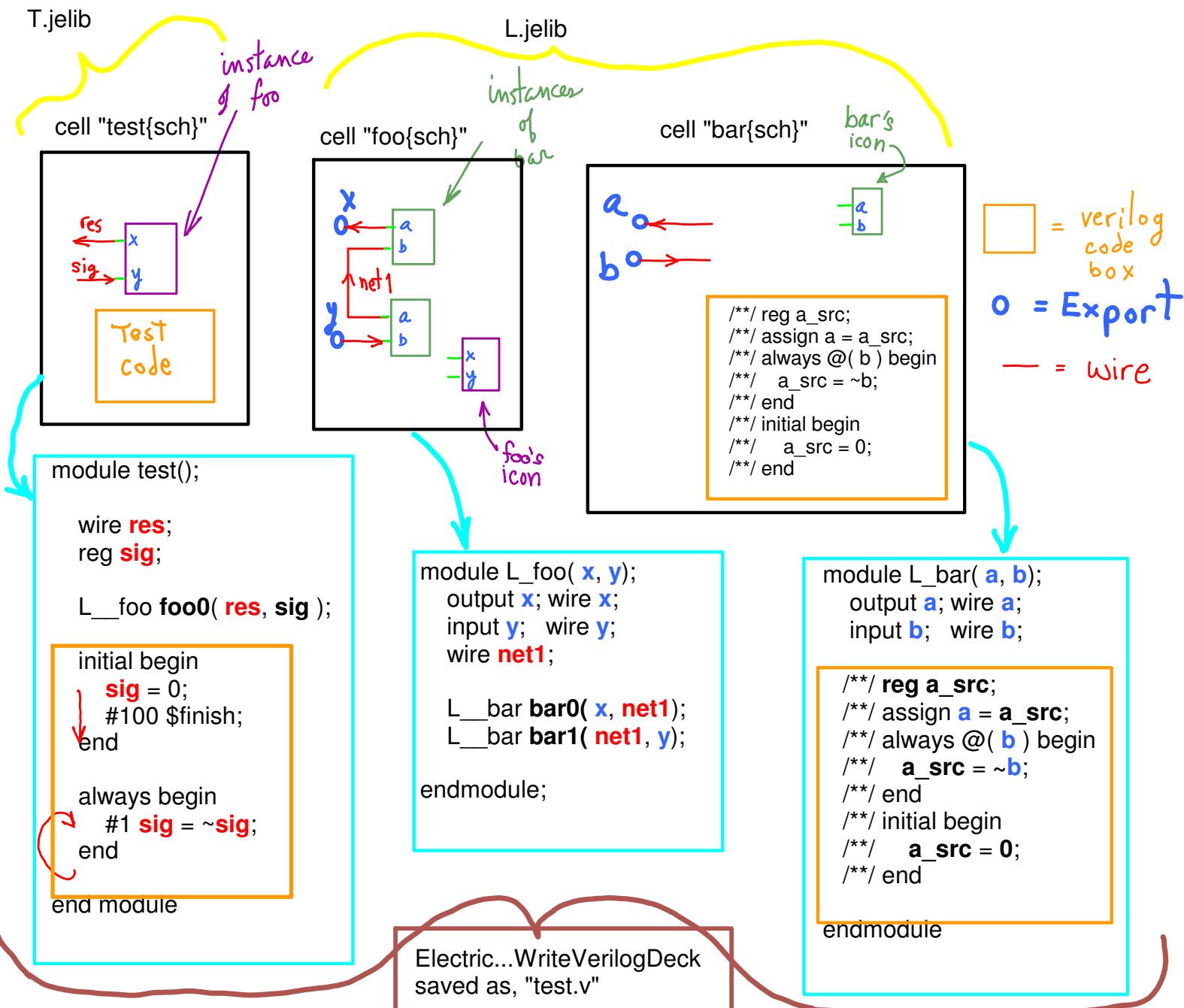Verilog Code Structure from Electric Cells



cell "add16 {sch}"

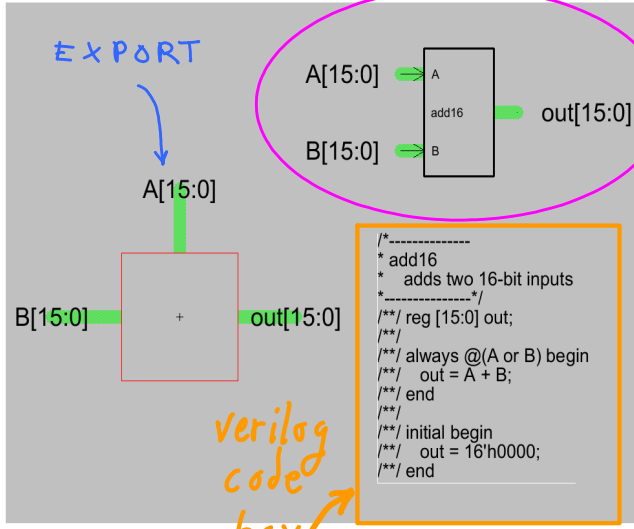

icon "add16 {ic}"

add16.v
Electric Tools Simulation Write Verilog

```

/* Verilog for cell 'parts:add16{sch}'
from library 'parts'*/
  
```

```

module add16(A, B, out);
input [15:0] A;
input [15:0] B;
output [15:0] out;
  
```

```

/* user-specified Verilog code */
/*-----*/
  
```


```

* add16
* adds two 16-bit inputs
*-----*/
/**/ reg [15:0] out;
/**/
/**/ always @(A or B) begin
/**/   out = A + B;
/**/ end
/**/
/**/ initial begin
/**/   out = 16'h0000;
/**/ end
  
```

```
endmodule /* add16 */
```

Write Verilog

cell "add16_test{sch}"

 

```

/*-----*/
* Drive adder inputs
*-----*/
/**/ reg[15:0] Asrc;
/**/ reg[15:0] Bsrc;
/**/ assign A = Asrc;
/**/ assign B = Bsrc;
/**/ initial begin
/**/   #0 Asrc = 16'h0000;
/**/   #0 Bsrc = 16'h0000;
/**/   #7000 $finish;
/**/ end
/**/ always begin
/**/   #1 $display(" %d + %d = %d", Asrc, Bsrc, out);
/**/   #1 Bsrc = Bsrc + 7;
/**/   #1 $display(" %d + %d = %d", Asrc, Bsrc, out);
/**/   #1 Asrc = Asrc + 17;
/**/ end
  
```

```

module parts__add16(A, B, out);
input [15:0] A;
input [15:0] B;
output [15:0] out;
  
```

```

/* user-specified Verilog code */
/*-----*/
* add16
* adds two 16-bit inputs
*-----*/
/**/ reg [15:0] out;
...
/**/ end
endmodule /* parts__add16 */
  
```

```
module add16_test();
```

```

wire [15:0] A;
wire [15:0] B;
wire [15:0] out;
  
```

```

/* user-specified Verilog code */
/*-----*/
* Drive adder inputs
*-----*/
/**/ reg[15:0] Asrc;
...
/**/ end
  
```

```

parts__add16 ADDER(.A(A[15:0]), .B(B[15:0]), .out(out[15:0]));
endmodule /* add16_test */
  
```

def'n of add16

add16_test's code

Top-level, no args

BUS

instance of add16


Export BUS

Structural vs. Behavioral

Structural — wires and gates: **verilog wire, reg, and, or, buff, ... (other primitives)**

Behavioral — description of behavior: **verilog if(), while(), case(), ... (other constructs)**

Gate-level Modeling

 

STRUCTURAL

via
"primitives"

```
module foo ( y, x, b );
    input x, b;
    output y;
    wire y, x, a, b;

    and and_0( y, x, a );
    or or_0( a, b, x );
endmodule
```

Data Flow

via
"continuous assignment"

```
module foo ( y, x, b );
    input x, b;
    output y;
    wire y, x, b;

    assign y = (x & (x | b));
endmodule
```

Delays

--- We can specify delays for devices and wires (modeling real life). But then we have to check circuit timing issues.

--- We can have 0 delay devices (math/logic). But then we don't know how things actually occur.

--- If you cannot be sure how events will be ordered, put in a delay.

Q. Will the \$display() and \$write() events occur before or after signal changes?

--- This will make you more certain,
#1 \$display();

```
module f();
    reg A, B, C;

    initial begin
        #2 A = 0;
        #2 B = 0;
        #2 C = 0;
        #2 $finish;
    end


    always @(A or B or C) begin
        $display("--- t=%0d ---", $time);
        $write("A=%b ", A);
        $write("B=%b ", B);
        $write("B=%b ", B);
        $write("\n");
    end
endmodule
```

Q. Trace all the output events, showing what is printed.

at what time do these events occur?
Are they ordered, i.e., blocking?

Ordering Events

 $c = 0$
 $a = 0$
 event: $c \leftarrow 1$



blocking assignment

```

input c;
wire c;
output a, b;
reg a, b;
    
```

```

initial begin
    a = 0;
    b = 0;
end
always @(c) begin
    a = c;
    b = a & c;
end
    
```

$c \leftarrow 1$
 $a \leftarrow 1$
 $b \leftarrow 1$

a's new value used for b.

RHS evaluated in order, after preceding LHS assignment

non-blocking assignment

```

input c;
wire c;
output a, b;
reg a, b;
    
```

```

initial begin
    a = 0;
    b = 0;
end
always @(c) begin
    a <= c;
    b <= a & c;
end
    
```

$c \leftarrow 1$
 $a \leftarrow 1$
 $b \leftarrow 0$

a's old value used for b

RHS evaluated in parallel, globally, before LHS assignment

Which is the correct, i.e., more realistic?

Depends on what we are modeling.

USE `<=` (non-blocking, for parallel occurring assignments)


USE `=` (blocking or procedural, for behavioral modeling)

BUSSES, Arrays

```
wire [7:0] busA;
wire [3:0] busB;
reg Asrc;
assign busA = Asrc;
assign busB = A[7:4];
```

```
initial begin
    Asrc = 8'd255;
end
//-- busAsrc = 8'hFF;
//-- busAsrc = 8'b11111111;
```

 not a wire/bus, art work only, "bus breakout," connect by name.



wire order assumed

Expressing multi-wire signal values

size(*bits)	format	number	interpret number as an expression in:
8	d	255	(d = decimal) (h = hex) (b = binary)
	h	FF	
	b	1111 1111	

Combining busses

```
input [3:0] a, b;
output [9:0] y;
assign y = { 3 { a[1:0] }, b[3:2], 2'b00 };
```

(duplicate 3 times) and (concatenate)

{ a[1], a[0], a[1], a[0], a[1], a[0], b[3], b[2], 1'b0, 1'b0 }



$$\begin{aligned}
 \text{hex } 2D &= 2 \times 16^1 + D \times 16^0 \\
 &= (0010) \times 2^4 + (1101) \times (2^4)^0 \\
 &= 00100000 + 1101 \\
 &= 00101101 \text{ binary}
 \end{aligned}$$

⇒ easy to convert hex ↔ binary

4-bit numbers

decimal	hex	binary
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
10	A	1010
11	B	1011
12	C	1100
13	D	1101
14	E	1110
15	F	1111

definitions, parameters

```

`define BUSWIDTH 16
reg [(`BUSWIDTH - 1) : 0] busA;

```

macro substitution.

Equivalently: `reg [15 : 0] busA;`

(put defs in a header file and include it) `include header.vh`
 (ie., back single quote)

Parameters

```

module F();
  parameter WIDTH = 8;
  reg [ (WIDTH - 1) : 0 ] busA;
  ...
endmodule

```

Seems redundant, but here's how we use it.

```

module H();
  defparam foo.WIDTH = 32;
  F foo;

```

override parameter explicitly affects following def


or

```
F #(16) bar;
```

implicit override: by order parameters were defined. E.g., `#(10, 16, 2)` means 1st param gets 10, 2nd gets 16, 3rd gets 2

Arrays

```
reg [7:0] regWords [15:0];
```

 

e.g.,

```

regWords[1] = 8'b01010000;
regWords[1][0] = 1'b1;

```

Q. What's in `regWords[1]` now?

Tasks = methods

```

module memory(...);
  ...
  reg [7:0] regWords [15:0];
  integer i;

  task clear;
  begin
    for (i = 0; i < 15; i = i + 1)
    begin
      regWords[i] = 8'd0;
    end
  end
endtask
endmodule

```

Task

"helper" code = shorthand

otherwise, 16 assignments

```

module top ();
  memory mem;
  initial begin
    mem.clear;
    mem.regWords[0] = 8'b000111;
  end
endmodule

```

invoke Task

Naming in hierarchy

`name1.name2.name3`

top-level instance name instance inside name1 instance inside name2

Pre-defined Tasks

`$display("...", ...);`

— has eoln

`$write("...", ...);`

— no eoln

`$time;`

— simulation time step

`$monitor("...", ...);`

`$strobe(...);`

} — like `$display`, but w/ implicit "always @(x)"
(broken?)

`$fopen(...);`

`$fwrite(...);`

} — uses Multi-Channel Descriptor: multiple files,
or use a File-Descriptor: 1 file

`$readmemb("filename", dataArray);`

— (reads data into model,
text file contains binary notation)

`$readmemh("filename", dataArray, ...);`

— (text file contains hex notation)

`$dump(...);`

optional: Begin/end indices (both binary and hex)

— dumps every signal @ every change, use w/ GTK wave

`$stop;`

— goes to interactive mode, then enter "`$finish`" to quit.

(`ctrl-c` during simulation also goes to interactive mode.)

`$finish;`

— quit simulation

More Signal propagation delays

*2 A = B } B sampled and A changes both at $t+2$

A = *2 B } B sampled at t ,
A changes at $t+2$

and *(3,2) and 1(y, A, B) } A or B changes, causing Y change Y changes @

↑ implicit set parameters

Y → 1	t+3
Y → 0	t+2
Y → 3	t + min(3,2)

wire A
assign *2 A = B & C } B + C sampled at t
A changes at $t+2$
(unless b, c change → canceled)

wire *2 A;
assign A = B & C } wire A takes 2 ticks to see (B&C),
same as above.

always @(posedge clk) begin
 a = b;
 @(negedge clk)
 a = ~b;
 @(c or clk)
 a = 0;
end

} What's in "a" if c doesn't change?

How many times does c change?

always begin

```
wait( a );
#1
c = ~c;
```

end

only waits if
 $a \neq 1$ (0,x,3)
 \cong wait-until (a==1)

initial begin

```
c = 0;
a = 0;
#3
a = 1;
#3
a = 0;
#1
$finish;
```

end

→ easy way to find the answer:

always @(c) begin

```
*1 $display ("%b", c);
end
```

```
always @( posedge clk ) Q1 = D;
```

```
always @( posedge clk ) Q2 = Q1;
```


initial begin

```
@( posedge clk ) D = 0;
```

```
@( negedge clk ) D = 1;
```

end

what happens to Q1, Q2?

 

Other language elements

---- Looping (forever, while, for)

These can appear inside an "initial" or "always", and can thus start at times other than 0. Conditionals are T if they evaluate to 1, F if they evaluate to 0, x, or z. "Forever" is the same as "while(1)".

---- Control (fork, join)

Creates parallel event streams that synchronize at the "join": all enclosed "begin-end" blocks run in parallel and the last to finish exits the "fork-join". E.g.,

```
fork
  begin ... end
  begin ... end
join
```