
 


# TM Implementation

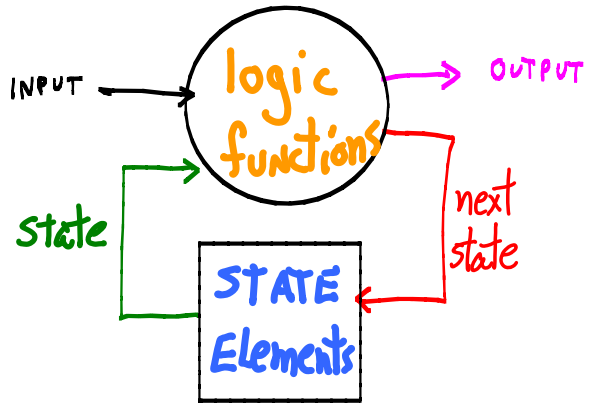

implement




To build any TM, WE NEED:

- (1.) FSM:
  - state
  - logic functions (output and next-state)
- (2.) Tape: methods to R/W symbols, we'll use registers (RAM).
- (3.) Symbol set = a set of fixed length bit strings, e.g.,
  - S = {0,1} (2 symbols)
  - S = {00, 01, 10, 11} (4 symbols)
  - S = {000, 001, 010, 011, 100, 101, 110, 111} (8 symbols)

## Build FSM

## even-odd parity

 

{symbols} = {0, 1}

{states} = {A, B}  $\xrightarrow{\text{encode}}$  {0, 1}

functions

OUT: {states} x {symbols}  $\rightarrow$  {symbols}

next-state: {states} x {symbols}  $\rightarrow$  {states}

(A, 0) $\implies$ 0	$\xrightarrow{\text{encode}}$	(0, 0) $\implies$ 0
(A, 1) $\implies$ 1		(0, 1) $\implies$ 1
(B, 0) $\implies$ 1		(1, 0) $\implies$ 1
(B, 1) $\implies$ 0		(1, 1) $\implies$ 0

(A, 0) $\implies$ A	$\xrightarrow{\text{encode}}$	(0, 0) $\implies$ 0
(A, 1) $\implies$ B		(0, 1) $\implies$ 1
(B, 0) $\implies$ B		(1, 0) $\implies$ 1
(B, 1) $\implies$ A		(1, 1) $\implies$ 0

Two things to build to implement a FSM:

1. Boolean functions
2. State elements

Our Computer/Simulator is a FSM.  
Our simulated machines are FSMs, too.

Boolean functions

current STATE  $\uparrow$   
symbol read  $\uparrow$   
next state  $\uparrow$

**Turing Complete/Universal** (can simulate any TM) we need:

- a **Language** to describe any TM,
- a **Simulator** that understands that language.

We need to describe arbitrary TMs so that our computer/simulator can execute/simulate them.

We can build the machines physically. We need a language to describe them as well.

**LANGUAGE**

Our description language must be able to describe:


- Arbitrary **set of states**, including regs (= vars)
- Arbitrary **set of symbols**
- Arbitrary **branching** (via binary trees)
- **RW to tape**
- Arbitrary **functions** (next-state, output)

**UTM/simulator/computer**

A physical computer/simulator has to be able to do only a small number of steps to execute/simulate a program/description of some TM M.

- know M's **current state** (PC, vars)
- **read M's tape** (LDR)
- compute M's **OUT function**:  
ADD, AND, NOT ...
- compute M's **next-state function**:  
ADD, AND, NOT ...
- **write M's tape** (STR)
- **change M's state**  
PC++, JMP, BR
- STR ==> new data state (vars)
- STR ==> new control state

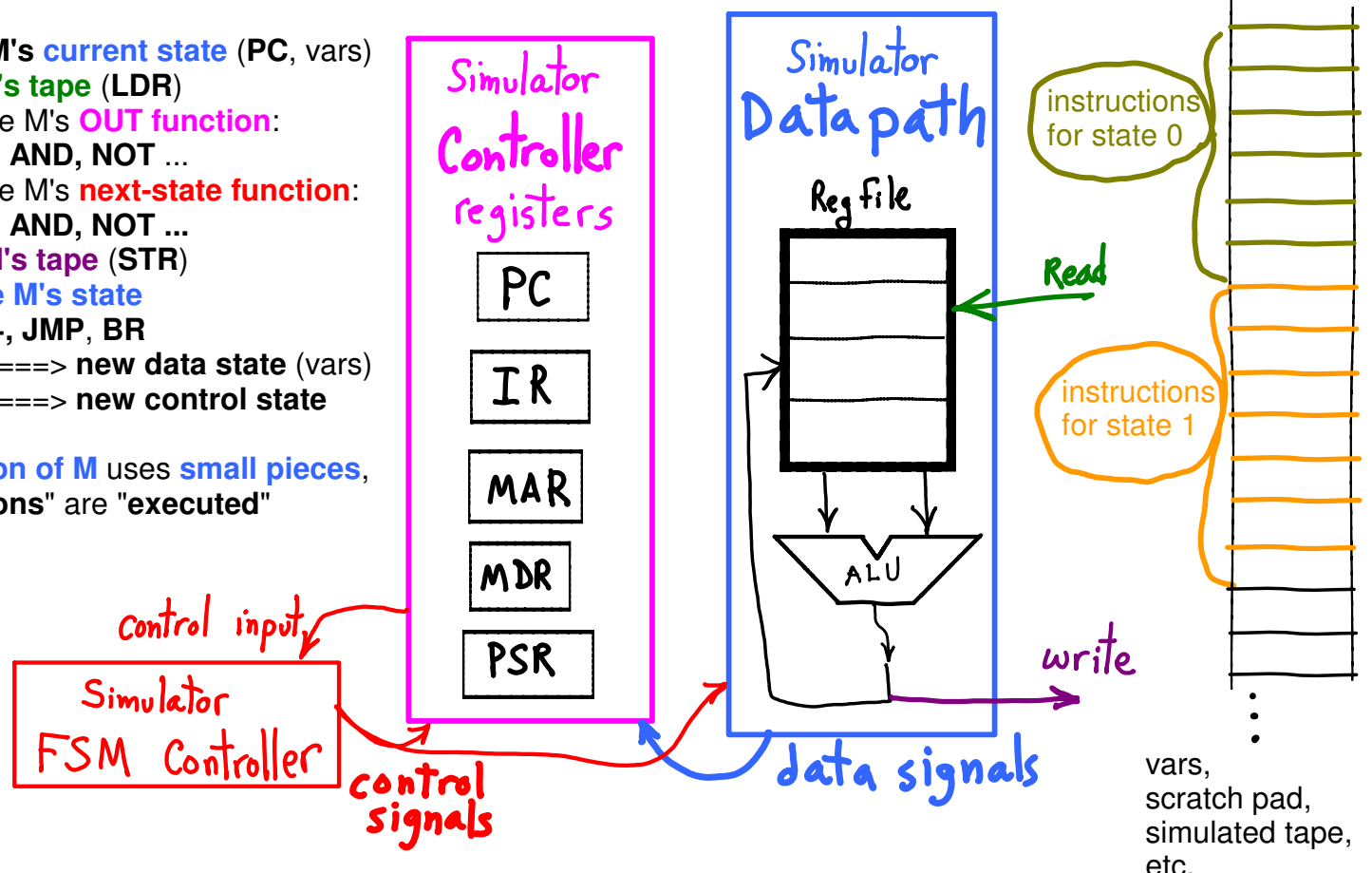Description of M uses **small pieces**, "instructions" are "executed"




**FSM Controller** uses **registers** (e.g., PC) to remember:

- M's **state** (control + data states)
- **symbols read** (RegFile)
- **symbols to write** (RegFile)
- **step of simulation** (UTM's controller's state)
- **partial steps of function evaluations** (next-state, output)  
data registers, PSR, on tape, ...

# STATE ELEMENTS

pos. edge-triggered  
FF

Problem:  
*Katy bar  
the door*

 

Feedback loop:  
state change,  
NS change,  
state change,  
NS change, ...

State changes w/o control.


We want coordination w/  
input data.

When the input is ready,  
Then allow a state change.


Input has to be stable for a  
minimum time.

Current state has to remain  
stable to get correct next  
state.


①

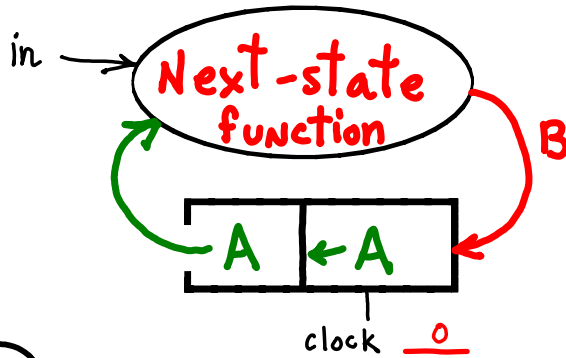

②

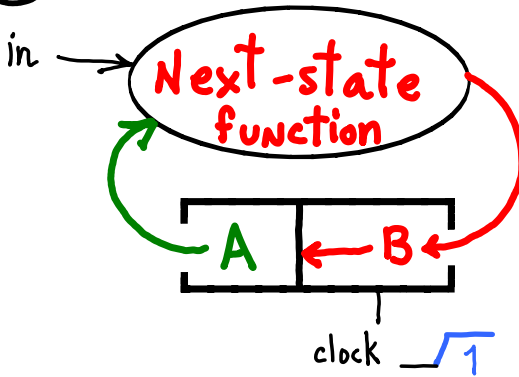

③

 

## Solution

Never allow a complete cycle path.

Break path at the state element.

1. Current state = **A**


2. Allow NS signal **B** in (read/sample  
state element input).

3. Then, close the barn door.

**B is captured**, cannot be changed  
by changes in NS function output.

input "sampled"  
"latched"


4

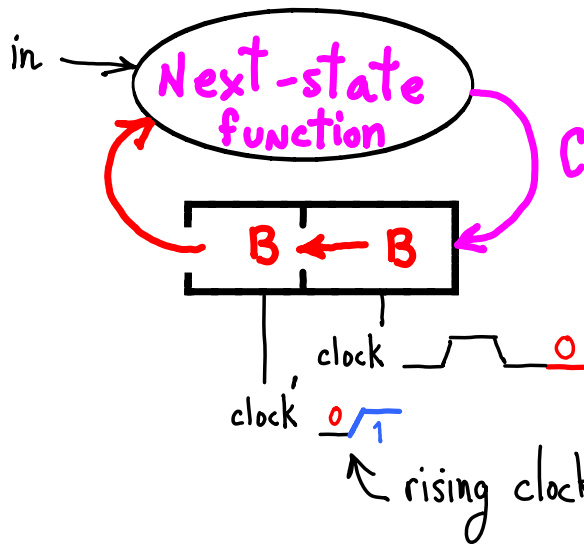

Let the NS out:  
open the output side barn door,  
== change current state to **B**

NS function immediately responds with  
new next-state **C**.

5

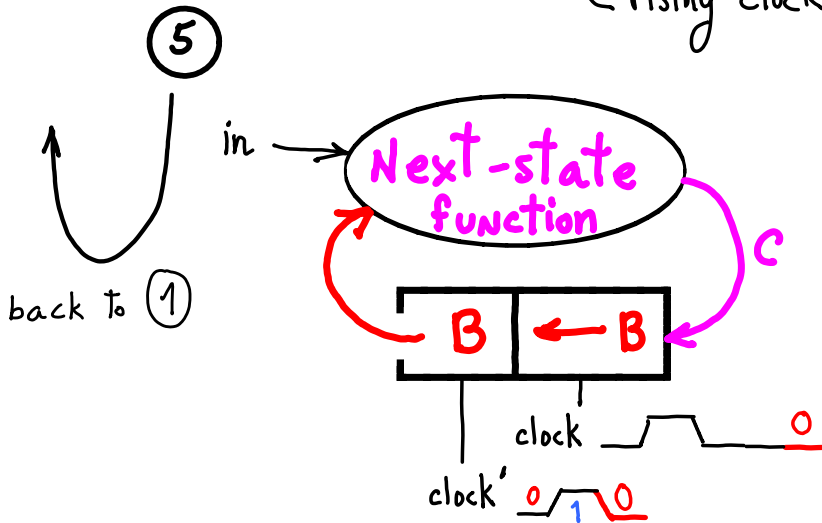


Close the output side's input door.

New state **B** is latched.

Path is never a complete cycle.

 This is what we need for implementing **STATE**:  
a D-FF register.



Note:

We add a "write-enable" because sometimes we need to choose  
whether or not the register will change its value.

So far, for FSMs, our D-FFs are always write-enabled, we==1.

# Describing Functions

## Two Ways to Specify a Function $f(x)$

(1)

Describe how to evaluate  $f(x)$ :

E.g.

$$f(x) = 2x$$

(given any value  $x$ )

(2)


Show a table of values of  $f(x)$ :

E.g.

$x$	$f(x)$
0	1
1	0

(for every value of  $x$ )
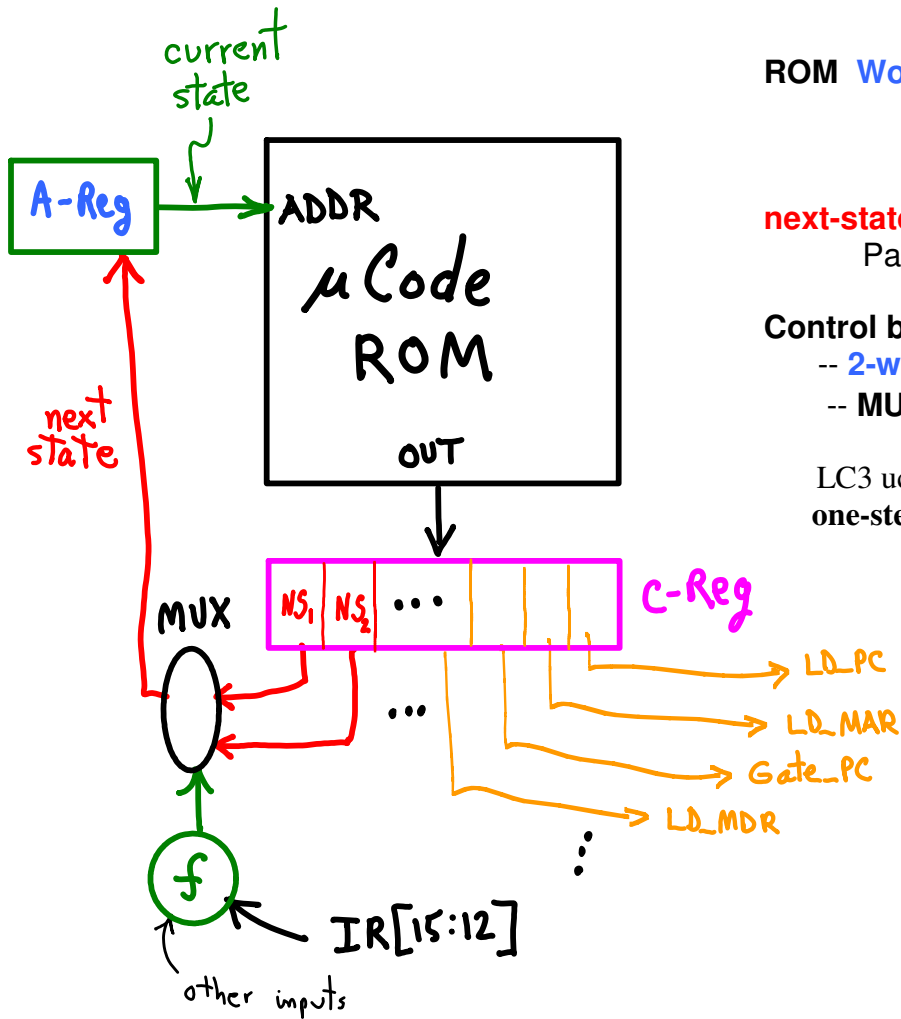
# (B) microcoded controller next-state & output functions



**A-Reg** == controller's **current state**  
addresses **uCode ROM**  
gives memory **word at output**


**ROM Word** == datapath **control bits**  
**C-Reg** has **current control word**  
**controls datapath**

**next-state fields of C-Reg**  
Part of Controller's **next-state** function

**Control branching** (the rest of **next-state** function)  
-- 2-way, **NS1** or **NS2**  
--  $MUX.select = f(STATE, IR, \dots)$

LC3 ucode branching also includes  
**one-step, 16-way branching (DECODE)**.

As a general FSM,  
it looks like this,

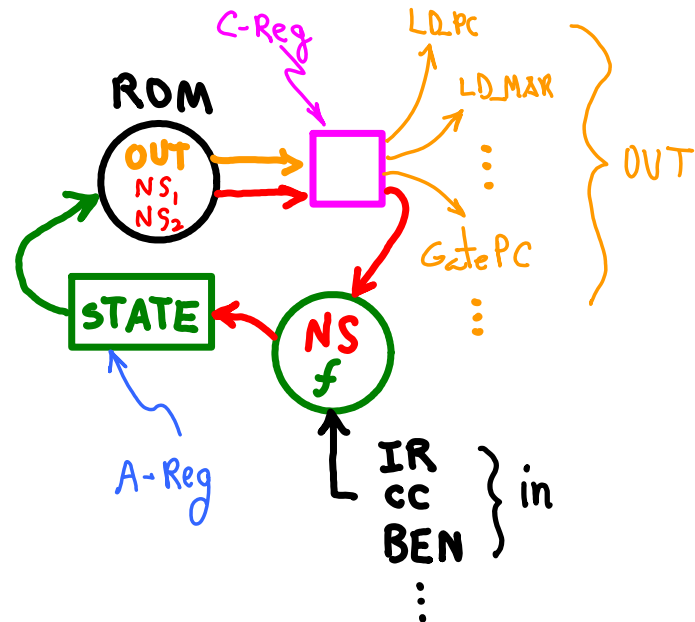

## Advantages of ucode controller:

- easier to **change**
- easier to **figure out**
- easier to **expand**  
install bigger ROM.

## Advantages of "random logic" controller:

- **faster**
- **smaller** (?)
- **distributed** throughout machine

Caveat: The C-Reg is just to make the picture clearer, it doesn't actually exist in LC3. Instead, the ROM's outputs go directly to control inputs.


Suppose we have,

- 1-bit state elements
- 1-bit function elements


e.g., mod-3 machine

HOW do we put them together to implement a FSM M?

 We need to encode the states of M in bits. We get boolean functions for next-state function (and output function).




1-hot encoding 3 state elements

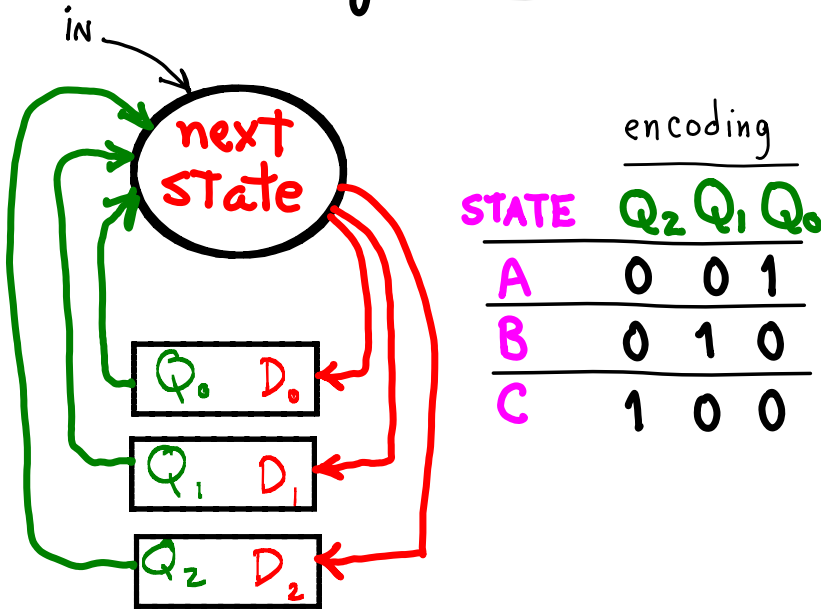

STATE	encoding		
	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
A	0	0	1
B	0	1	0
C	1	0	0

binary encoding 2 state elements

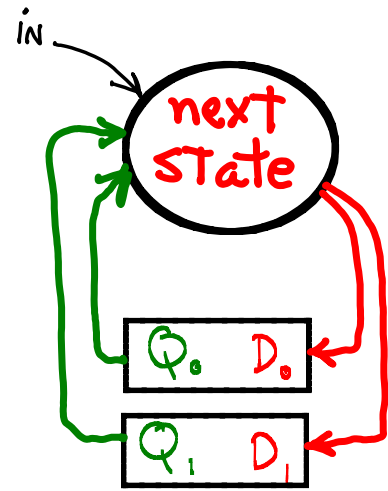

STATE	encoding	
	Q <sub>1</sub>	Q <sub>0</sub>
A	0	0
B	0	1
C	1	0

The next-state function as a table:

input	$x$			current state		$f(x)$			next state
	IN	Q <sub>2</sub>	Q <sub>1</sub>			Q <sub>0</sub>	D <sub>2</sub>	D <sub>1</sub>	
0	0	0	1	(A)	0	0	1	(A)	
1	0	0	1	(A)	0	1	0	(B)	
0	0	1	0	(B)	0	1	0	(B)	
1	0	1	0	(B)	1	0	0	(C)	
0	1	0	0	(C)	1	0	0	(C)	
1	1	0	0	(C)	0	0	1	(A)	
*	*	*	*		X	X	X		

input	$x$		current state		$f(x)$		next state
	IN	Q <sub>1</sub>			Q <sub>0</sub>	D <sub>1</sub>	
0	0	0	(A)	0	0	(A)	
1	0	0	(A)	0	1	(B)	
0	0	1	(B)	0	1	(B)	
1	0	1	(B)	1	0	(C)	
0	1	0	(C)	1	0	(C)	
1	1	0	(C)	0	0	(A)	
*	*	*		X	X		

\* rows that cannot be reached. X is for don't care, either 0 or 1.

\* rows cannot be reached. X is for don't care: either 0 or 1.

**IF** we have a **universal language** (able to describe **any TM**)

**All we need** to know is **How To Build**:

--- **1-bit state elements**?

--- **1-bit functions**?

