

Boolean Equivalence

Are these the same?

A	B	C	$(A \cdot B) \cdot C$
0	0	0	
0	0	1	
0	1	0	?
0	1	1	?
1	0	0	
1	0	1	
1	1	0	
1	1	1	

A	B	C	$A \cdot (B \cdot C)$
0	0	0	
0	0	1	
0	1	0	?
0	1	1	?
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Do they have exactly the same output values for exactly the same input values? Check ALL input values.

If so, equivalent: $(A \cdot B) \cdot C = A \cdot (B \cdot C)$

Basic Algebraic Properties

Proof by truth table.

equivalent functions

logical constant = TRUE for all inputs.

$1 \cdot P = P$

proof

{	P	$1 \cdot P$	=	P	P	}
	0	0		0	0	
	1	1		1	1	

$0 \cdot P = 0$

$P \cdot P = P$

proof

{	P	$P \cdot P$	=	P	P	}
	0	0		0	0	
	1	1		1	1	

$P \cdot \bar{P} = 0$

proof

{	P	$P \cdot \bar{P}$	}
	0	0	
	1	0	} always 0

$A \cdot B = B \cdot A$

$(A \cdot B) \cdot C = A \cdot (B \cdot C)$

Handy tricks: DeMorgan's Laws and Duality (Aside: can you prove Duality?)


- (1) prove algebraic properties or do algebraic manipulations,
- (2) convert one type of logic gate to another.

DeMorgan's Laws


$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

A	B	$\overline{A} + \overline{B}$
0	0	1
0	1	1
1	0	1
1	1	0

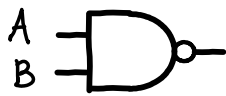


=

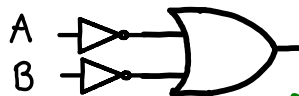

DUAL



=

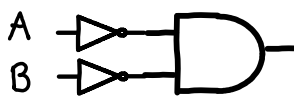

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

DUALITY

$\left. \begin{matrix} \cdot \\ + \\ 0 \\ 1 \end{matrix} \right\} \rightarrow \left. \begin{matrix} + \\ \cdot \\ 1 \\ 0 \end{matrix} \right\}$
 starting with an identity, gives an identity.

$$1 \cdot P = P \rightarrow 0 + P = P$$

$$0 \cdot P = 0 \rightarrow 1 + P = 1$$

$$(A + B)C = AC + BC$$

↓ dual

$$AB + C = (A + C)(B + C)$$

Can We Build ANY k-input function? YES ==> OR k-input minterm functions.

A	B	C	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

=

A	B	C	m_0
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

+

A	B	C	m_3
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

+

A	B	C	m_6
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$$f(A, B, C) = m_0(A, B, C) + m_3(A, B, C) + m_6(A, B, C)$$

Actually, we ONLY know how to build 2-input functions (NAND, NOR) and NOT (AND and OR).

PROVE that OR and AND are associative: then we can use 2-input gates.

MAXTERMS

We found a complete orthogonal set of functions, minterms.

Are there other complete orthogonal sets? YES.

A	B	C	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

six minterms

But

A	B	C	NOT(f)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

only 2 minterms

$\bar{A}\bar{B}\bar{C}$

$\bar{A}BC$


Simplify by noticing

$$\text{NOT}(\text{NOT}(f)) = f$$

$$f = \bar{\bar{f}} = \overline{\bar{A}\bar{B}\bar{C} + \bar{A}BC} \stackrel{\text{DeMorgan}}{=} \overline{\bar{A}\bar{B}\bar{C}} \cdot \overline{\bar{A}BC}$$

$$\stackrel{\text{DeMorgan}}{=} (A+B+C) \cdot (A+\bar{B}+\bar{C})$$

maxterms

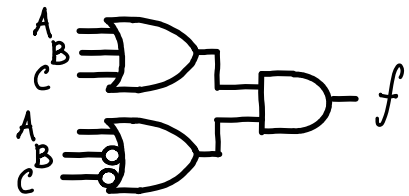

Maxterms are also a complete orthogonal set.

OR-AND Tree


AND-OR and OR-AND Trees can express any function:

====> { AND, OR, NOT } is a complete set of logical primitives


Simplifying Logic Circuits

DeMorgan's Laws can be used to change NAND to NOR and vice versa
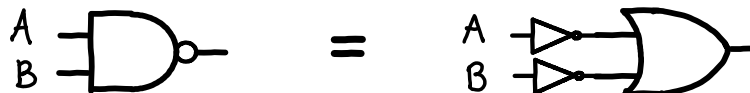
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



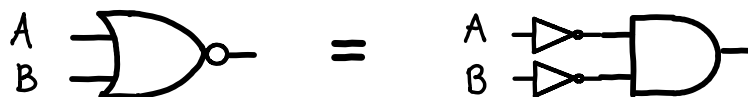
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



← push bubble to inputs


Combine with

$$f = \overline{\overline{f}}$$


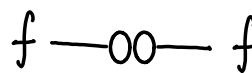


AND-OR \Rightarrow NAND-NAND


ADD BUBBLES

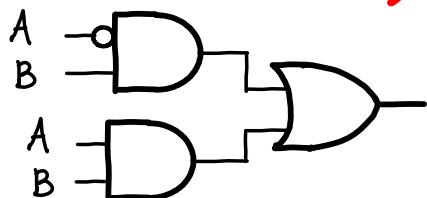

PUSH BUBBLES

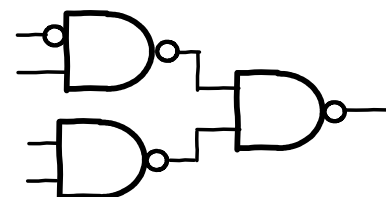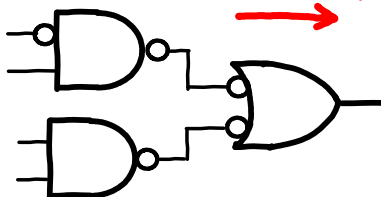

NAND can do NOT



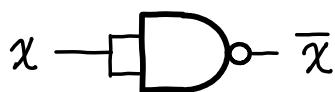


A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

NAND alone is a complete logic set.

OR-AND \Rightarrow NOR-NOR

NOR-NOR is also complete.

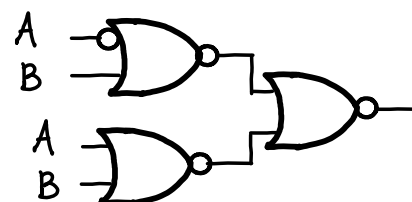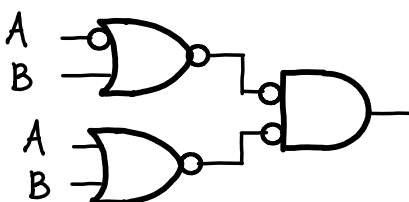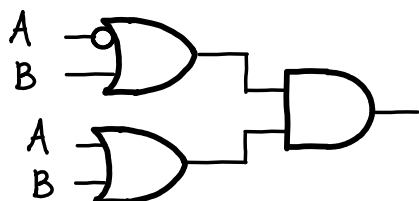

Karnaugh Maps are truth tables \implies See simpler logic.

Similar to extracting minterms, but not orthogonal.

Can be done algebraically, but usually harder.

Is there a general procedure for minimizing circuits? (Is it computable?)

A	B	f
0	0	f_0
0	1	f_1
1	0	f_2
1	1	f_3



		B	0	1
A	0	f_0	f_1	
	1	f_2	f_3	

IF

$$f_0 == f_1 == 1$$

THEN

$$f == 1 \text{ when } A = 0 \text{ (B doesn't matter)}$$

A	B	f
0	0	1
0	1	1
1	0	0
1	1	1



		B	0	1
A	0	1	1	
	1	0	1	

$$\bar{A} + B = f$$

Find a collection of terms that:

1. covers all ones
2. has the fewest terms,
each term covers as many 1s as possible

		C		0	1
A	B	00	1	1	0
		01	1	1	1
11	1	1	1	1	
10	0	0	1	1	

$\bar{A}\bar{C}$ (B changes, but f doesn't)

B (A and C change, but f doesn't)

AC (B changes, but f doesn't)

$$f = \bar{A}\bar{C} + B + AC$$

General Algorithm:

Quine-McClusky

