 


# Finite State Machine Implementation




Build TMs ==> Build FSMs

Symbol sets {a, b, c, d} ==> sets of bit strings {00, 01, 10, 11}

State sets {state-W, state-X, state-Y, state-Z} ==> {00, 01, 10, 11}

We need:

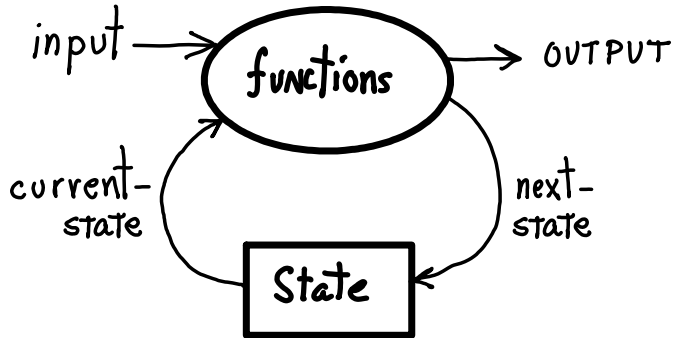- State Elements
- Boolean Functions (Next-State, Output)





FSM has input/output, but from/to where?

- (1) Other FSMs
- (2) Feedback loops

"Computers": Mentally Split State


**Control STATE** and  
"control" state elements  
next-state function

 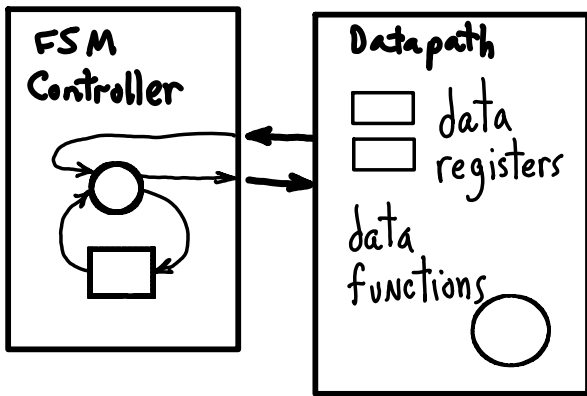**Data STATE**  
"data" state elements.  
data operation functions



# State Elements

gating  
a  
signal

 


$E = 1: Y = A$   
 $E = 0: Y = 0$

BUILD a State element that does not cause feedback problems: D-FF


We have an S-R latch:

 - $(S, R) == (0, 0) : Q$  is stable
- $(S, R) == (1, 0) : Q == 1$
- $(S, R) == (0, 1) : Q == 0$




We need to isolate its inputs:  
GATING

 - $E == 0 : Q$  is stable
- $E == 1 : Q$  can change



1-bit input:

 - $E == 0 : Q = D$
- $E == 1 : Q$  is stable





"D-latch w/ enable"

# 2-phase clocking


We need to prevent feedback from changing FSM state until we are ready.

A D-latch acts like a wire when  $E == 1$ .

State changes continually w/o control.

  

 Current state  $Q == 0$ . Next state = 1. Latches stable.




Current state  $Q == 0$ . Right latch propagates 1.

 
## 2-Phase Clocking

Independent signals for each latch's enable.

On breadboard:  
connect Es to different switches.



 
Current state  $Q == 0$ . Right latch stable.



Current state  $Q == 1$ . Left latch propagates  $1$ .  
Feedback may change  $D$ , but right latch is stable.

State  $Q$  changed when left  $E$  when from  $0$  to  $1$ .


implement 2-phase clock

 

Positive Edge-Triggered D FlipFlop

State  $Q$  changes when  
clock makes  $0-1$  transition

 Next state sampled on clock  $1-0$   
transition





Control if D-FF will be written.

Add a write-enable.

$we == 1$ :  $D$  propagates to input  
state changes

  
$we == 0$ :  $Q$  propagates to input  
state is stable



NO FEEDBACK path from  $Q$  to  $D$ ?

Can use D-latch instead.

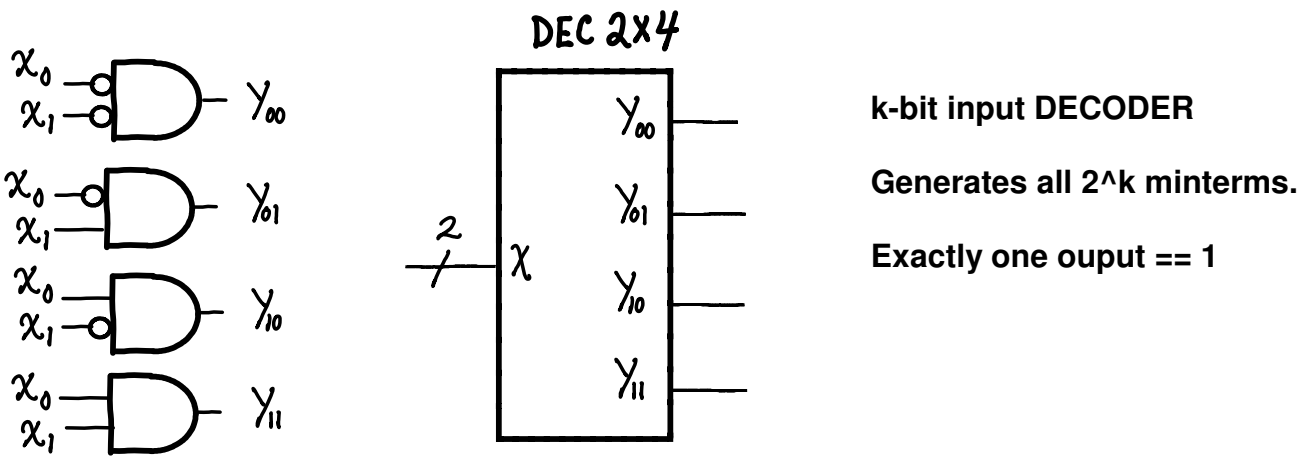
# implementing functions: DEC, PLA, MUX, ROM




PLA (Programmable Logic Array): **OR'ing minterms.**

Share logic to implement multiple functions.

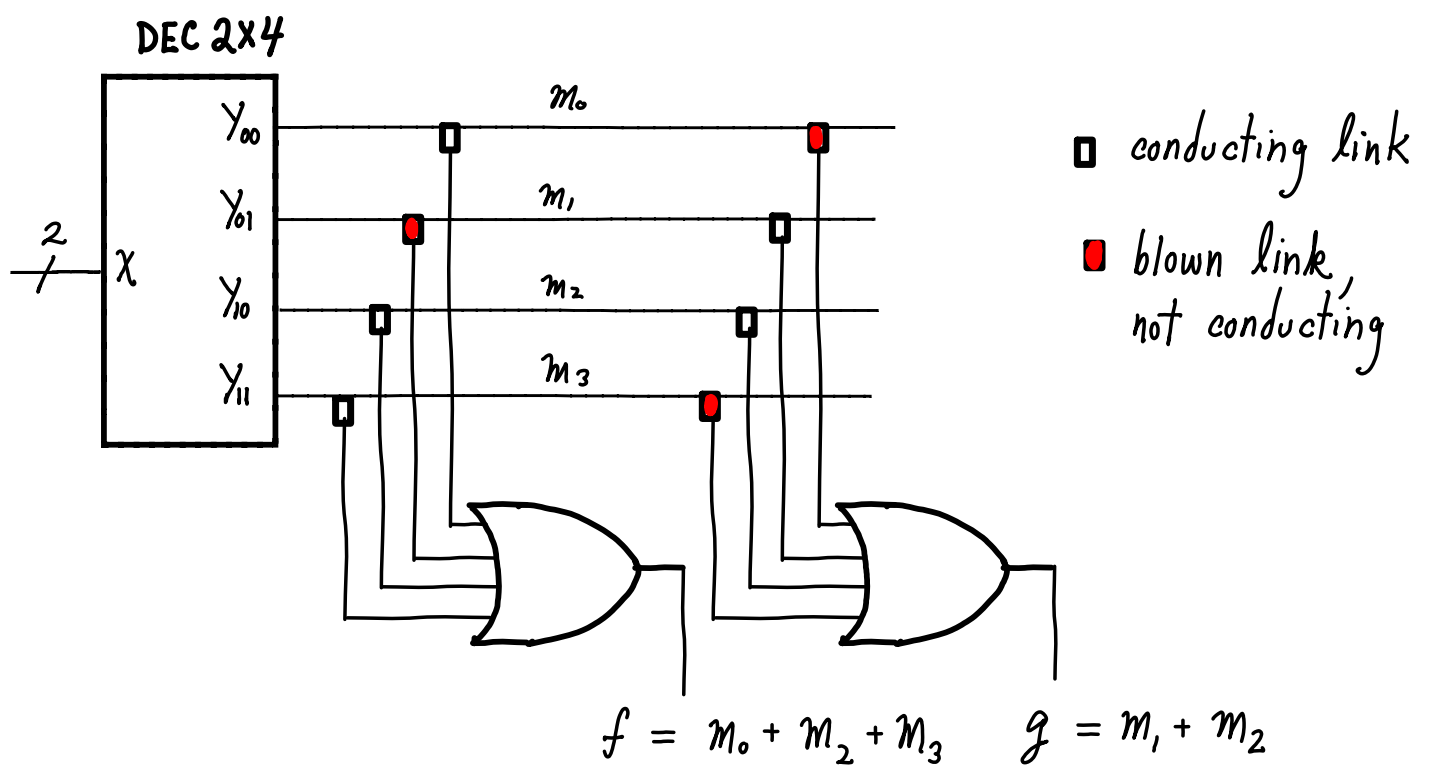
Programmable:  
minterm lines can be "blown" to disconnect them:  
select function's minterms.






# MUX

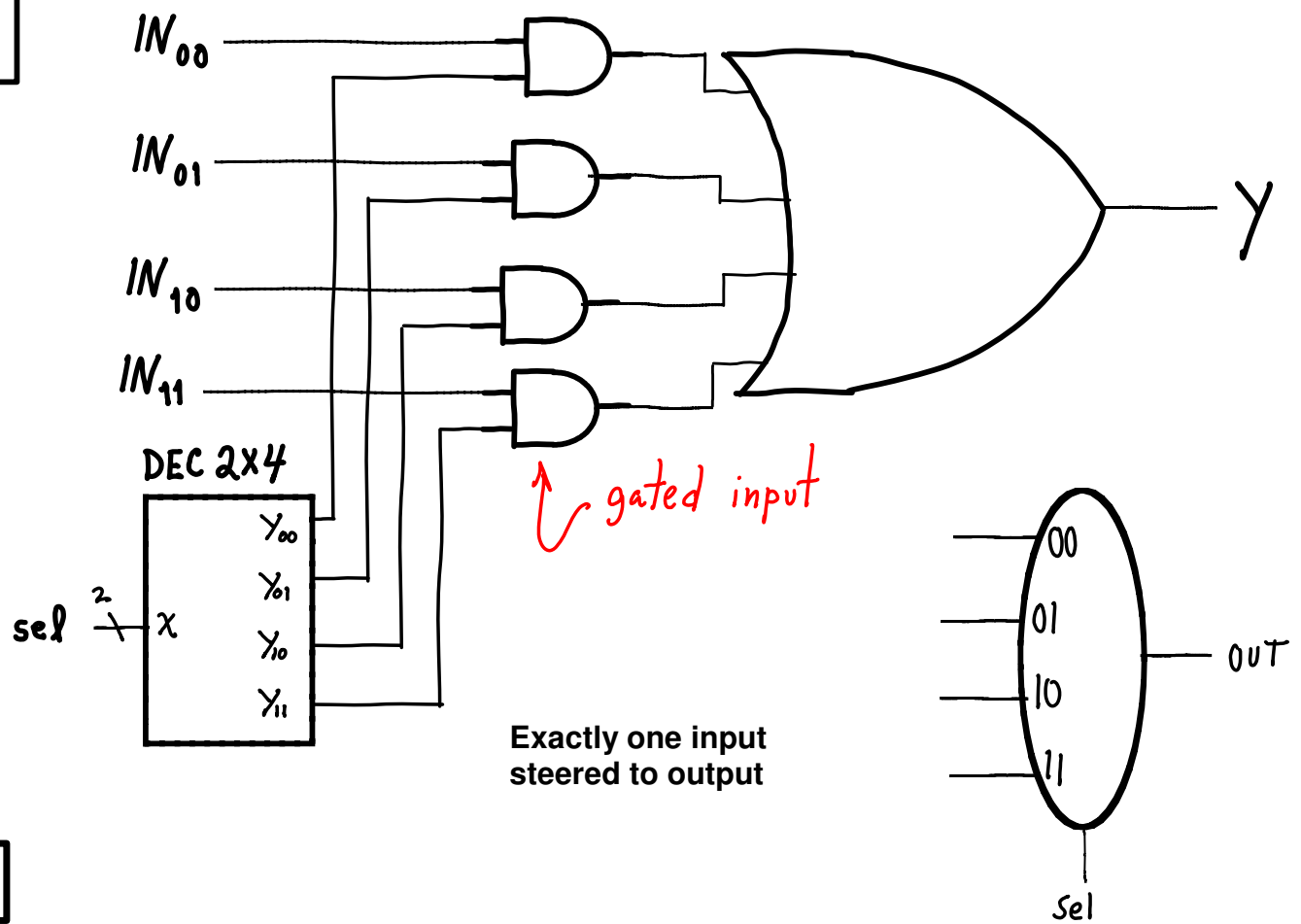

# ROM

 

addr	content
00	1
01	0
10	0
11	1

 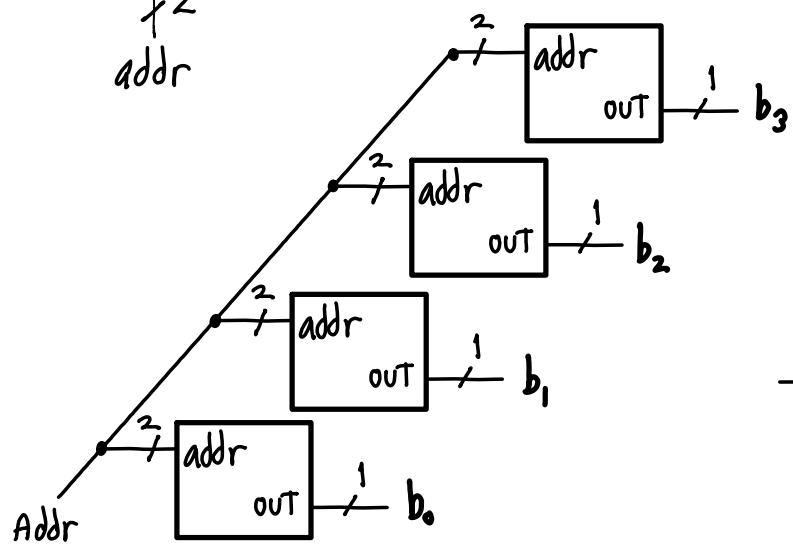 

addr	content
00	1 1 1 1
01	0 0 0 0
10	0 1 1 0
11	1 0 0 1

$b_3 \ b_2 \ b_1 \ b_0$

**FSM = ROM + STATE**

FSM functions as ROM




**i** input bits ( $2^i$  different inputs)

**n** state bits ( $2^n$  different states)

$(2^i) \times (2^n)$  combinations  
 $\implies 2^{(i+n)}$  words in ROM  
 $i+n$  address bits

ROM word == (next-state, output)

output for two functions

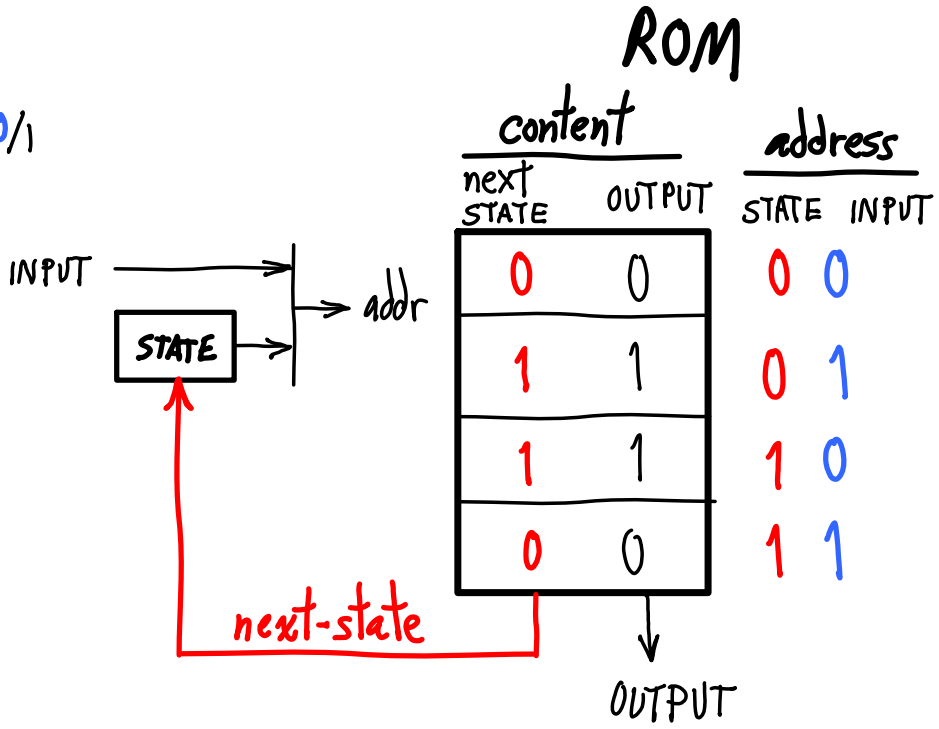 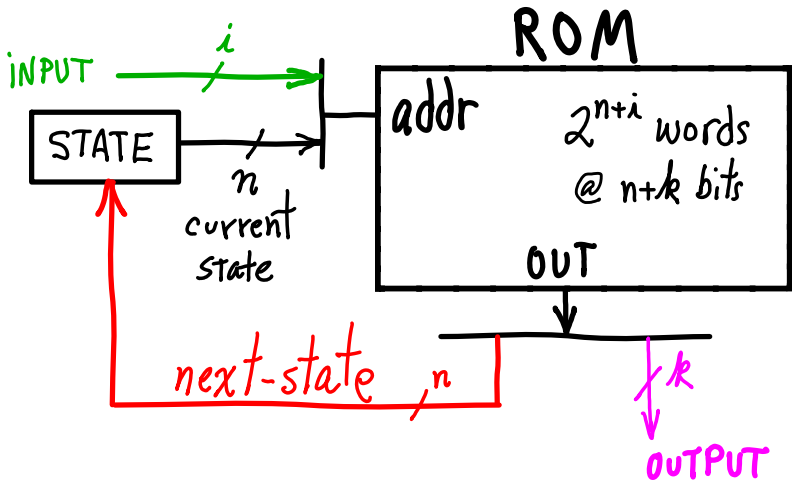

ANY FSM can be built:

ROM + STATE

One ROM word per (STATE, INPUT) combination

BUT, very big?

SMALLER?

One word per state (Moore Machine)?  
 Next-state function outside of ROM?

We can list all ROMs  $\implies$  list all FSMs  $\implies$  all TMs

ROM

address	content
00	00
01	11
10	11
11	00

Concatenate ROM content:  $\implies$  00111100

Each is an integer (make unique, no leading 0s)

